

Q) Simplify the following 5 variable expression using k-map

1) $T = f(a, b, c, d, e) = \sum (0, 2, 8, 10, 16, 18, 24, 26)$

~~ab~~ ~~cde~~

		000	001	011	010	100	101	111	110	
		00	01	11	10	00	01	11	10	
Poly	f	00	1	0	3	2	4	0	5	7
		1	0	1	0	1	0	0	1	0
Poly	f	11	4	5	22	20	1	29	31	30
		1	0	0	1	0	0	0	0	0
Poly	f	10	16	17	19	18	20	21	23	22
		1	0	0	0	0	0	0	0	0

$$T = \overline{c}e$$

2) $R = f(w, x, y, z) = \sum (5, 7, 13, 15, 21, 23, 29, 31)$

~~vw~~ ~~xyz~~

		000	001	011	010	100	101	111	110			
		00	01	11	10	00	01	11	10			
Poly	f	00	0	1	0	3	2	4	0	5	7	6
		8	9	0	0	11	10	12	13	15	14	0
Poly	f	11	24	25	27	26	28	29	31	30	0	0
		0	0	0	0	0	0	1	1	1	0	0
Poly	f	10	16	17	19	18	20	21	23	22	0	0
		0	0	0	0	0	1	1	1	1	0	0

$$R = xz$$

3) $w = f(a, b, c, d, e) = \sum (1, 3, 4, 6, 9, 11, 12, 14, 17, 19, 30, 28, 20, 22, 25)$

~~ab~~ ~~cde~~

		000	001	011	010	100	101	111	110	
		00	01	11	10	00	01	11	10	
Poly	f	00	0	1	1	0	2	1	0	1
		0	1	1	0	1	0	0	1	0
Poly	f	11	0	1	1	0	1	0	0	1
		0	1	1	0	1	0	0	1	0
Poly	f	10	0	1	1	0	1	0	0	1
		0	1	1	0	1	0	0	1	0

$$w = \overline{c}e + c\overline{e}$$

$$= c \oplus e$$

$$4) j = f(w, w, x, y, z) = \sum (4, 5, 6, 7, 9, 11, 13, 15, 25, 27, 29, 31)$$

$\checkmark w \checkmark y \checkmark z$

	000	001	011	010	100	101	111	110
00	0	0	0	1	1	1	1	0
01	0	1	1	0	0	1	1	0
11	0	1	1	0	0	1	1	0
10	0	0	0	0	0	0	0	0

$$\begin{aligned}
 j &= \cancel{w} \bar{x} \bar{z} + \bar{w} \bar{x} + \cancel{w} x z \\
 &= \cancel{w} (\bar{x} + x) + \bar{w} \bar{x} \\
 j &= \cancel{w} \bar{z} + \bar{w} \bar{x} = w \bar{z} (\bar{x} + x) + \bar{w} \bar{x} \\
 &\underline{\quad j = w \bar{z} + \bar{w} \bar{x}}
 \end{aligned}$$

④ Incompletely specified functions (Don't care terms) →

- * When an output value is known for every possible combination of input variables the function is said to be completely specified.
- + However, when an output value is not known for every combination of input variable usually because all combinations cannot occur, the function is said to be incompletely specified.
- + This means that the truth table does not generate an output value for every possible input combination.
- + The min terms or max terms that are not used as part of the output function are called don't care terms.

Ex:

The truth table for binary (to Ex-3) BCD
is shown below!

Binary

Ex-3 BCD

w	x	y	z
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

A	B	C	D
0	0	0	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0

Don't care terms

11	11	11
11	11	11
11	11	11
11	11	11
11	11	11

$$A = f(w, x, y, z) = \sum (5, 6, 7, 8, 9) + \sum d(10, 11, 12, 13, 14, 15)$$

w	x	y	z
00	00	00	00
01	01	11	11
11	d	d	d
10	11	d	d

$$A = w + xz + xy$$

$$B = f(w, x, y, z) = \sum (1, 2, 3, 4) + \sum (10, 11, 12, 13, 14, 15)$$

		00	01	11	10
		00	01	11	10
		00	01	11	10
w	x	0	1	1	1
y	z	1	0	0	0
d	d	d	d	d	d
00	01	11	10		

$$B = \overline{xyz} + \overline{x}z + \overline{xy}$$

$$\cancel{B = \overline{wxyz} + \overline{wx}y + x\overline{yz} + wz}$$

$$C = f(w, x, y, z) = \Sigma(0, 3, 4, 7, 8) + \Sigma(10, 11, 12, 13, 14, 15)$$

		00	01	11	10
		00	01	11	10
		00	01	11	10
w	x	0	1	1	0
y	z	1	0	1	0
d	d	d	d	d	d
00	01	11	10		




$$\cancel{C = \overline{yz} + yz}$$

$$d = f(w, x, y, z) = \Sigma(0, 2, 4, 6, 8) + \Sigma(10, 11, 12, 13, 14, 15)$$

		00	01	11	10
		00	01	11	10
		00	01	11	10
w	x	0	1	0	1
y	z	1	0	1	1
d	d	d	d	d	d
00	01	11	10		

$$\cancel{D = \overline{y} \cdot \overline{z}}$$

Circuit diagram → (SOP)

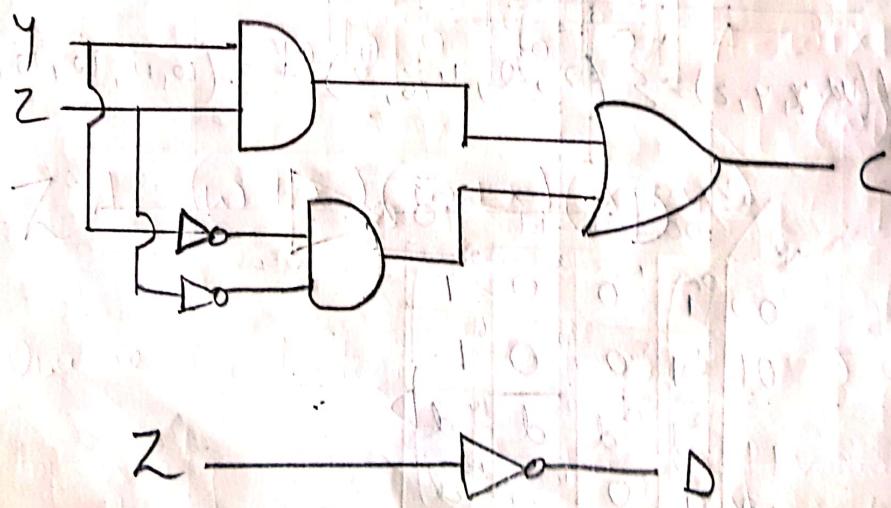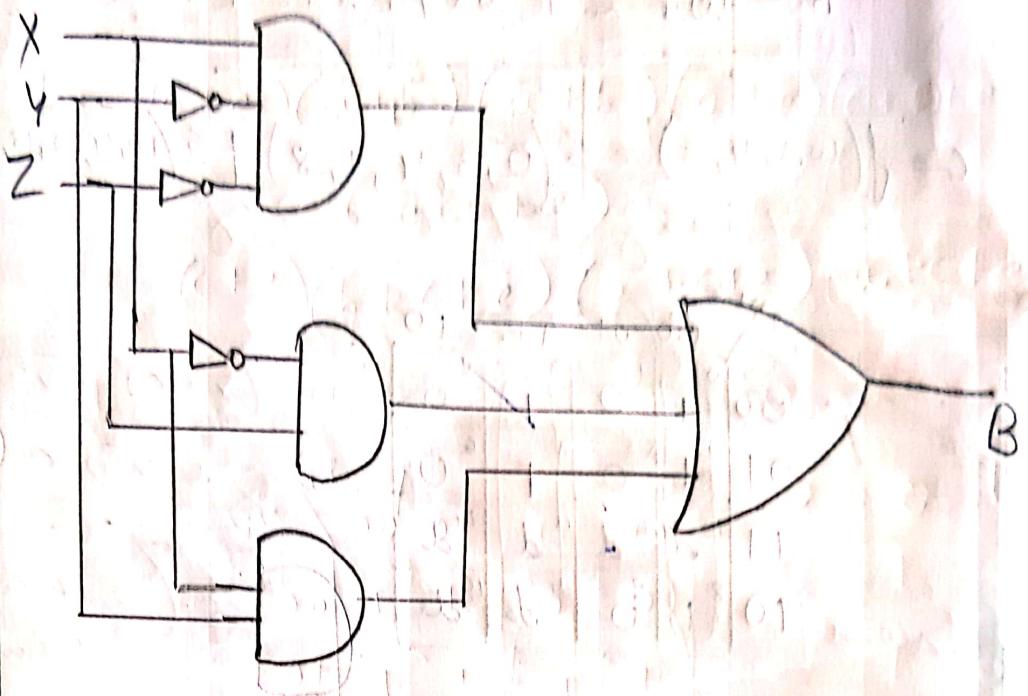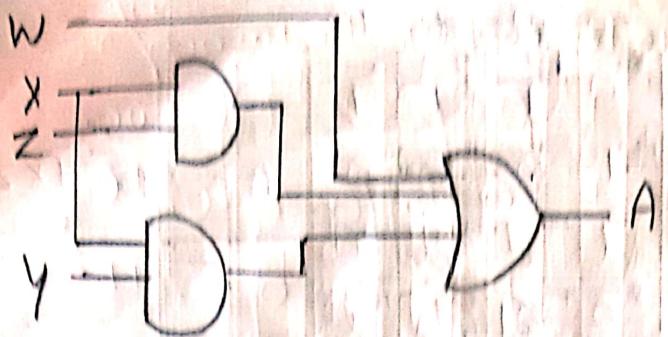

④

Simplify the max term equation

11

$$f(x, y, z) = \bar{x}(\bar{y}, \bar{z}) + \bar{y}(x, \bar{z}) + \bar{z}(x, y)$$

x^2	00	01	11	10
0	0	1	2	2
1	0	1	0	1

$$\underline{J = (\bar{y} + \bar{z})(y + z)}$$

$$2) G_1 = \overline{f(a, b, c, d)} = \pi(10, 4, 5, 7, 8, 9, 11, 12, 13, 15)$$

	00	01	11	10
00	0	1	3	2
01	4	0	7	6
11	2	0	5	4
10	8	0	6	0

$$G = (c+d) \neq (\bar{b}+\bar{a})(\bar{a}+\bar{d})$$

w_x	u^2	00	0-1	11	10	01	11
00	1	0	0	3	2	0	0
01	1	5	1	7	6	0	0
11	9	13	0	15	0	14	0
00	10	9	x	11	10	0	0

$$T = (\omega + x + \bar{z}) (\bar{\omega} + z) \\ (\bar{\omega} + \bar{x})$$

$$\cancel{F \geq W} \cancel{\wedge} H \cdot (W + X) \cancel{C}$$

$$4) L \hat{=} f(a, b, c, d, e) = tc(0, 2, 4, 6, 8, 9, 10, 11, 12, 14, 16, 17, \\ 18, 19, 24, 25, 26, 27)$$

$$5) A = f(w, x, y, z) = \text{TC}((2, 3, 8), 9, 10, 11, 12, 13, 14, 15)$$

4) ab'cd'e'

	00	01	011	010	100	1001	1111	110
00	0	1	1	0	0	1	1	0
01	0	0	11	10	0	13	15	0
11	0	0	0	0	1	1	1	1
10	0	0	17	19	18	22	23	22

$$L = \cancel{(c+e)(\bar{a}+\bar{b})(\bar{a}+\bar{b})(\bar{a}+b)(c+a+e)} \\ L = \underline{(c+e)(\bar{b}+c+\bar{e})(\bar{a}+c+\bar{e})(a+\bar{c}+e)}$$

5)

	w	x	y	z
00	00	01	.11	10
00	0	1	1	0
01	a	1	5	7
11	12	13	15	14
10	8	9	11	10

~~A = (wz*)~~
~~A = (w+x+y)~~
~~(\bar{w})*~~
~~A = (\bar{w} + \bar{x})(\bar{w} + x)(x + y)~~

④ Quine-McCluskey Technique \Rightarrow

- + For many applications the no. of variables in the problem is too large to simplify manually using k-maps
- + K-maps although capable of adding any no. of variables become difficult beyond 6

in 7 variables.

- + ∵ Some automatic or computer driven simplification routine is desirable.
- + The Quine-McCluskey minimization technique is an algorithm that uses the same boolean algebra postulates that were used with k-maps, but in a form suitable for a computer solution.
- + Large k-maps require recognition of group of terms that may form EPI.
- + The larger the map the more difficult this pattern recognition becomes.
- + This pattern recognition eliminates the need for such pattern recognition.

④ Ex:- Simplify the following using Quine McCluskey minimization technique.

$$D = f(a, b, c, d) = \sum(0, 1, 2, 3, 6, 7, 8, 9, 14, 15)$$

Group	Minterm	Variables				
			a	b	c	d
0	0		0	0	0	0 ✓
1	1		0	0	0	1 ✓
2	2		0	0	1	0 ✓
	8		1	0	0	0 ✓
2	3		0	0	1	1 ✓
	6		0	1	1	0 ✓
	9		1	0	0	1 ✓

3	7, 14	0, 1, 14, 14	0, 1, 1, 0	0, 1, 1, 0
4	15	1, 1, 1, 1	1, 1, 1, 1	1, 1, 1, 1
Group	n unique	variables	a	b
0	0, 1 0, 2 0, 8	0, 0, 0	0, 0, 0	0, 0, 0
1	1, 3 1, 9 2, 3 2, 6 8, 9	0, 0, 0, 0, 0	0, 0, 0, 1, 0	0, 0, 0, 0, 0
2	3, 7 6, 7 6, 14	0, 0, 0	0, 1, 1, 0	1, 0, 0, 0
3	7, 15 14, 15	—	1, 1, 1	1, 1, 1
4	0, 1, 2, 3 0, 1, 8, 9 0, 2, 1, 3 0, 9, 1, 9	0, 0, 0, 0	0, 0, 0, 0	0, 0, 0, 0

1	2, 6, 3, 7	0	-	1	-
2	6, 7 , 14, 15	-	1	1	-
	6, 14, 7, 15	-	1	1	-

- * All non-checked minterm groups are now considered to be Prime Implicants.
- + All of the prime implicants are joined into a prime implicant table as shown below.

PI terms	Decimal Minterms	Decimal Minterm									
		0	1	2	3	6	7	8	9	14	15
$\bar{a}\bar{b}$	0, 1, 2, 3	x	x	x	x						
$\bar{b}\bar{c}$	0, 1, 8, 9	x	x							(x) (x)	
$\bar{a}c$	2, 6, 3, 7		x	x	x	x					
$b\bar{c}$	6, 7, 14, 15					x	x			(x) (x)	

- + The PI table test each of the minterms contained in the original switching equation across the top of the table.
- + Each PI is listed vertical in 2 rows, PI terms & the decimal list of minterms that make up the PI.
- * Evaluate the PI by reading those minterms that are contained in only one PI.
(only one x in a column)
- + These circled minterms represent Essential Prime Implicants (EPI).
- + Minterms $(0, 1, 8, 9) \rightarrow \bar{b}\bar{c}$ ← minterms
 $(6, 7, 14, 15) \rightarrow b\bar{c}$
are EPI

$$D = \overline{b} \overline{c} + bc + \overline{a} b$$

$$D = \overline{b} \overline{c} + bc + \overline{a} c$$


19/8/19

Module - 02Decoders

- * Decoders → Are a class of combinational logic circuits that convert a set of input variables representing a code into a set of output variables representing a different code.


- + Encoded information is presented as 'n' inputs producing 2ⁿ outputs.
- + The 2ⁿ output values can range from 0 to 2ⁿ-1.

- * Typical decoder ⇒

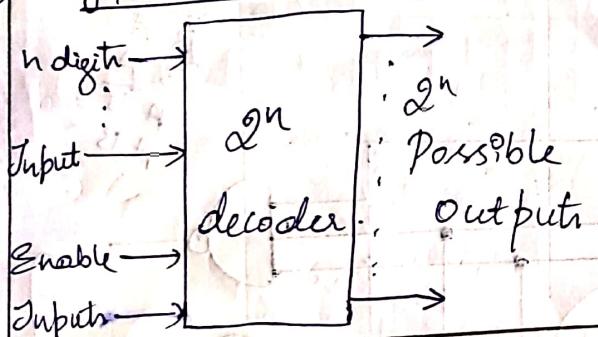


- * The above fig. shows a dual 2 to 4 decoder IC, 74XX139.
- * One & only one of the outputs, Y₀ to Y₃ is active for a given input.
- * Y₀ is asserted when inputs A = B = 0 & the active low enable input Tr = 0.

- * JEE Logic symbol ⇒

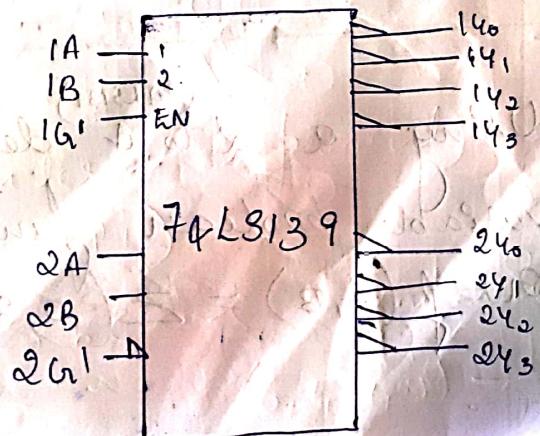


Inputs			Outputs			
Enable	select		y_0	y_1	y_2	y_3
G ₁	B	A				
H	X	X	H	H	H	H
L	L	L	L	H	H	H
L	L	H	H	L	H	H
L	H	L	H	H		
L	H	H	H	H	L	H

Function Table

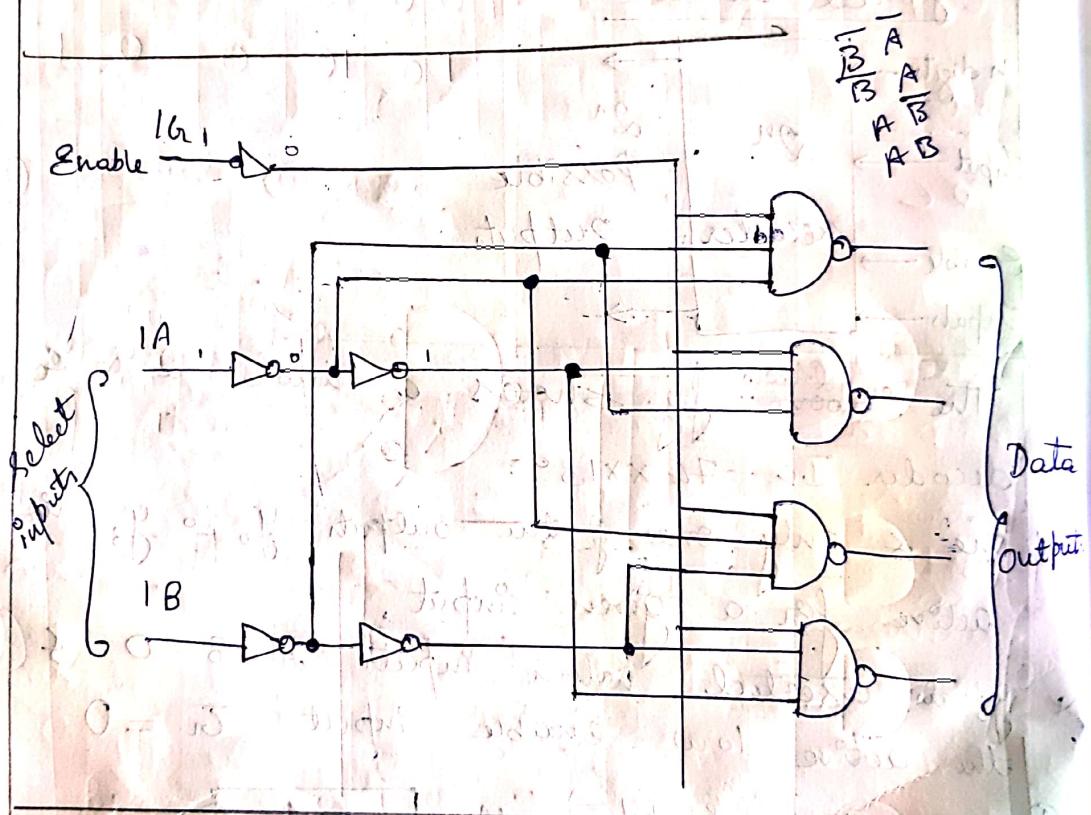

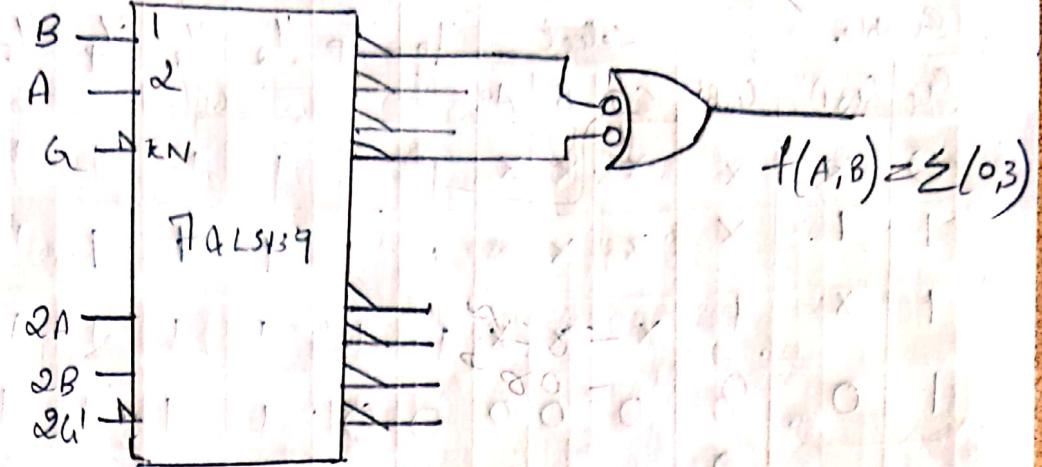- ④ Using a 2×4 decoder realize a two variable boolean function,
 $OR = f(A, B) = \sum(0, 3)$



$$\text{Or} = f(A, B) = \Sigma(0, 3) = \bar{A}\bar{B} + AB$$

- ④ The 74xx138 is a 3 to 8 decoder IC.
- The 3 inputs are decoded to produce one of the 8 outputs.
- 3 enable inputs are provided all of which must be active before decoding can occur.
- The logic circuit, symbol & function table is shown below.



⑤ Function Table \Rightarrow


Inputs

Outputs

Enable	Select			y_0	y_1	y_2	y_3	y_4	y_5	y_6	y_7
	G_1	G_2A'	G_2B'	C	B	A					
0	x	x	x	x	x	x	1	1	1	1	1
1	1	1	x	x	x	x	1	1	1	1	1
1	x	1	x	x	x	x	1	1	1	1	1
1	0	0	0	0	0	0	0	1	1	1	1
1	0	0	0	0	1	0	1	0	1	1	1
1	0	0	0	1	0	1	1	0	1	1	1
1	0	0	0	1	1	1	1	0	1	1	1
1	0	0	0	0	0	1	1	1	0	1	1
1	0	0	0	0	1	0	1	1	1	0	1

④


Circuit diagram \Rightarrow

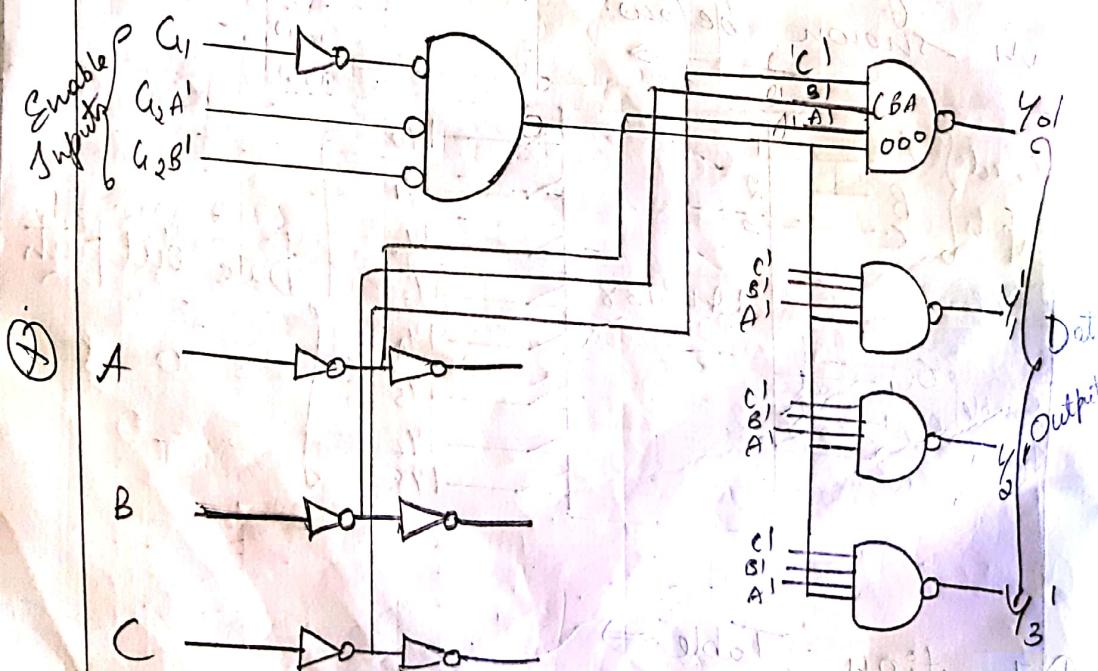


⑤

Using a 3 to 8 decoder Simplify the following boolean expression,

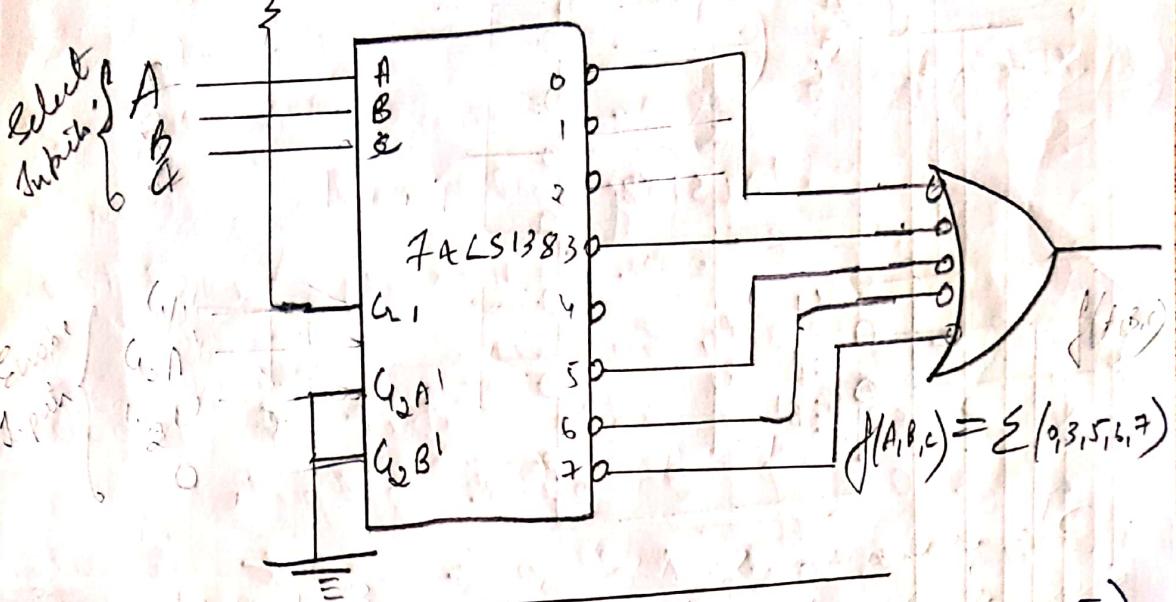
$$x = f(a, b, c) = \sum (0, 3, 5, 6, 7)$$



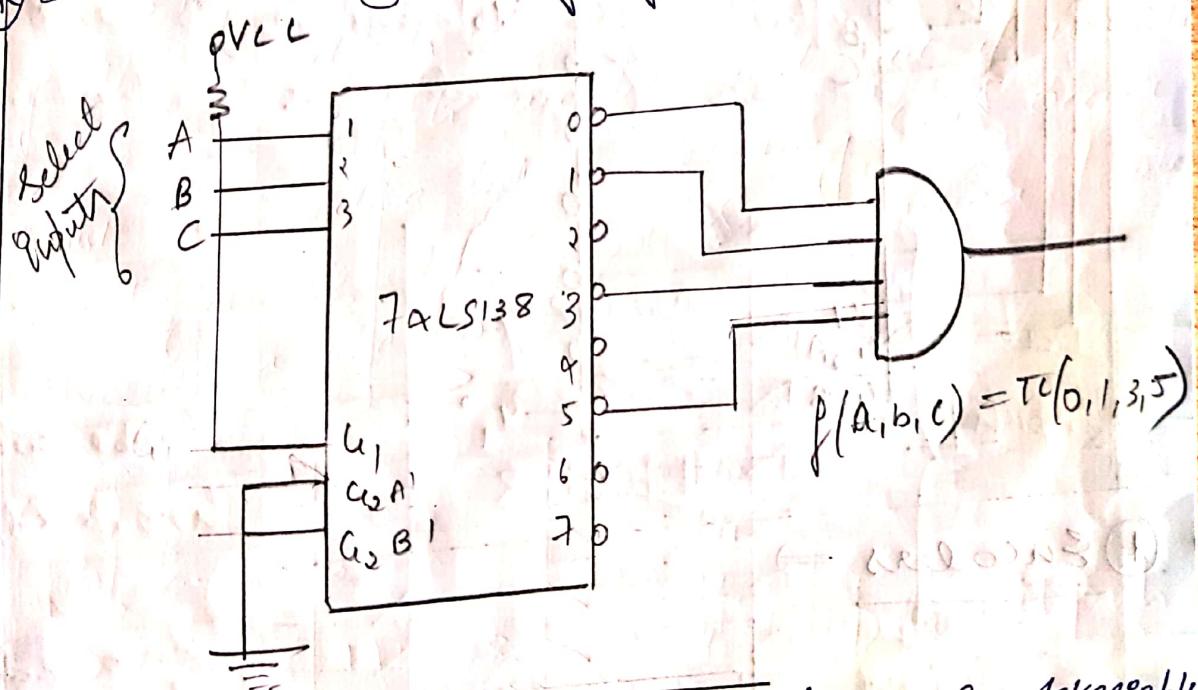
* Decoder realization of $f(a, b, c) = \sum (0, 1, 3, 5)$



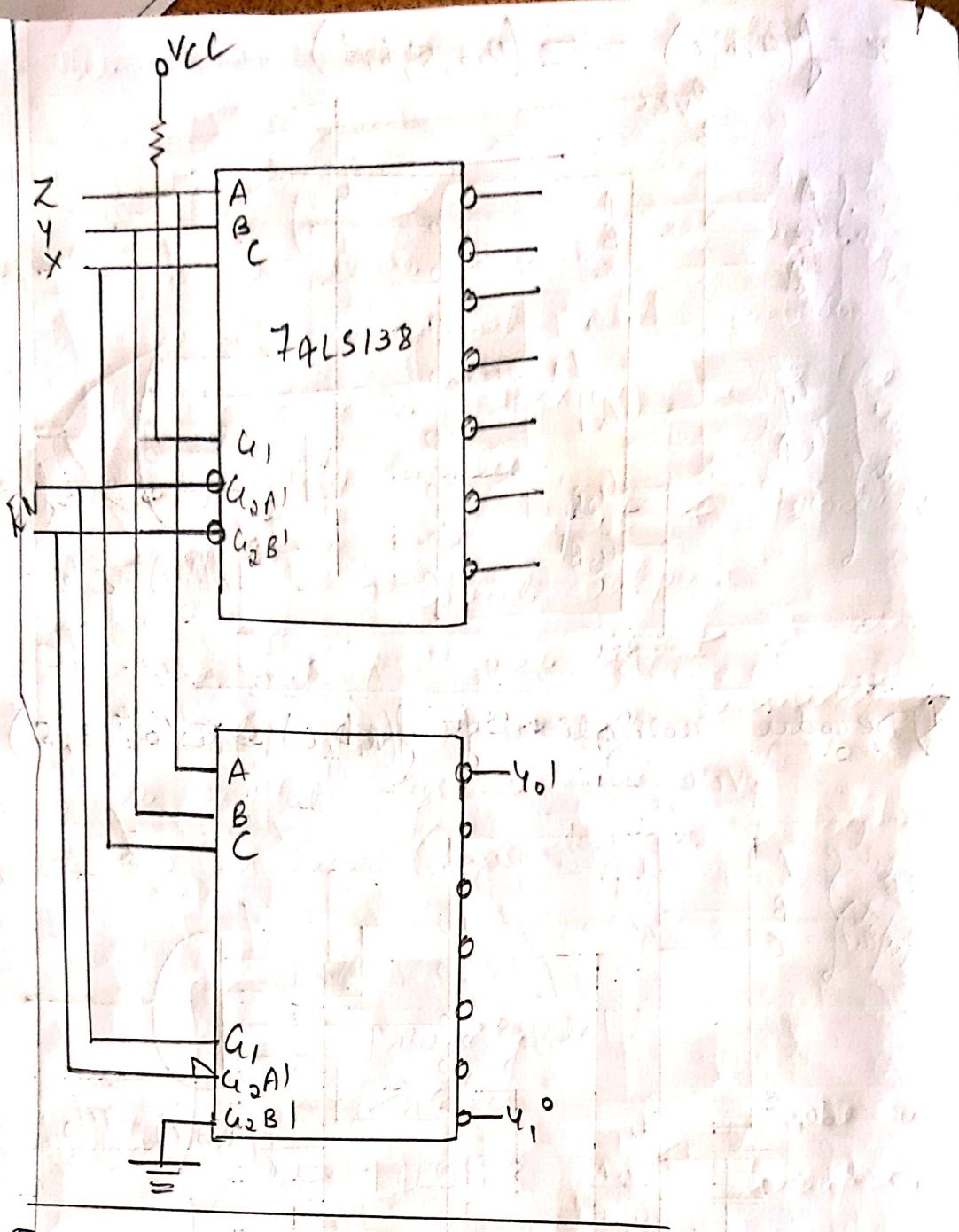- ① Using 2 74XX138 decoders realize a 4-variable multiple output function.



* Encoders \Rightarrow

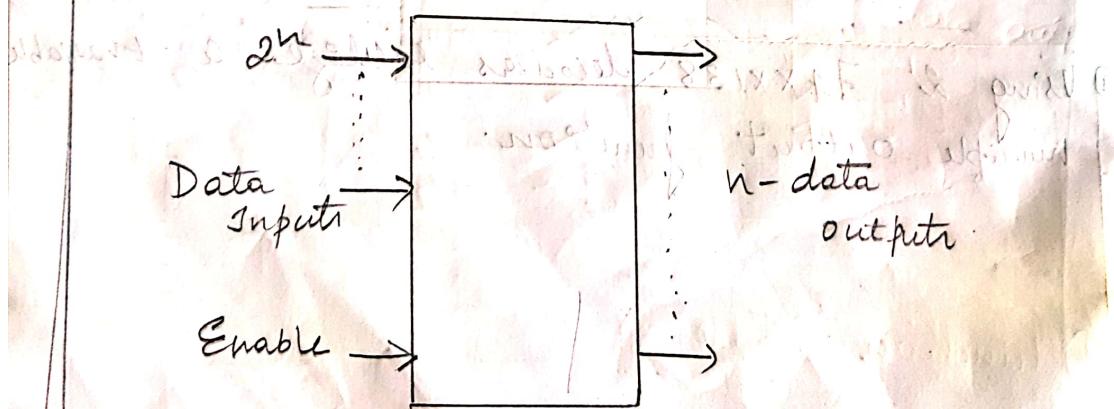


Encoders perform a function that is

Inverse of decoders.

+ An Encoder produces 'n' outputs from 2 inputs as shown in fig below.

+ The logic diagram of 74XX147, IEE symbol & function table is shown in fig below. (A 10 -line \rightarrow BCD encoder)

(Circuit diagram
refer text book)

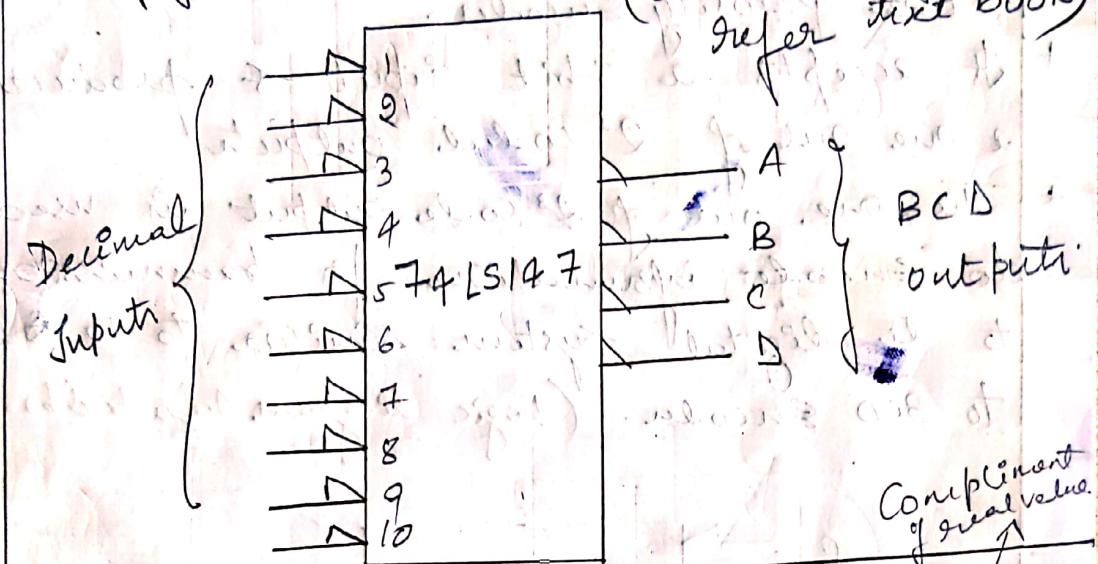


Decimal value	Inputs									Outputs			
	1	2	3	4	5	6	7	8	9	D	C	B	A
0	1	1	1	1	1	1	1	1	1	1	1	1	1
1	0	1	1	1	1	1	1	1	1	1	1	1	0
2	1	0	1	1	1	1	1	1	1	1	1	0	1
3	1	1	0	1	1	1	1	1	1	1	1	0	0
4	1	1	1	0	1	1	1	1	1	0	1	1	1
5	1	1	1	1	0	1	1	1	1	0	1	0	0
6	1	1	1	1	1	0	1	1	1	0	0	1	1
7	1	1	1	1	1	1	0	1	1	0	0	0	0
8	1	1	1	1	1	1	1	0	1	0	1	1	1
9	1	1	1	1	1	1	1	1	0	0	1	1	0

$9 \rightarrow 1001$
complement of real value

* The 9 input lines to the encoder

⊕ Priority Encoder \Rightarrow

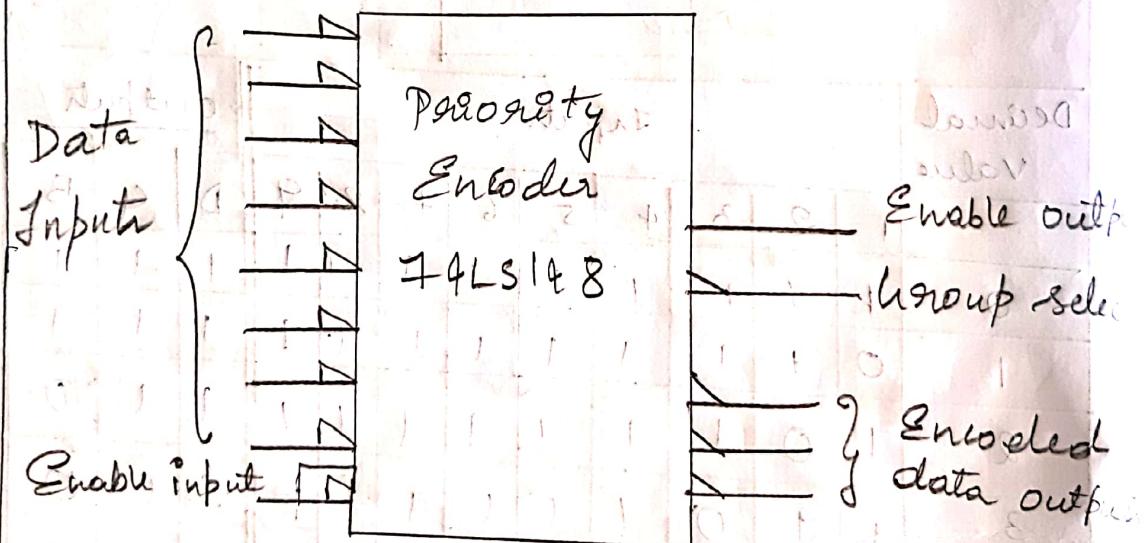
- * The below figure shows the logic diagram, logic symbol and function table of priority Encoder (74xx148), a 3 line to 3 line priority encoder.
- + It accepts a 3-bit input & produces a one out of 2^3 coded outputs
- * The one out of 2^3 code output is used to encode information for transmission to a digital system similar to 10 bits to BCD Encoder. (Logic diagram refer textbook)




Inputs								Outputs (Priority)			If busy (Priority)			
	E _i	0	1	2	3	4	5	6	7	A ₂	A ₁	A ₀	GS	EO
1	X	X	X	X	X	X	X	X	X	1	1	1	1	1
0	1	1	1	1	1	1	1	1	1	1	1	1	1	0
0	0	1	1	1	1	1	1	1	1	1	1	1	0	1
0	X	0	1	1	1	1	1	1	1	1	1	0	0	1
0	X	X	0	1	1	1	1	1	1	1	0	1	0	1
0	X	X	X	0	1	1	1	1	1	0	0	0	0	1
0	X	X	X	X	0	1	1	1	1	0	1	1	0	1
0	X	X	X	X	X	0	1	1	1	0	1	0	0	1
0	X	X	X	X	X	X	0	1	1	0	0	1	0	1

- * The output \overline{GS} goes low when any of the inputs to the encoder is active.
- + The purpose of the signal is to communicate to the control system logic that an event has occurred & priority encoded data are present.
- + When EO is active no priority event come feed to the IC if present. It is used as enable input to the next lower priority encoder.
- * EO is an active low signal that can be used to cascade several devices to form a larger priority Encoding System.

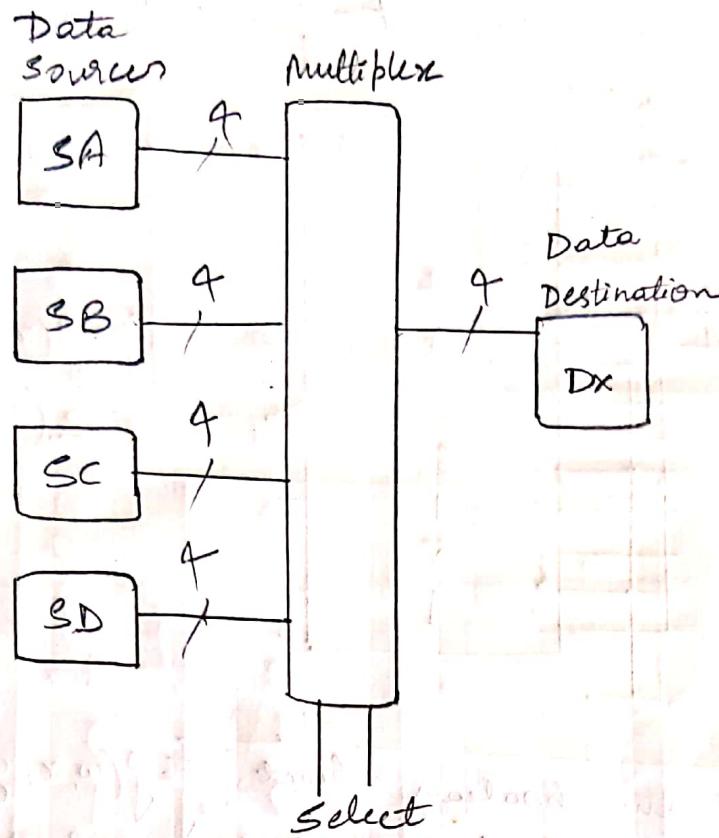④ 4-bit data sources multiplex to a single 4-bit destination ⇒




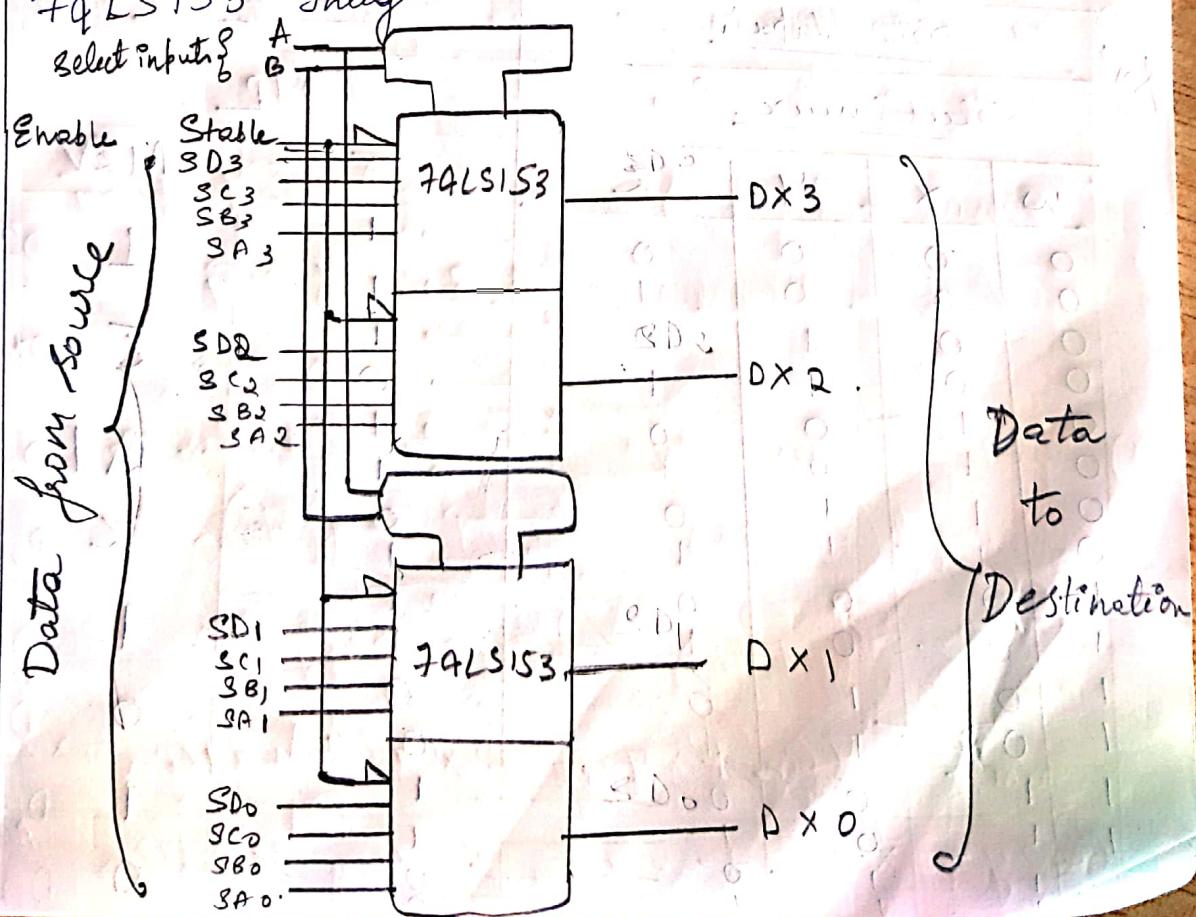⑤ A 4-bit multiplexer system using 2 74LS153 Integrated circuits.



(*) Problem →

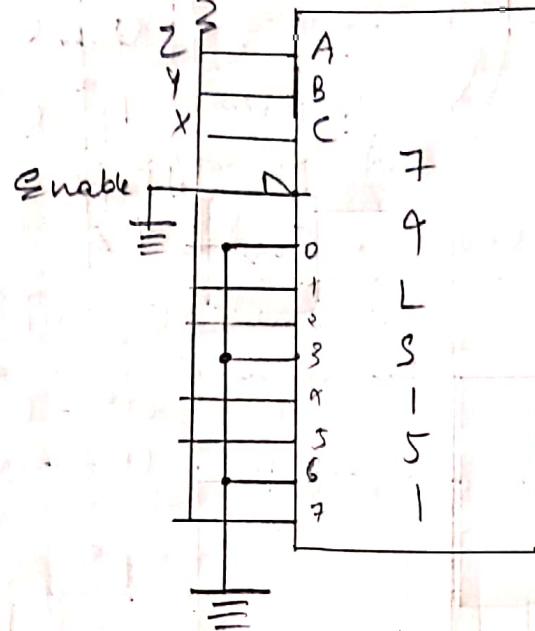Using an 8:1 mux to realize the boolean function $F = f(x, y, z) = \sum(1, 2, 4, 5, 7)$




$$F = f(x, y, z) = \sum(1, 2, 4, 5, 7)$$

g) Realize the boolean funct $T = f(w, x, y, z) = \sum(0, 1, 2, 4, 5, 7, 8, 9, 12, 13)$ using 8:1 mux (74LS151)

~~Soln~~

Data Inputs				Data outputs	
Select mux.				O/P	
w	x	y	z	T	MEX
0	0	0	0	0 → 1	1 - D ₀
0	0	0	1	1 → 1	1 - D ₁
0	0	1	0	2 → 1	1 - D ₂
0	0	1	1	3 → 0	1 - D ₃
0	1	0	0	4 → 1	1 - D ₄
0	1	0	1	5 → 1	1 - D ₅
0	1	1	0	6 → 0	1 - D ₆
0	1	1	1	7 → 1	1 - D ₇
1	0	0	0	9 → 1	1 - D ₈
1	0	0	1	10 → 1	1 - D ₉
1	0	1	0	11 → 0	0 - D ₁₀
1	0	1	1	12 → 0	0 - D ₁₁
1	1	0	0	13 → 1	1 - D ₁₂
1	1	0	1	14 → 1	1 - D ₁₃
1	1	1	0	15 → 0	0 - D ₁₄

VLC

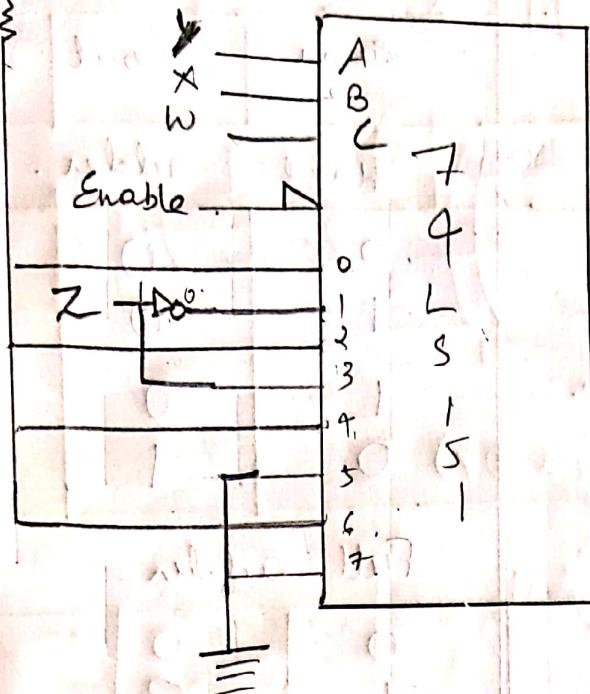

$$F = f(w, x, y, z)$$

$$= \sum(6, 11, 12, 14, 15, \\ 7, 18, 9, 10, 13)$$

④ Adder And Subtractors \Rightarrow

- * Adding two single bit binary values produces a sum & a carry output.
- * This operation is called a Half Adder & the circuit that realises the function is called a Half Adder.
- + Adding two single bit binary values with the inclusion of a carry input produces 2 outputs: a sum & a carry.
- + This circuit is called a Full Adder.
- + The truth table for Half & Full Adder is given below.

⑤ Truth Table \Rightarrow

X	Y	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Inputs			Outputs		
x	y	Cin	Sum	Cout	
Half adder.			Half adder.		
0	0		0	0	
0	1		1	0	
1	0		1	0	
1	1		0	1	
Full adder.			Full adder.		
0	0	0	0	0	
0	0	1	1	0	
0	1	0	1	0	
0	1	1	0	1	
1	0	0	1	0	
1	0	1	0	1	
1	1	0	0	1	
1	1	1	1	1	

④ The boolean equations for the outputs is given below,

$$\text{Sum} = f(x, y) = \sum (1, 2) = \bar{x}y + x\bar{y}$$

$$\text{Cout} = f(x, y) = \sum 3 = xy$$

⑤ The boolean eqn for full adder is,


$$\text{Sum} = f(x, y, \text{Cin}) = \sum (1, 2, 4, 7)$$

$$\text{Cout} = f(x, y, \text{Cin}) = \sum (3, 5, 6, 7)$$


$$\text{Sum} = \bar{x}\bar{y}\text{Cin} + \bar{x}y\bar{\text{Cin}} + x\bar{y}\bar{\text{Cin}} + xy\text{Cin} \text{ or } x\oplus y \oplus \text{Cin}$$

$$\text{Carry} = \bar{x}y\text{Cin} + x\bar{y}\text{Cin} + x\bar{y}\bar{\text{Cin}} + xy\text{Cin}$$


* Half Adder logic diagram →

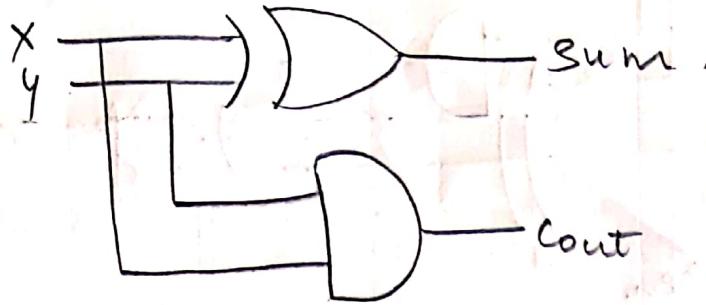


* Full Adder logic diagram →

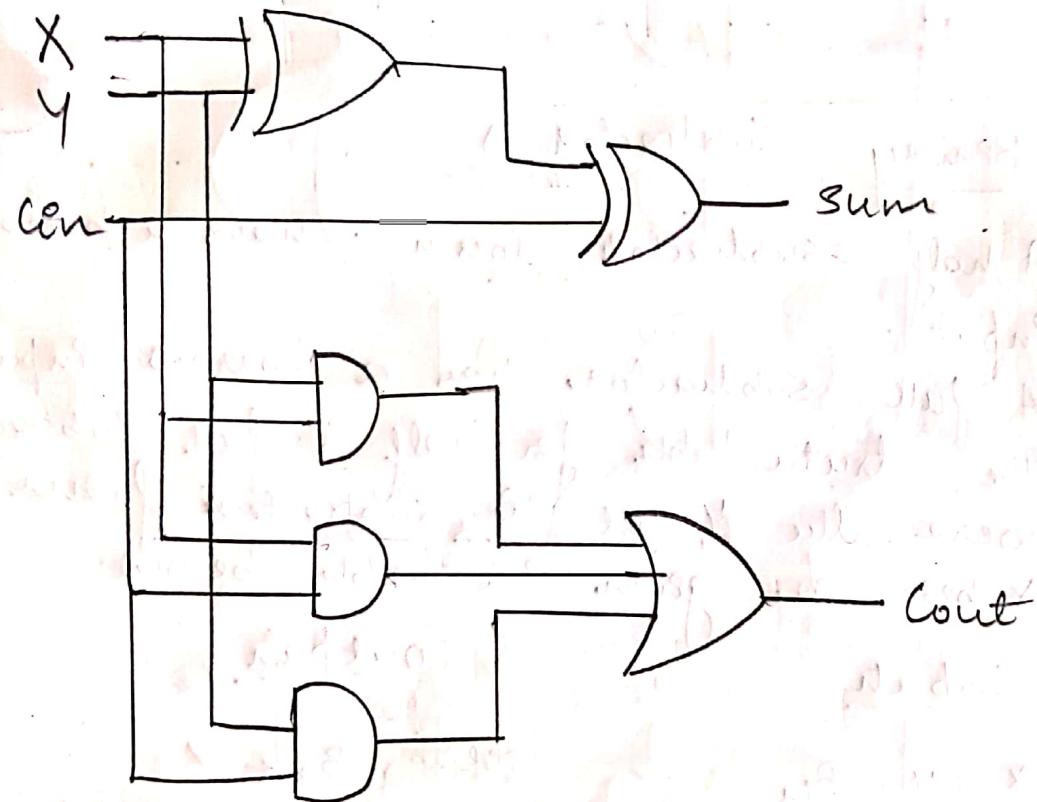

④ Design a Full Adder using Half Adder →

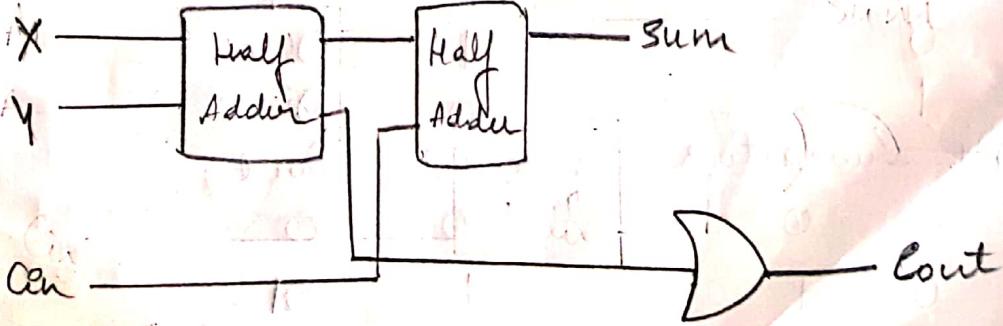

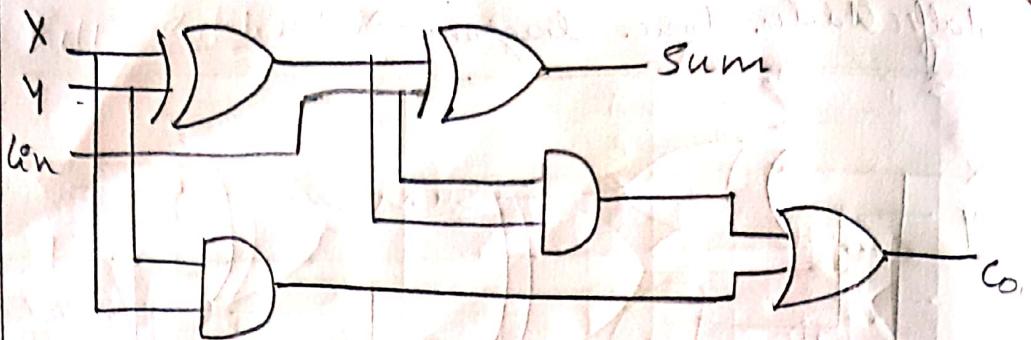

$$\text{sum} = X \oplus Y \oplus \text{Cin}$$

$$\text{carry} = XY + \text{Cin} (X \oplus Y)$$

$$XY + \text{Cin} (\bar{X}Y + X\bar{Y})$$

$$XY + \text{Cin} \bar{X}Y + \text{Cin} X\bar{Y}$$

Binary Subtractor \Rightarrow

- * A half subtractor does not have a borrow input.
- + A full subtractor has a borrow input
- + The truth table for half & full Subtractor were the Y-bit is subtracted from X-bit. are given in table below.

Inputs Output

X	Y	Bin	Diff	Bout
---	---	-----	------	------

Half Subtractor

0	0		0	0
0	1		1	0
1	0		1	0
1	1		0	1

Full Subtractor

X	Y	Cin	Diff	Bout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1

1	0	0	.	1	0	0	0
1	0	0	.	0	0	0	0
1	1	0	.	0	0	0	0
1	1	1	.	1	1	1	1

+ The output eqn for half subtractor are

$$Diff = f(x, y) = \Xi(1, 2) = \bar{x}y + x\bar{y}$$

$$B_{out} = f(x, y) = \Xi(1) = \bar{x}y$$

+ The output eqn for full subtractor are

$$B_{in} = \Xi(1, 2, 4, 7) =$$


$x^4 B_{in}$	00	01	11	10
0	1	0	1	0
1	0	1	0	1

$$Diff = x\bar{y} B_{in} + \bar{x}\bar{y} B_{in} + x\bar{y} B_{in} + \bar{x}y B_{in}$$


$$Diff = x \oplus y \oplus B_{in}$$

$$B_{out} = \bar{x}y + \bar{x}B_{in} + yB_{in}$$


④ ~~Half~~ ~~Subtractor~~ \Rightarrow

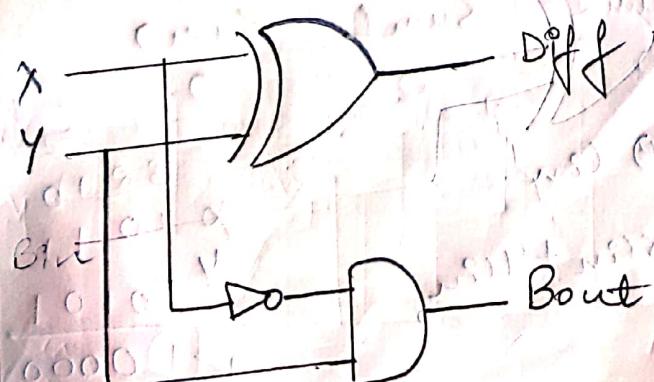

Full Subtractor \Rightarrow

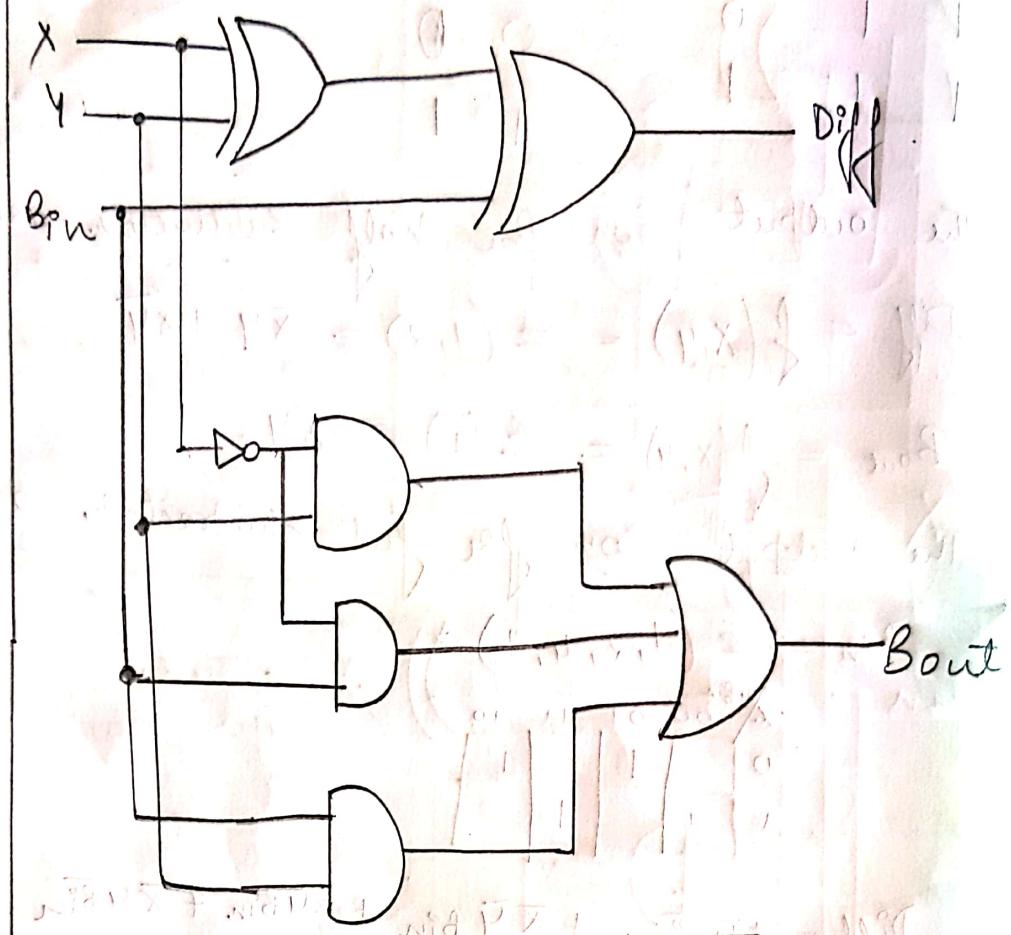

Cascading Full Adders \Rightarrow

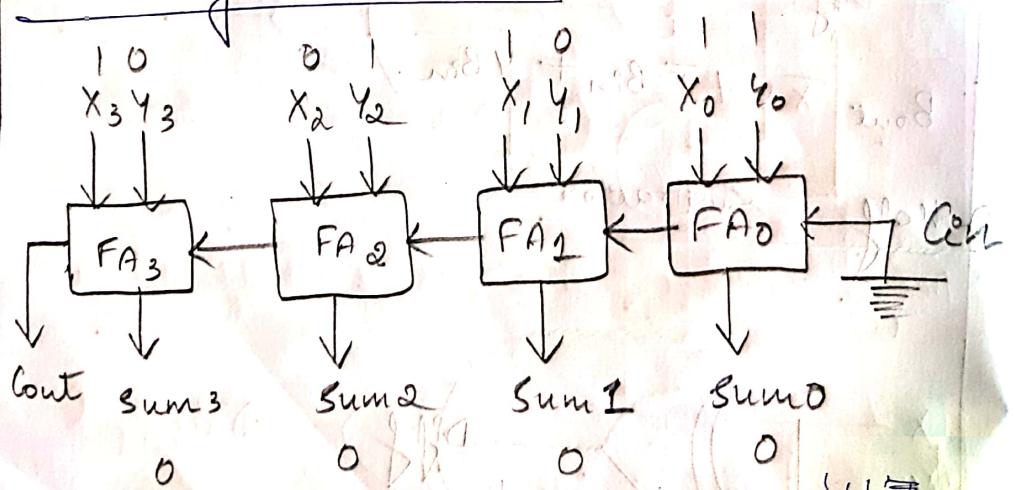

$$\text{Sum} = x \oplus y \oplus \text{Cin}$$

$$\text{Cout} = x_4 + x_3 \text{Cin} + y_4 \text{Cin}$$

$$\begin{array}{r} 1010 \\ 0101 \\ \hline 10000 \end{array}$$

Cout Sum₃:Sum