

Module -

Two port network.

<u>Parameter</u>	<u>Dependent variable</u>	<u>Independent variable</u>	<u>Equations</u>
Z-parameter	V_1, V_2	I_1, I_2	$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$
Y parameter	I_1, I_2	V_1, V_2	$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$
h parameter	V_1, I_2	I_1, V_2	$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$
T parameter	V_1, I_1	V_2, I_2	$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$

① Impedance parameter or Z or open circuit ^{impedance} parameter

$$V_1 = f(I_1, I_2) = Z_{11} I_1 + Z_{12} I_2 \quad - \textcircled{1}$$

$$V_2 = f(I_1, I_2) = Z_{21} I_1 + Z_{22} I_2 \quad - \textcircled{2}$$

In matrix form

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$[V] = [Z] [I]$$

The independent Z-parameter are defined as follows.

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

driving imped.

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

reverse transfer imped.



$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

forward transfer imped.


$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

output imped.

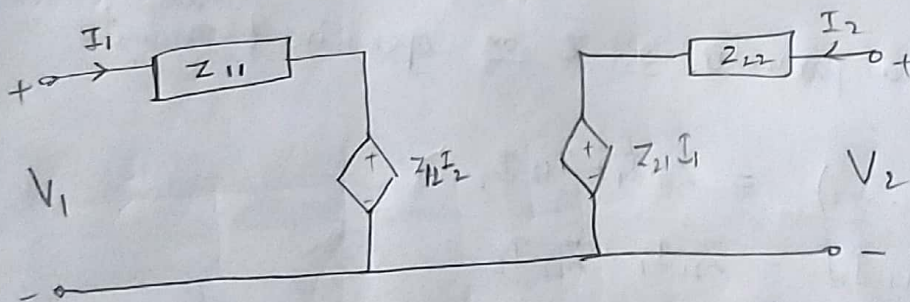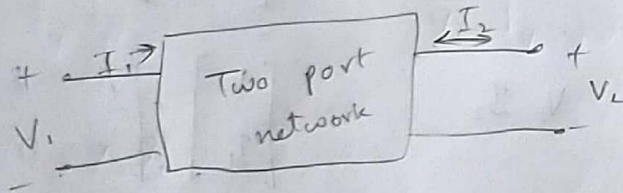

Equivalent network of a 2 port network in terms of Z parameters.

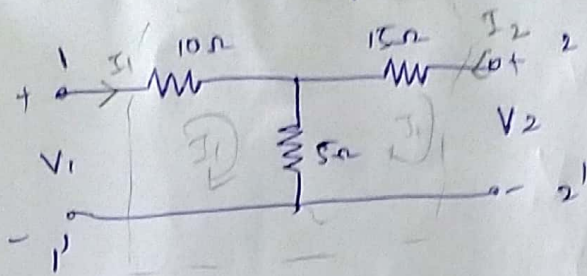① Find Z parameters for network shown in figure.




$$\rightarrow V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

Let $I_2 = 0$ i.e. port 2 is open circuit.

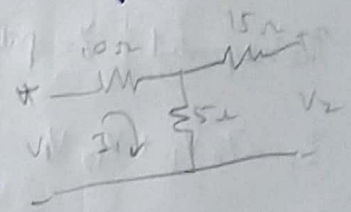As port 2 is open current flowing through 5Ω is only I_1 .




$$-10I_1 - 5I_1 + V_1 = 0 \Rightarrow \frac{V_1}{I_1} = \underline{\underline{15\Omega = Z_{11}}}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = \frac{5I_1}{I_1} = \underline{\underline{5\Omega}}$$

Let $I_1 = 0$ i.e. port 1 is open circuit

Current through 5Ω is only I_2 .

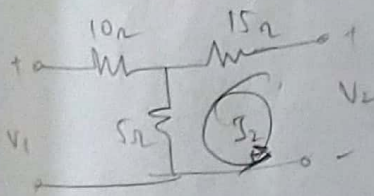

$$V_2 - 5I_2 - 15I_2 = 0$$

$$V_2 - 20I_2 = 0$$

$$Z_{22} = \frac{V_2}{I_2} = \underline{\underline{20\Omega}}$$

$$Z = \begin{bmatrix} 15 & 5 \\ 5 & 20 \end{bmatrix} \Omega$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = \frac{5I_2}{I_2} = \underline{\underline{5\Omega}}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 15 & 5 \\ 5 & 20 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

② Y-parameter or Admittance parameter or

$$I_1 = f(V_1, V_2) = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = f(V_1, V_2) = Y_{21} V_1 + Y_{22} V_2$$

In matrix form

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$[I] = [Y][V]$$

The independent Y-parameters are defined as follows

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$


$$Y_{11} = \frac{I_1}{V_1} \bigg|_{V_2=0}$$

$$Y_{12} = \frac{I_1}{V_2} \bigg|_{V_1=0}$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$


$$Y_{21} = \frac{I_2}{V_1} \bigg|_{V_2=0}$$

$$Y_{22} = \frac{I_2}{V_2} \bigg|_{V_1=0}$$

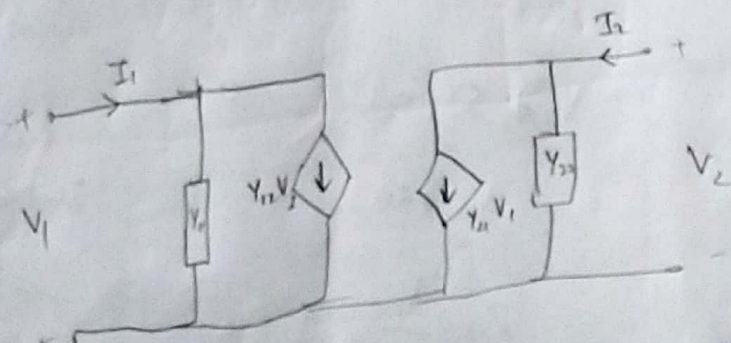

Equivalent n/w of a 2port n/w of Y parameter

Find Y parameters for circuit shown.

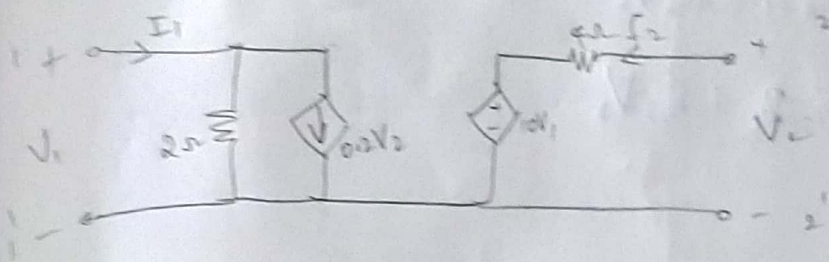


$$[Y] = \begin{bmatrix} 0.5 & 0.2 \\ -2.5 & 0.25 \end{bmatrix} \text{ S}$$

$$\rightarrow I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

Let $V_2 = 0$

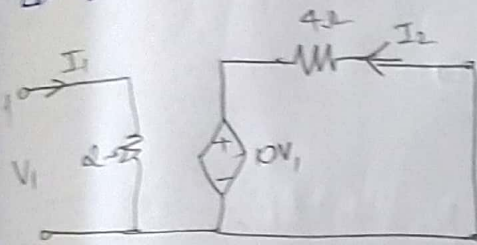

$$V_1 = 2I_1$$

$$Y_{11} = \frac{I_1}{V_1} \bigg|_{V_2=0} = \frac{I_1}{2I_1} = \underline{\underline{0.5 \text{ S}}}$$


KVL at output side

$$4I_2 + 10V_1 = 0$$


$$-10V_1 = 4I_2$$

$$Y_{21} = \frac{I_2}{V_1} \bigg|_{V_2=0} = \frac{-10V_1}{4V_1} = \underline{\underline{-2.5 \text{ S}}}$$

Let $V_1 = 0$

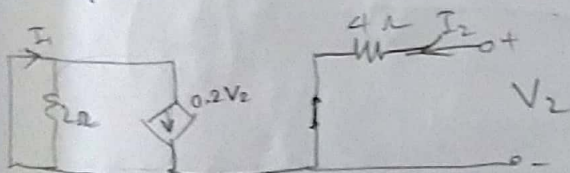

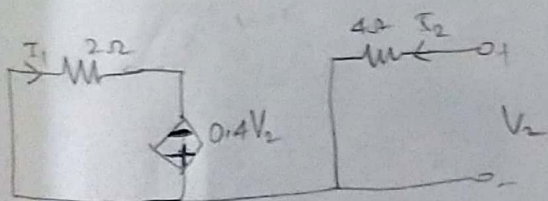convert current source into voltage source



$$V_2 = 4I_2$$

$$Y_{22} = \frac{I_2}{V_2} \bigg|_{V_1=0} = \frac{I_2}{4I_2} = \underline{\underline{0.25 \text{ S}}}$$

$$\text{KVL at input } 2I_1 - 0.4V_2 = 0 \Rightarrow 2I_1 = 0.4V_2$$

$$Y_{12} = \frac{I_1}{V_2} \bigg|_{V_1=0}$$

$$= \frac{0.2V_2}{V_2}$$

$$\underline{\underline{Y_{12} = 0.2 \text{ S}}}$$

(3) h parameter or hybrid parameter

$$V_1 = f(I_1, V_2) = h_{11}I_1 + h_{12}V_2$$

$$I_2 = f(I_1, V_2) = h_{21}I_1 + h_{22}V_2$$

In matrix form

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$


Individual h parameters are defined as follows.

$$h_{11} = \frac{V_1}{I_1} \bigg|_{V_2=0}$$


$$h_{12} = \frac{V_1}{V_2} \bigg|_{I_1=0}$$

$$h_{21} = \frac{I_2}{I_1} \bigg|_{V_2=0}$$

$$h_{22} = \frac{I_2}{V_2} \bigg|_{I_1=0}$$

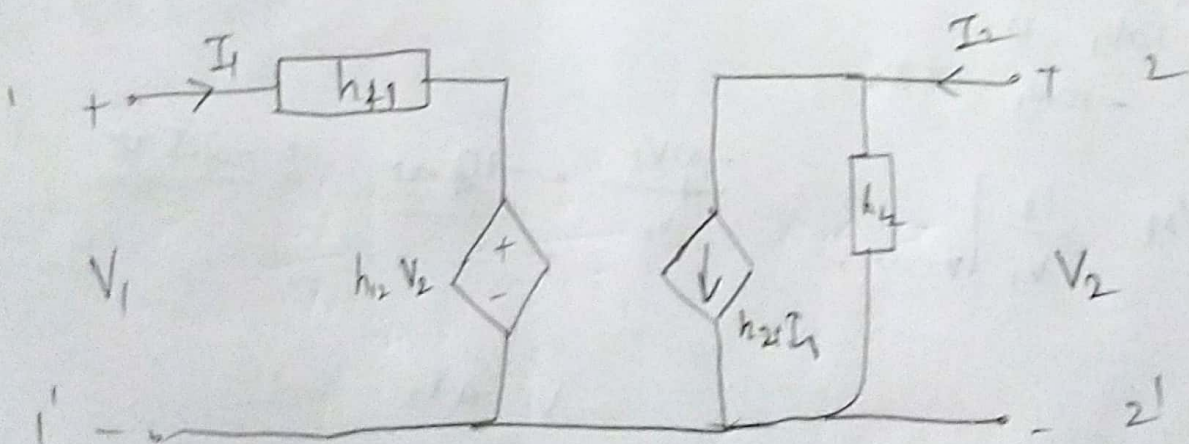

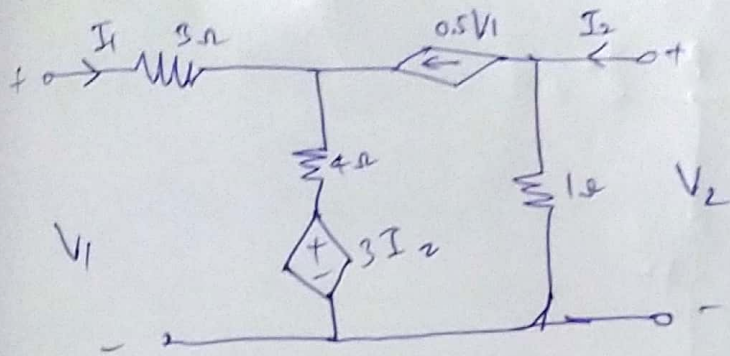
Find h parameters for 2 port network shown.



$$\rightarrow V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

Let $V_2 = 0$

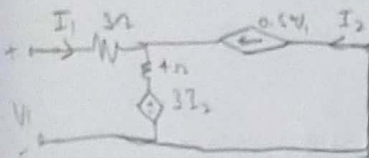

KVL at a/p

$$-V_1 + 3I_1 + 4(I_1 + I_2) + 3I_2 = 0$$

$$V_1 = 7I_1 + 7I_2$$

$$I_2 = 0.5 V_1$$

$$V_1 - 7(0.5)V_1 = 7I_1$$

$$-\frac{5}{2} V_1 = 7I_1$$

$$-\frac{5}{14} V_1 = I_1$$


$$h_{11} = \frac{V_1}{I_1} \bigg|_{V_2=0} = \frac{V_1}{-\frac{5}{14} V_1} = \underline{\underline{-2.8 \Omega}}$$

KVL at i/p $V_1 = -2.8 I_1$

$$I_2 = 0.5 (-2.8) I_1 = -1.4 I_1$$

$$h_{21} = \frac{I_2}{I_1} \bigg|_{V_2=0} = \frac{-1.4 I_1}{I_1} = \underline{\underline{-1.4}}$$

Let $I_1 = 0$

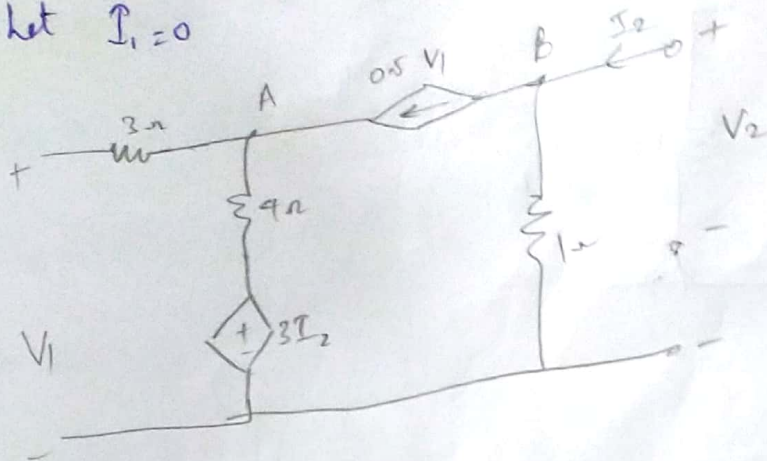

KCL at B

$$0.5V_1 + \frac{V_B}{1} - I_2 = 0$$

$$I_2 = V_B + 0.5V_1 \quad \text{--- (1)}$$

also

$$V_1 = 4(0.5V_1) + 3I_2$$

$$V_1 = 2V_1 + 3I_2$$

$$V_1 = -3I_2 \quad \text{--- (2)}$$

$$I_2 = V_B + (0.5)(-3I_2) \Rightarrow I_2 + 1.5I_2 = V_B$$

$$V_2 = V_B = 2.5I_2$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \frac{I_2}{2.5I_2} = \underline{0.4 \text{ S}}$$

$$\textcircled{1} \quad V_1 = -3 \left(\frac{V_2}{2.5} \right) = \underline{\underline{\frac{-3V_2}{2.5}}}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

$$= \frac{-3/2.5 V_2}{V_2}$$

$$\underline{h_{12} = -1.2}$$

$$[h] = \begin{bmatrix} -2.8 & -1.2 \\ -1.4 & 0.4 \end{bmatrix}$$

$$V_1 = f(V_2, I_2) = AV_2 + B(-I_2)$$

$$I_1 = f(V_2, -I_2) = CV_2 + D(-I_2)$$

Matrix

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$




$$A = \left. \frac{V_1}{V_2} \right|_{-I_2=0}$$

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0}$$


$$C = \left. \frac{I_1}{V_2} \right|_{-I_2=0}$$

$$D = \left. \frac{I_1}{-I_2} \right|_{V_2=0}$$

Find T parameters

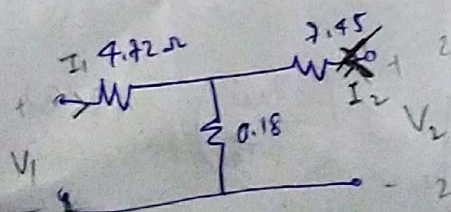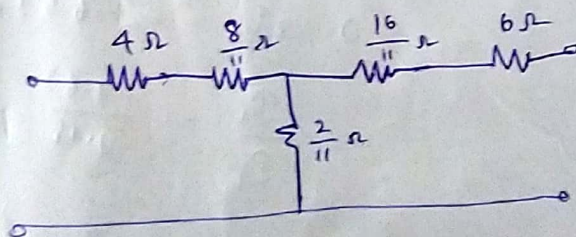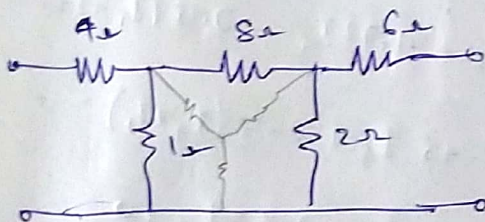

Let $I_2 = 0$

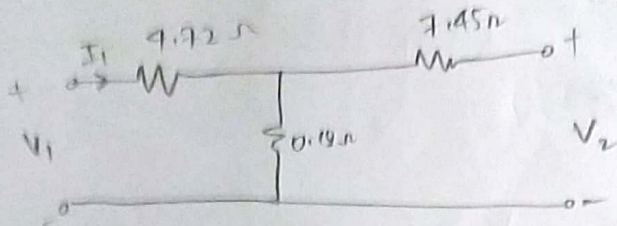

$$V_2 = 0.18 I_1$$


$$C = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{I_1}{0.18 I_1} = \underline{\underline{5.55 \text{ V}}}$$

KVL $-V_1 + 4.72 I_1 + 0.18 I_1 = 0$

$$-V_1 + 4.9 I_1 = 0 \Rightarrow V_1 = 4.9 I_1$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{4.9 I_1}{0.18 I_1} = \underline{\underline{27.22}}$$

Let $V_2 = 0$

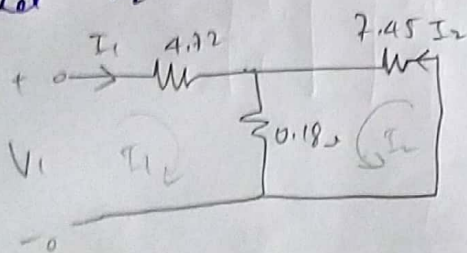

$$-V_1 + 4.72 I_1 + 0.18 (I_1 + I_2) = 0$$

$$7.45 I_2 + 0.18 (I_2 + I_1) = 0$$

$$0.18 I_1 + 7.63 I_2 = 0$$

$$0.18 I_1 = -7.63 I_2$$

$$\frac{I_1}{I_2} = \frac{-7.63}{0.18}$$

$$D = \left. \frac{I_1}{-I_2} \right|_{V_2=0} = \frac{7.63}{0.18} = 42.38$$

$$D = \left. \frac{I_1}{-I_2} \right|_{V_2=0} = -\left(\frac{-7.63}{0.18} \right) = \underline{\underline{42.38}}$$

$$V_1 = 4.9 I_1 + 0.18 I_2$$

$$V_1 = 4.9 \left(-\frac{7.63}{0.118} I_2 \right) + 0.18 I_2$$

$$V_1 = -207.52 I_2$$

$$B = \frac{V_1}{-I_2} \bigg|_{V_2=0} = \frac{-207.52 I_2}{-I_2} = \underline{\underline{207.52 \, \Omega}}$$

$$\Rightarrow [T] = \begin{bmatrix} 27.22 & 207.52 \\ 5.55 & 42.38 \end{bmatrix}$$

Parameters	Condition for	
	Reciprocity	Symmetry
Z	$Z_{12} = Z_{21}$	$Z_{11} = Z_{22}$
Y	$Y_{12} = Y_{21}$	$Y_{11} = Y_{22}$
h	$h_{12} = -h_{21}$	$h_{11}h_{22} - h_{12}h_{21} = 1$
T	$AD - BC = 1$	$A = D$

Relation between 2 port parameters.

① Relation between Z and Y parameters

$$[V] = [Z][I]$$

then $[I] = [Z]^{-1}[V]$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}^{-1} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$Z^{-1} = \frac{1}{\Delta Z} \begin{bmatrix} Z_{22} & -Z_{12} \\ -Z_{21} & Z_{11} \end{bmatrix} \quad \text{where } \Delta Z = Z_{11}Z_{22} - Z_{12}Z_{21}$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} \frac{Z_{22}}{\Delta Z} & \frac{-Z_{12}}{\Delta Z} \\ \frac{-Z_{21}}{\Delta Z} & \frac{Z_{11}}{\Delta Z} \end{bmatrix} \quad \text{If } \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \frac{1}{\Delta Y} \begin{bmatrix} Y_{22} & -Y_{12} \\ -Y_{21} & Y_{11} \end{bmatrix}$$

② Relation between Y and h parameter

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

Comparing

$$Y_{11} V_1 = I_1 - Y_{12} V_2$$

$$Y_{21} V_1 = I_2 - Y_{22} V_2$$

$$\begin{bmatrix} Y_{11} & 0 \\ Y_{21} & -1 \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 1 & -Y_{12} \\ 0 & -Y_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$\therefore \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & 0 \\ Y_{21} & -1 \end{bmatrix}^{-1} \begin{bmatrix} 1 & -Y_{12} \\ 0 & -Y_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$= \frac{-1}{Y_{11}} \begin{bmatrix} -1 & 0 \\ -Y_{21} & Y_{11} \end{bmatrix} \begin{bmatrix} 1 & -Y_{12} \\ 0 & -Y_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$= \frac{-1}{Y_{11}} \begin{bmatrix} -1 & Y_{12} \\ -Y_{21} & Y_{12}Y_{21} - Y_{11}Y_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} \frac{1}{Y_{11}} & \frac{-Y_{12}}{Y_{11}} \\ \frac{-Y_{21}}{Y_{11}} & \frac{\Delta Y}{Y_{11}} \end{bmatrix} \quad \text{where } \Delta Y = Y_{11}Y_{22} - Y_{12}Y_{21}$$

③ Relation between T & h parameters

$$\left. \begin{aligned} V_1 &= AV_2 - BI_2 \\ I_1 &= CV_2 - DI_2 \end{aligned} \right\} \textcircled{1}$$

$$\left. \begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \\ I_2 &= h_{21} I_1 + h_{22} V_2 \end{aligned} \right\} \textcircled{2}$$

rearrange ②

$$V_1 - h_{11} I_1 = h_{12} V_2$$

$$-h_{21} I_1 = h_{22} V_2 - I_2$$

matrix

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 1 & -h_{11} \\ 0 & -h_{21} \end{bmatrix}^{-1} \begin{bmatrix} h_{12} & 0 \\ h_{22} & -1 \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}$$



$$[T] = \frac{1}{-h_{21}} \begin{bmatrix} -h_{21} & h_{11} \\ 0 & 1 \end{bmatrix} \begin{bmatrix} h_{12} & 0 \\ h_{22} & -1 \end{bmatrix}$$

take note
might be
wrong

$$= \begin{bmatrix} 1 & -\frac{h_{11}}{h_{21}} \\ 0 & \frac{1}{-h_{21}} \end{bmatrix} \begin{bmatrix} h_{12} & 0 \\ h_{22} & -1 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} h_{12} - \frac{h_{11} h_{22}}{h_{21}} & \frac{h_{11}}{h_{21}} \\ -\frac{h_{22}}{h_{21}} & \frac{1}{h_{21}} \end{bmatrix}$$

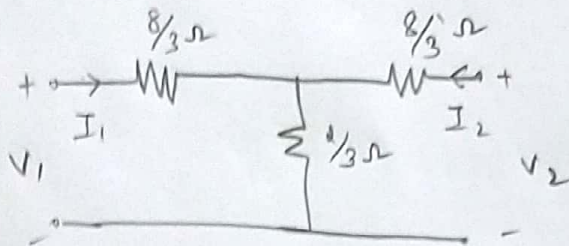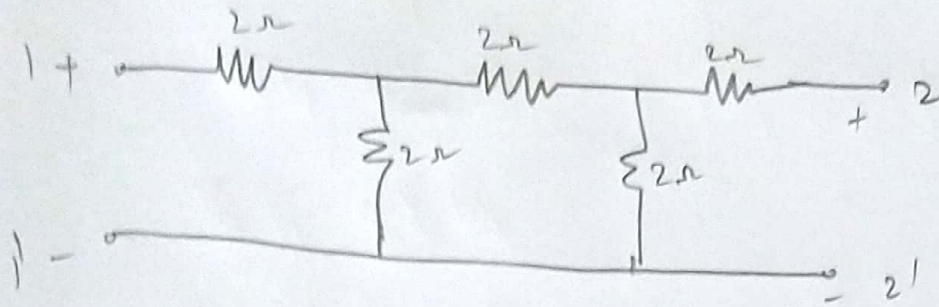
Find Z and Y parameters of the network shown in figure.



$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

Let $I_1 = 0$

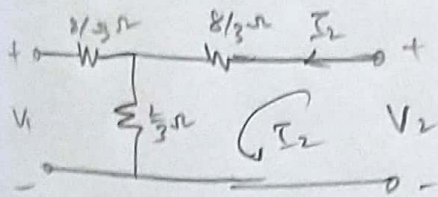

$$V_1 = \frac{2}{3} I_2$$

$$\Rightarrow \boxed{Z_{12} = \frac{2}{3} \Omega}$$