

29/07/16

classmate

Date _____

Page _____



Network Analysis (Electrical Circuit Analysis)

Chapter - 1



Basics About Network Analysis

The various electrical elements are passive elements and active elements.

Passive elements are:

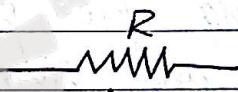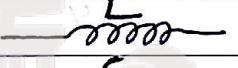- i) Resistor 
- ii) Inductor 
- iii) Capacitor 


Active elements are:

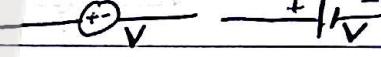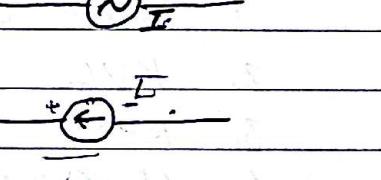- i) Voltage source
 - a) AC Voltage source 
 - b) DC Voltage source 
- ii) Current source
 - a) AC Current source 
 - b) DC Current source 

(Always current flows from positive polarity to negative polarity).

Electrical Circuit (or) Network:

A interconnection of various electrical elements (both passive and active) in the form of a closed path so that current flows through that is called electrical circuit.

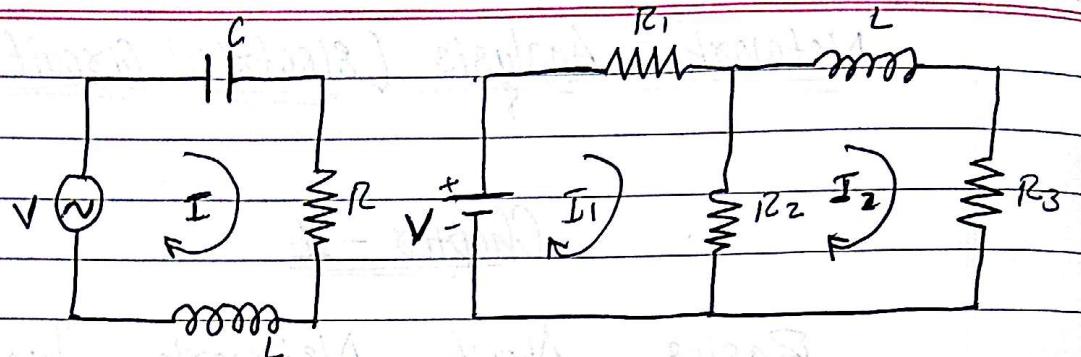Ex:

Network Analysis means studying about the given electrical network, understanding about its operation, rectifying the problems present in that (during failure) and giving a solution for the system.

NA gives various techniques or methods to solve the given electrical network, in the form of finding voltage across the new element or current flowing through the new via various elements.

The various ~~new~~ NA techniques available are:

1. Ohm's Law
 2. KVL
 3. KCL
 4. Star \leftrightarrow Delta Connection / Technique.
 5. Source Shifting
 6. Loop Analysis.
 7. Node Analysis
- etc;


$$P = VI$$

$$P = \frac{V^2}{R}$$

$$I^2 = \frac{V^2}{R}$$

Passive Elements:

1. Resistor (R):

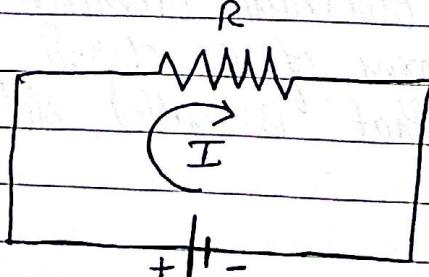


According to Ohm's Law,

$$V = I R$$

$$I = \frac{V}{R}$$

In Resistor, V and I are in same phase.

2. Inductor:

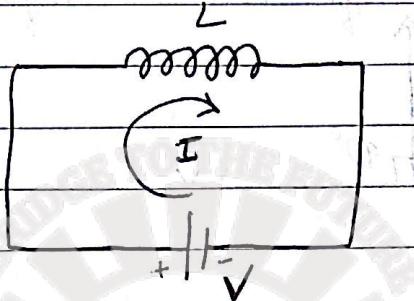

Voltage across the inductor, $V = I X_L$

where, X_L = inductive reactance


$$X_L = 2\pi f L$$

Also, Voltage across inductor,


$$V = L \frac{dI}{dt}$$

$$I = \frac{1}{L} \int V dt$$

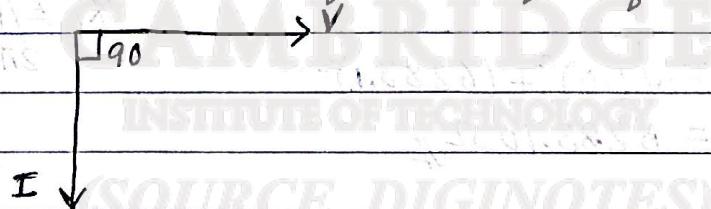In Inductor, Current lags Voltage by 90° .



3) Capacitor:

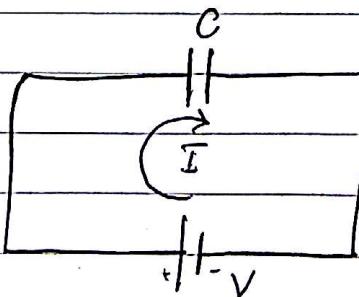

Voltage across the Capacitor, $V = I X_C$


where, X_C = capacitive reactance

$$X_C = \frac{1}{2\pi f C}$$

$$\text{Also, } \text{voltage } I = C \frac{dV}{dt}$$

$$V = \frac{1}{C} \int I \cdot dt$$

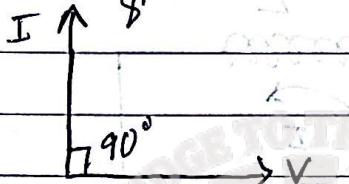In capacitor ~~voltage~~ leads voltage by 90° .



Impedance:

It is the total opposition made by the circuit if circuit consisting of R, L, C

$$\text{Impedance } (Z) = R + jX_L - jX_C$$

$$Z = R + jX_L - jX_C \quad X_L = 6283.185 \Omega$$


$$Z = 10 + j(X_L - X_C) \quad X_C = 1.591 \times 10^4 \Omega$$

$$Z = 10 + j(6283.18)$$

$$Z =$$

$$\text{Now, } |Z| = \sqrt{(10)^2 + (6283.1)^2}$$

$$= 6283.10 \Omega$$

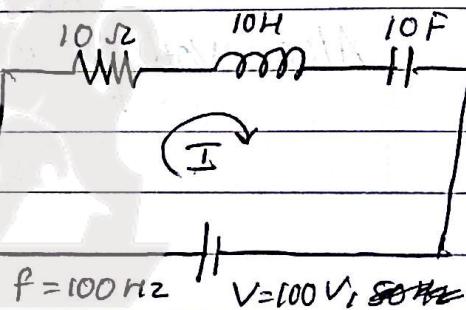

$$X_L = 2\pi f L = 1000 \pi \Omega$$

$$X_C = \frac{1}{2\pi f C} = 3.1830 \times 10^4 \Omega$$

$$I = \frac{V}{|Z|} = \frac{100}{6283.10}$$

$$I = 0.015 \text{ AMP}$$

Admittance (Y):

It is the reciprocal of impedance,



$$\text{i.e., } Y = \frac{1}{Z}$$

Kirchhoff's Voltage Law:

$$V = IR_1 + IR_2 + IR_3 + IR_4 \quad i)$$

$$V = I [R_1 + R_2 + R_3 + R_4]$$

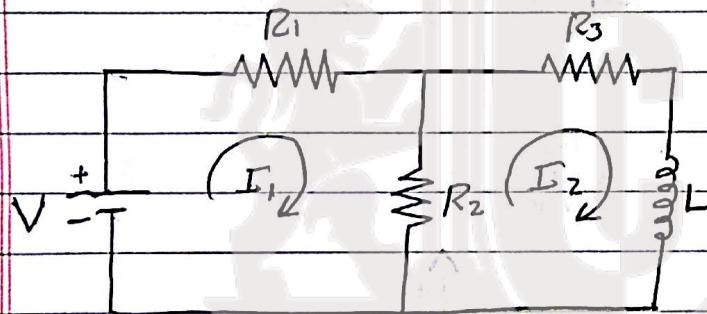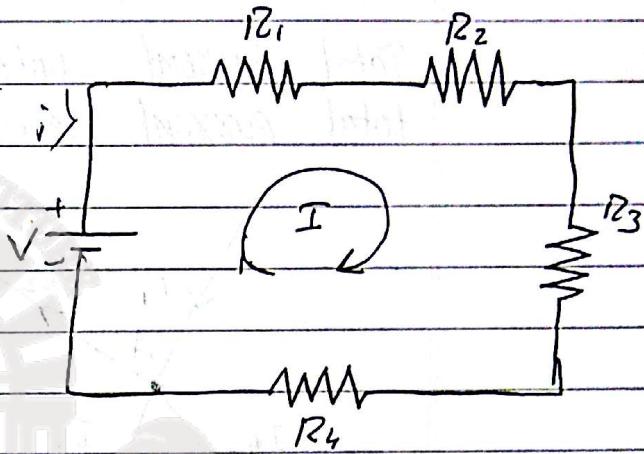Total voltage = sum of the voltage drops produced.



KVL for loop - I is,

$$V = I_1 R_1 + I_1 R_2 - I_2 R_2$$

$$V = I_1 R_1 + R_2 (I_1 - I_2) \cancel{,}$$

KVL for loop - II is,

$$0 = I_2 R_3 + I_2 jX_L + I_2 R_2 - I_1 R_2$$

$$0 = I_2 R_3 + I_2 jX_L + R_2 (I_2 - I_1) \cancel{,}$$

Note:


Series \rightarrow Voltage
 Current \Rightarrow θ , ϕ , ψ
 Parallel \rightarrow Current

Kirchhoff's Current Law:

Algebraic summation of all the currents at a node or junction is zero.

(or)

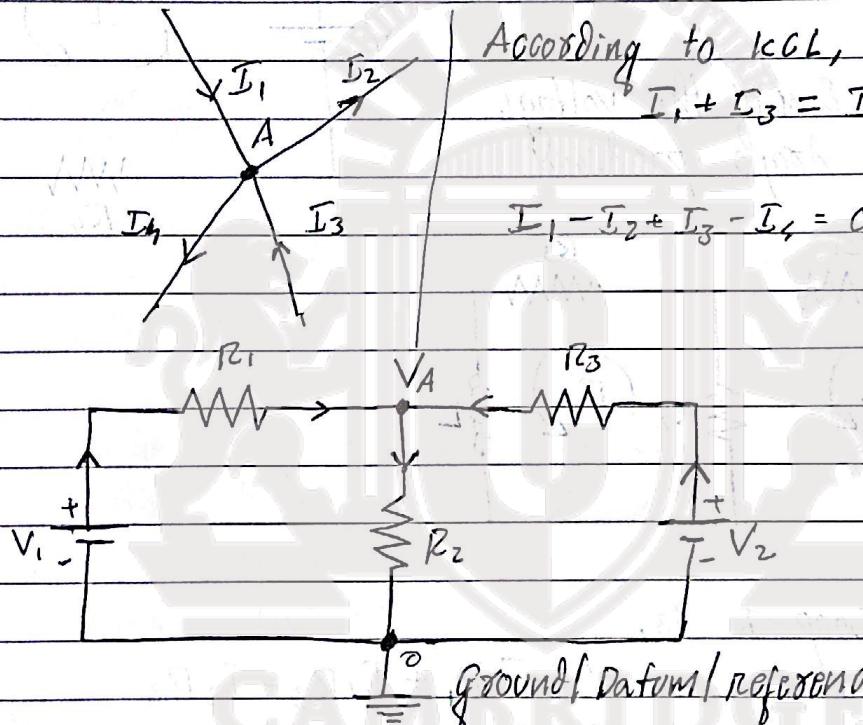Total current entering into a node is equal to total current leaving away from the node.



V_A - Node Voltage

According to KCL:


At Node V_A :

$$\frac{V_1 - V_A}{R_1} + \frac{V_2 - V_A}{R_3} = \frac{V_A - 0}{R_2} \cancel{\neq}$$


$$\frac{V_1}{R_1} + \frac{V_2}{R_3} - \frac{V_A}{R_1} \left(\frac{1}{R_1} + \frac{1}{R_3} \right) - \frac{V_A}{R_2} = 0 \cancel{\neq}$$

Voltage Sources

a. Ideal Voltage source

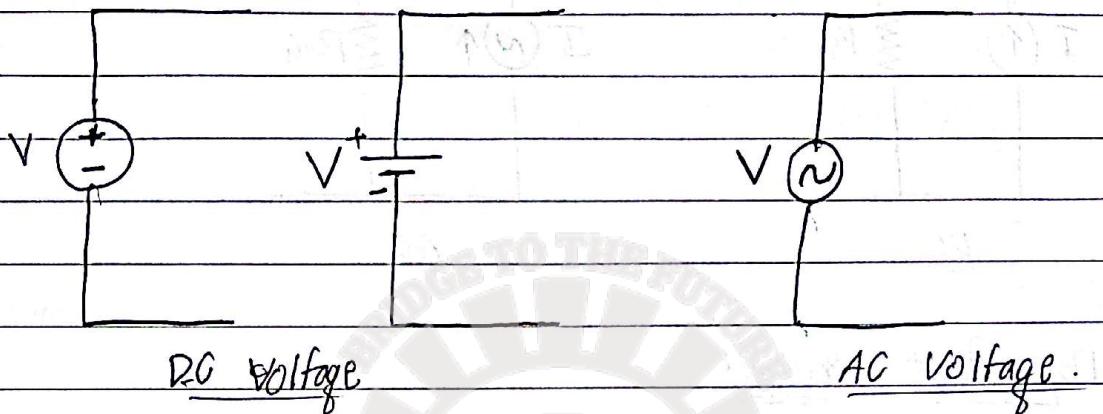


b. Practical Voltage source

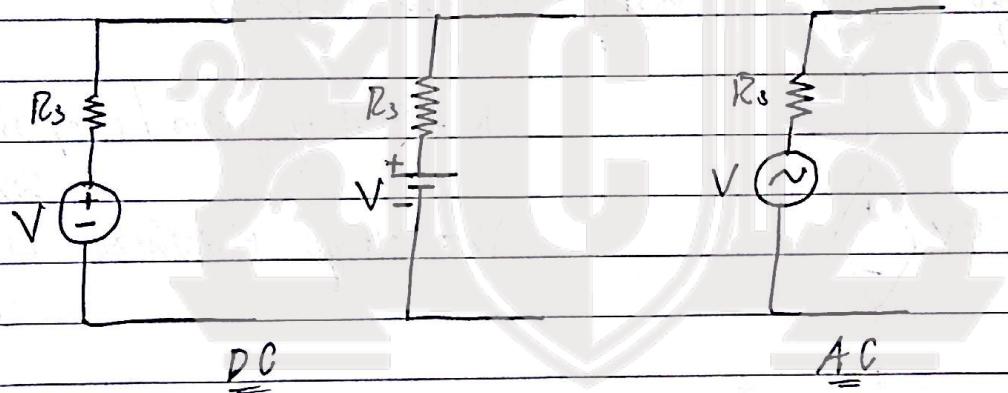


Current Sources

a. Ideal Current source

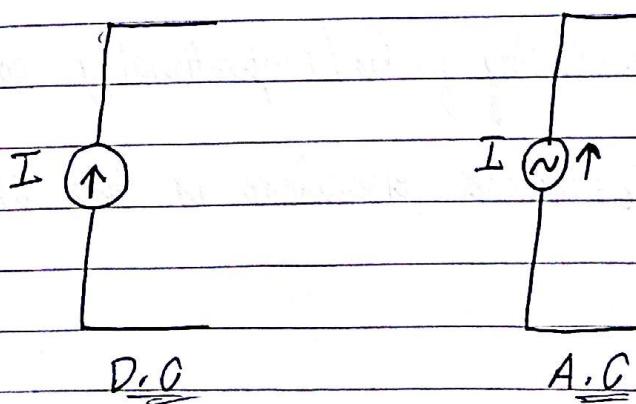


6. Practical Current sources

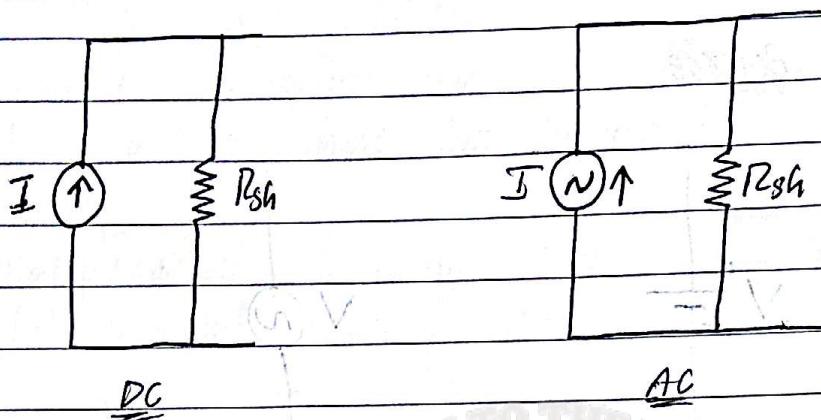

Dependent sources

There are 6 types of dependent sources:

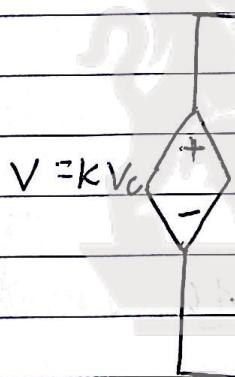
- i. \rightarrow Voltage Dependent Voltage Source (VDVS):



k = scaling factor / Proportionality constant.

V_c = voltage elsewhere in the circuit.

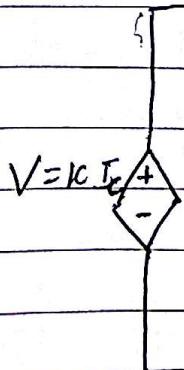
- ii. Current Dependent Voltage Source (CDVS):



k = scaling factor / Proportionality constant

I_c = current elsewhere in the circuit.

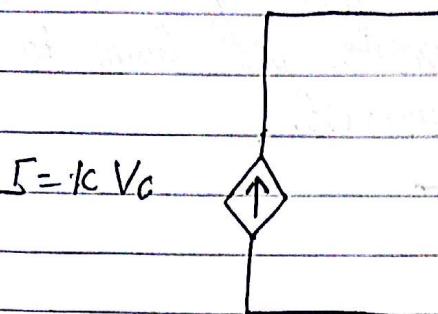
iii. Voltage Dependent Current Source (VDCS):



k_c = scaling factor / proportionality const.

V_o = Voltage elsewhere in the ckt.


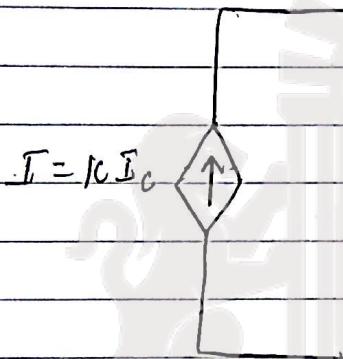
iv. Current Dependent Current Source (CDCS):



k_c = scaling factor / proportionality const.

I_o = current elsewhere in the ckt.

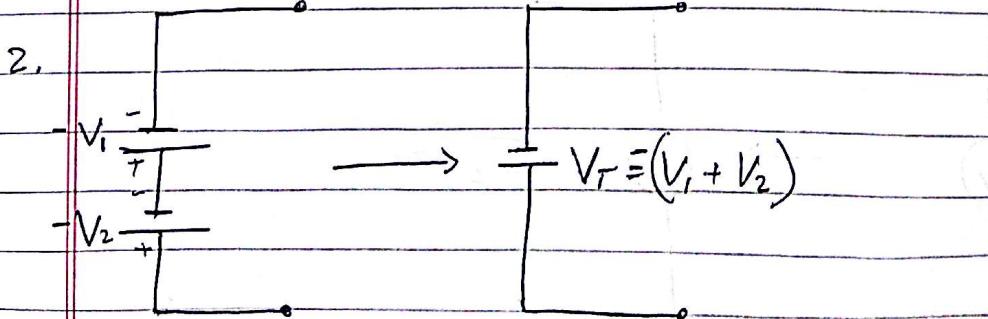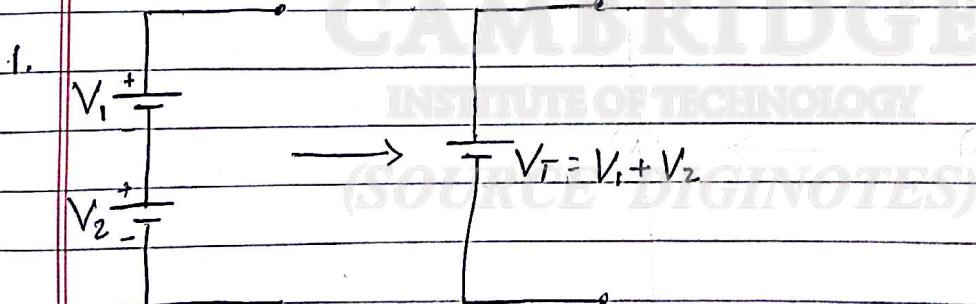
Addition & subtraction of Voltage sources:
(Combination of Voltage sources)




Note:

If the middle polarities of the two voltage sources are opposite, we have to add otherwise we have to subtract.

3.

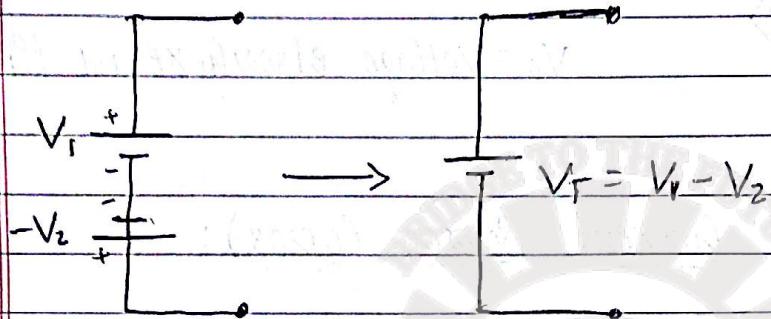


4.

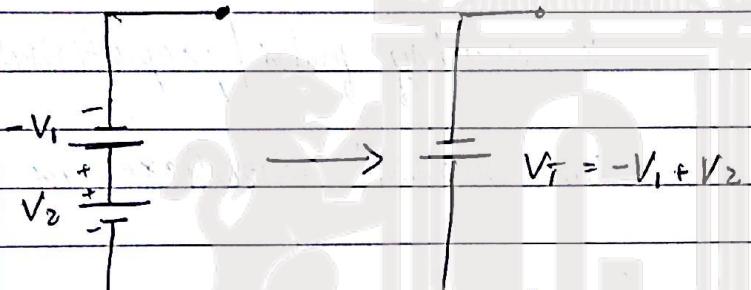
 $(V_1 > V_2)$

Addition & Subtraction of Current Sources:

1.

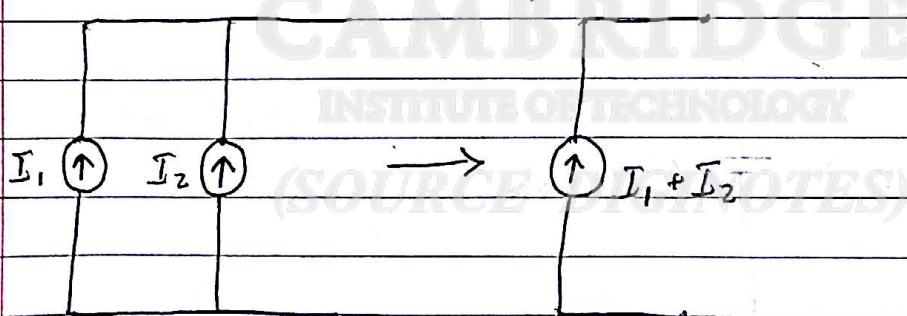


2.

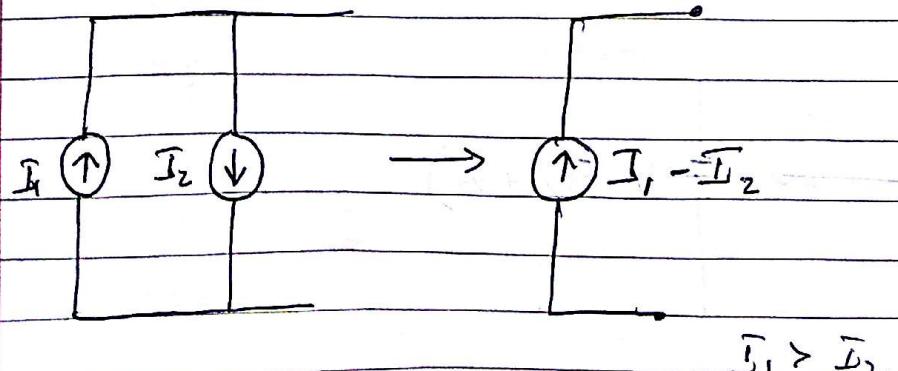


Note:

Current sources are added when they are in same direction otherwise subtracted.

3.

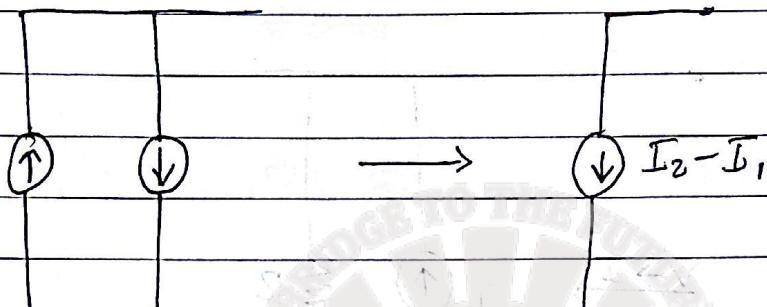


$$I_2 > I_1$$

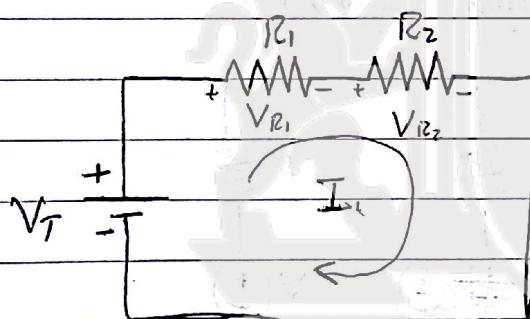Voltage Divider Rule:



$$V_{R1} = \frac{V_T \times R_1}{R_1 + R_2}$$

$$V_{R2} = \frac{V_T \times R_2}{R_1 + R_2}$$

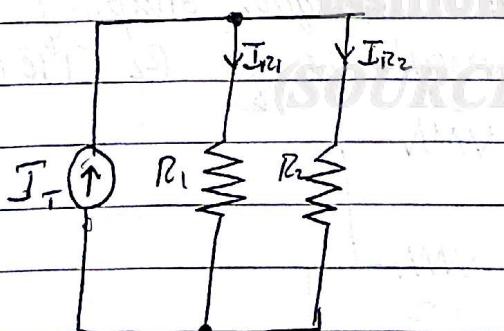
Current Divided Rule:

~~$$I_{R1} = \frac{I_T \times R_2}{R_1 + R_2}$$~~



~~$$I_{R2} = \frac{I_T \times R_1}{R_1 + R_2}$$~~

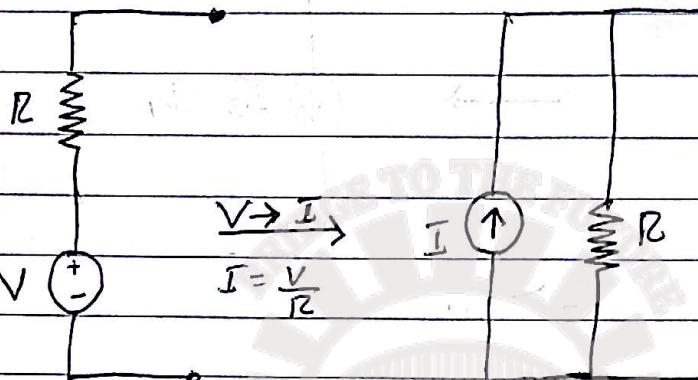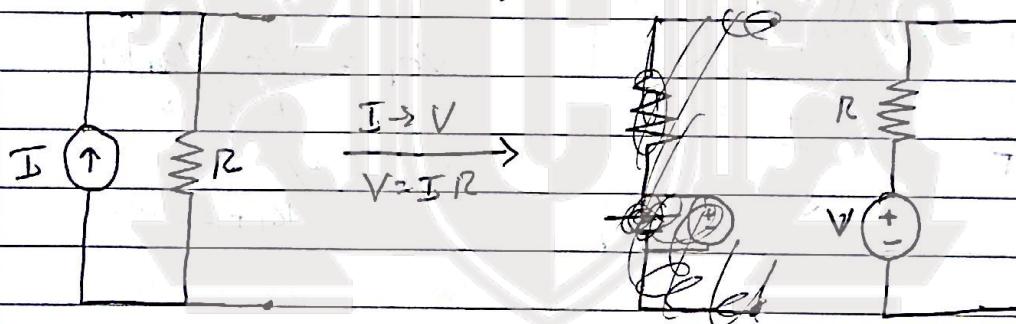Source Transformation:1. Voltage - Current Transformation ($V \rightarrow I$)2. Current - Voltage Transformation ($I \rightarrow V$)

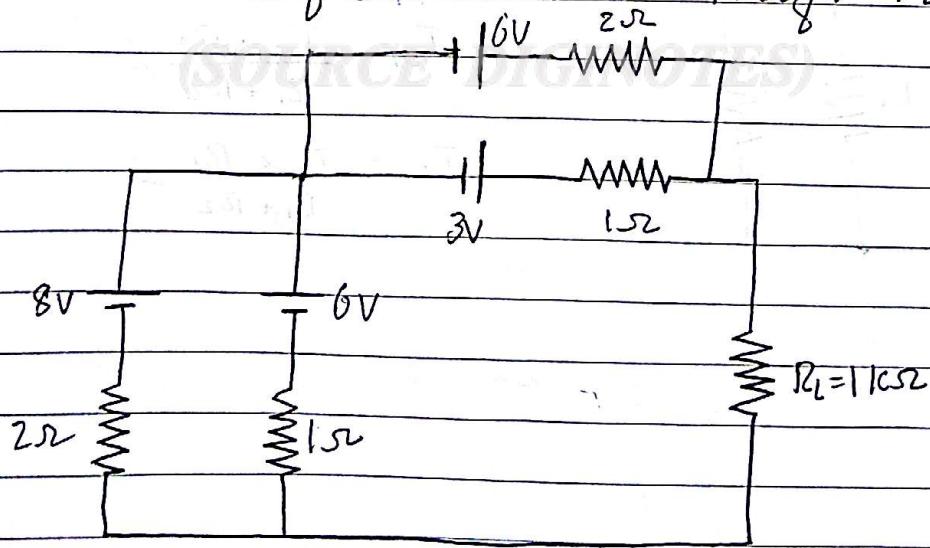
Q. Using current transformation technique, simplify the given N.W & find the current through $R_L = 1\text{ k}\Omega$.



Apply $V \rightarrow I$,

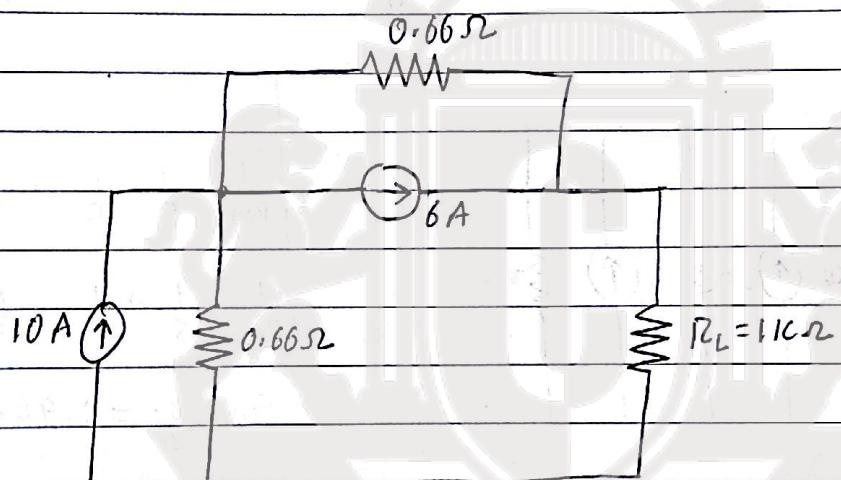
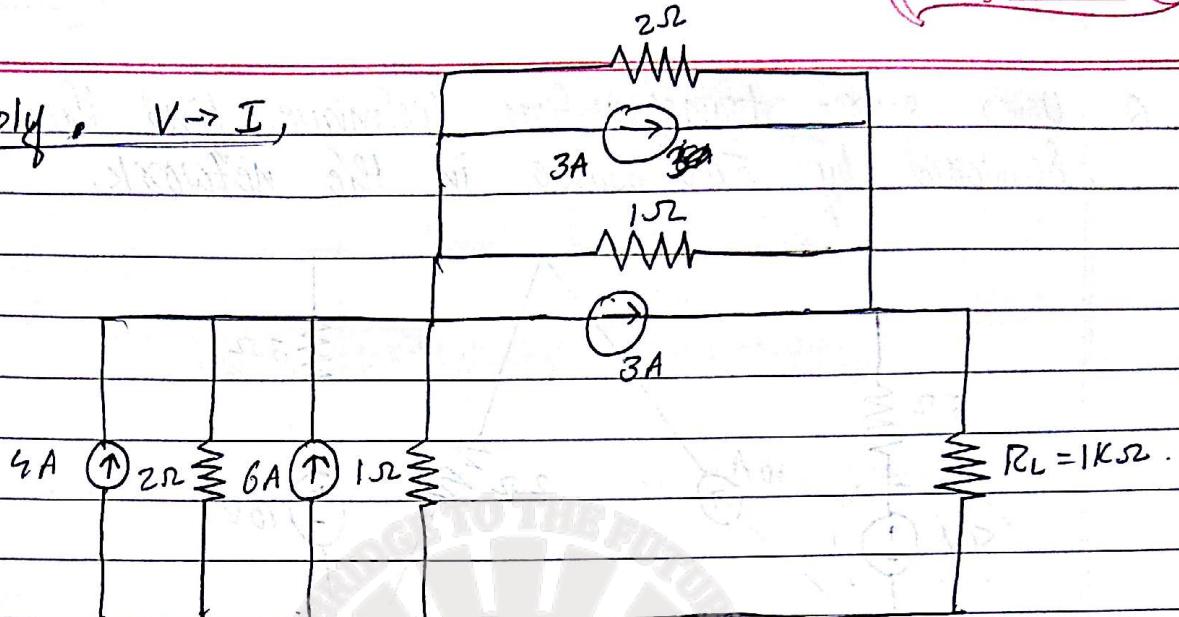


Apply $I \rightarrow V$,

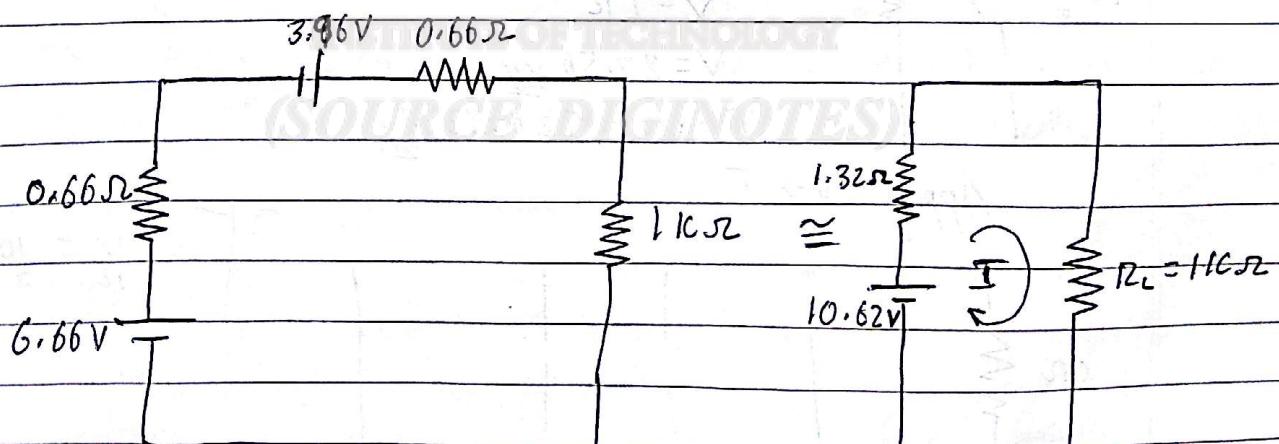

$$\therefore \text{Current through } R_L = I_{R_L} = \frac{10.62}{1000 + 1.32} = 0.0106 A \approx 10.6 \text{ mA}$$

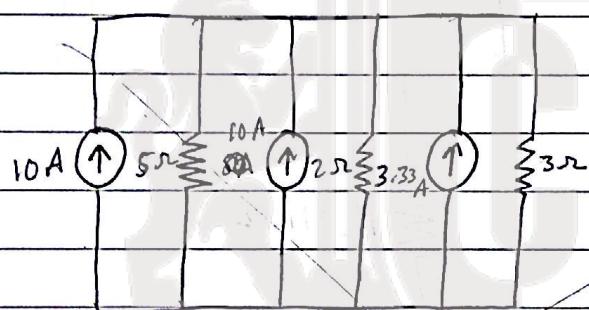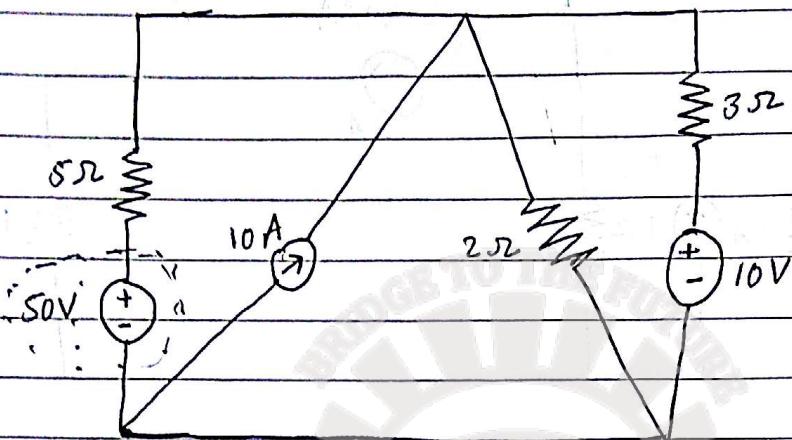
Q. Using source transformation technique, find the power delivered by 50V source in the network.



$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$


$$\frac{1}{R_{eq}} = \frac{1}{5} + \frac{1}{2} + \frac{1}{3} = \frac{31}{30}$$


$$R_{eq} = \frac{30}{31} = 0.967$$

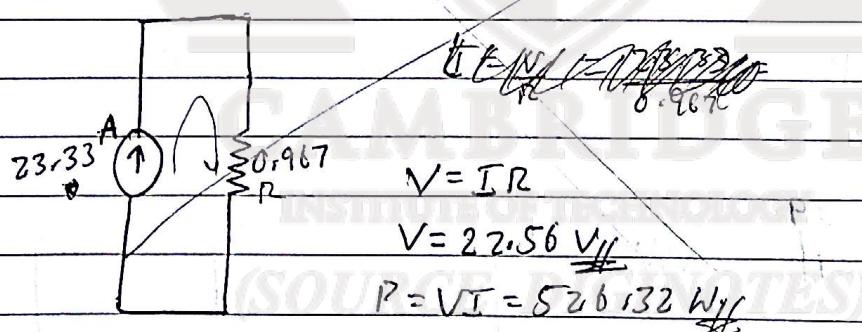

Apply $V \rightarrow I$
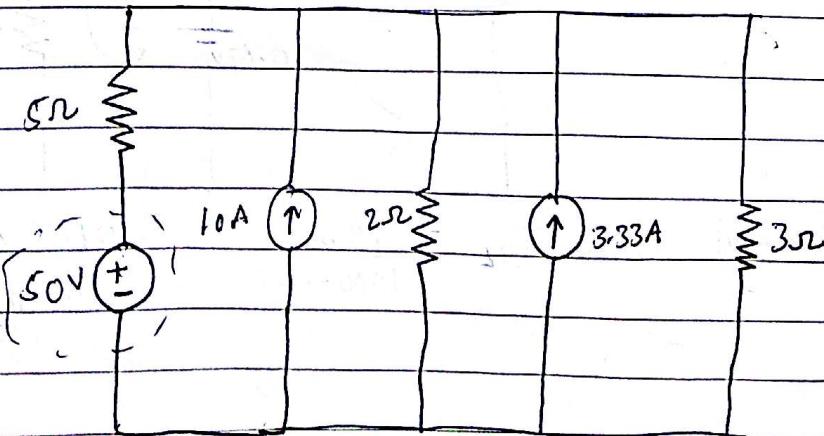
$$I = \frac{V}{R} = \frac{10}{3} = 3.33A$$



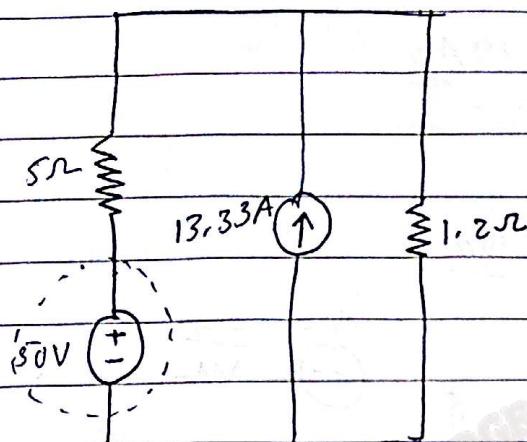


Apply $V = IR$

$$V = IR$$

$$V = 13.33 \times 1.2$$

$$V = 15.99 \text{ V} \cancel{A}$$

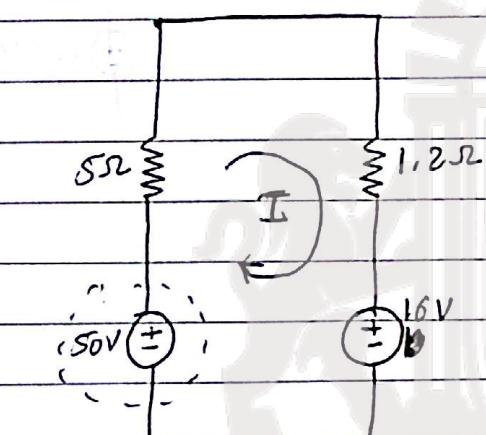

$$I = \frac{V}{R} = \frac{50 - 16}{6.2} = \frac{34}{6.2}$$


$$I = 5.48 \text{ A} \cancel{A}$$

∴ Power delivered by 50V source is,

$$P_{50V} = V \times I = 50 \times 5.48$$

$$P_{50V} = 274.2 \text{ W} \cancel{A}$$

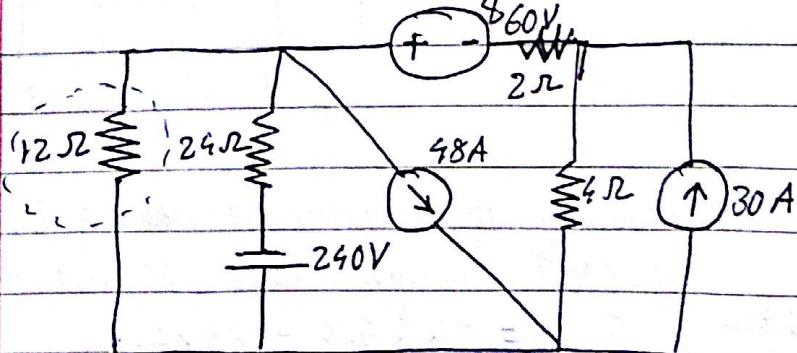Q. Find the current through 12Ω resistor in the network shown using the source transformation technique.





Apply $V \rightarrow I$


$$I = V = \frac{240}{24} = 10A //$$

Apply $I \rightarrow V$


$$V = IR = 30 \times 8 = 120V //$$

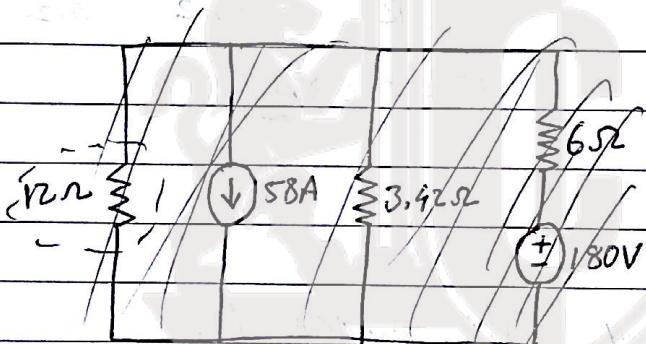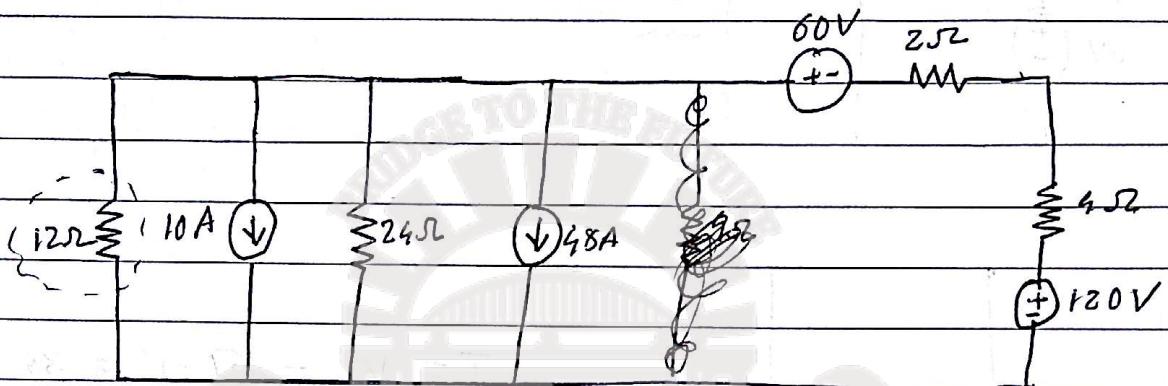

Apply $V \rightarrow I$

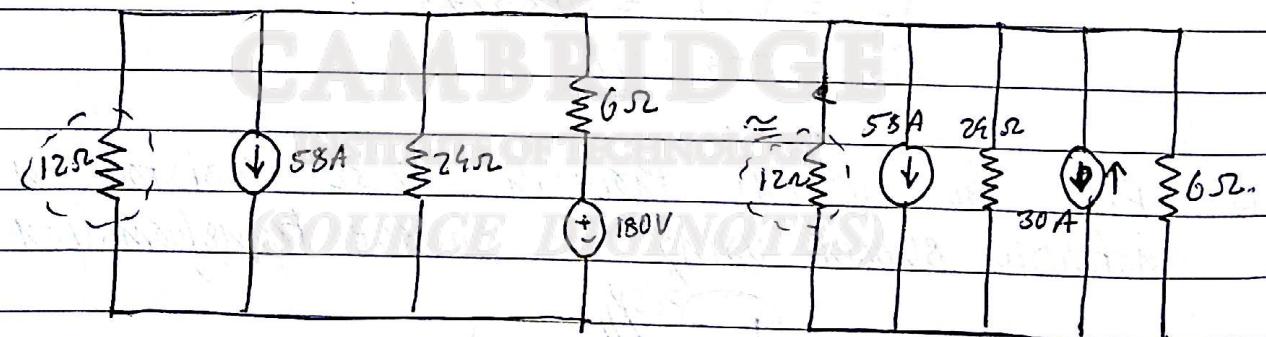
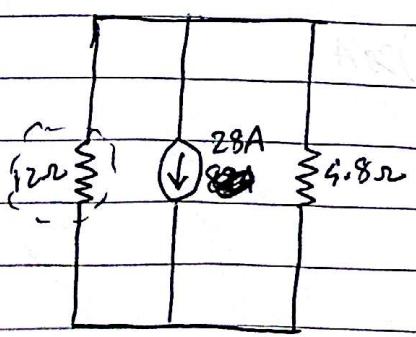
$$I = \frac{V}{R} = \frac{180}{6.5} = 30A -$$




According to current divider rule,
current through 12Ω resistor is,

$$I_{12\Omega} = \frac{28 \times 4.8}{12 + 4.8} = \frac{28 \times 4.8}{16.8}$$

$$I_{12\Omega} = 8A //$$


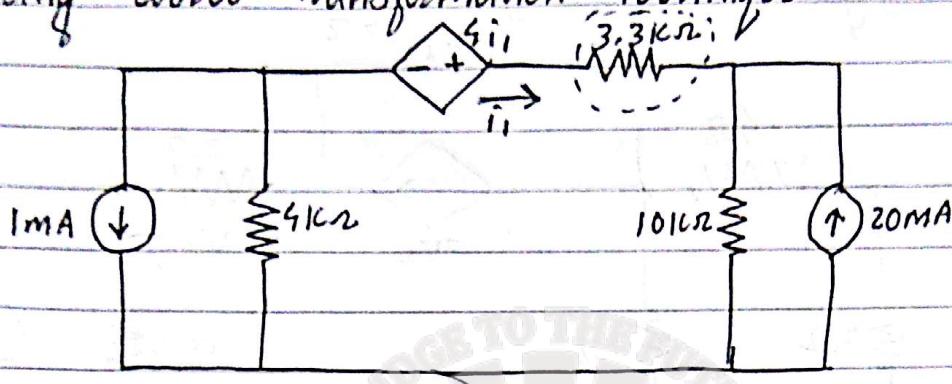
Q. Find the current i_1 in the network shown using source transformation technique.



Apply $E \rightarrow V$:

$$V = IR = 10^{-3} \times 4 \times 10^3 = 4\text{V}$$

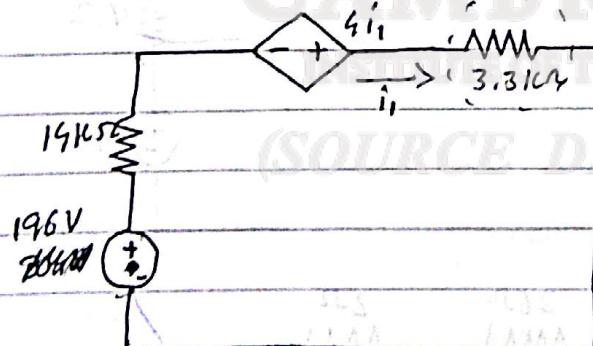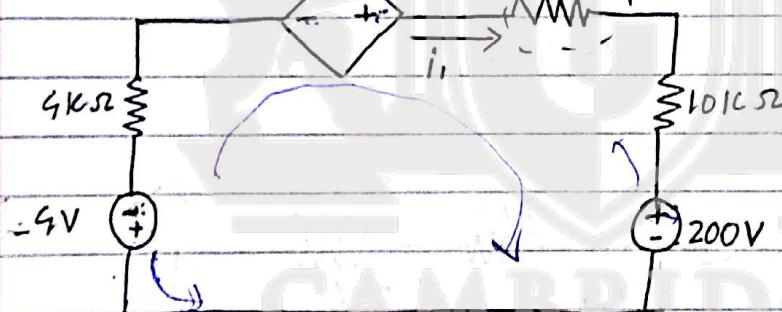~~$V = 20 \times 10^{-3} \times 10 \times 10^3 = 200\text{V}$~~



$$\text{Current } i_1 = \frac{V}{R} = \frac{196 - 4i_1}{17.3 \times 10^3}$$


$$17.3 \times 10^3 \cdot i_1 = 196 - 4i_1 \Rightarrow i_1 (17.3 + 4) = 196$$

$$i_1 = \frac{196}{17304} = 0.0113$$

$$i_1 = 11.3\text{mA}$$

$$200 - u_{ij} - 200$$


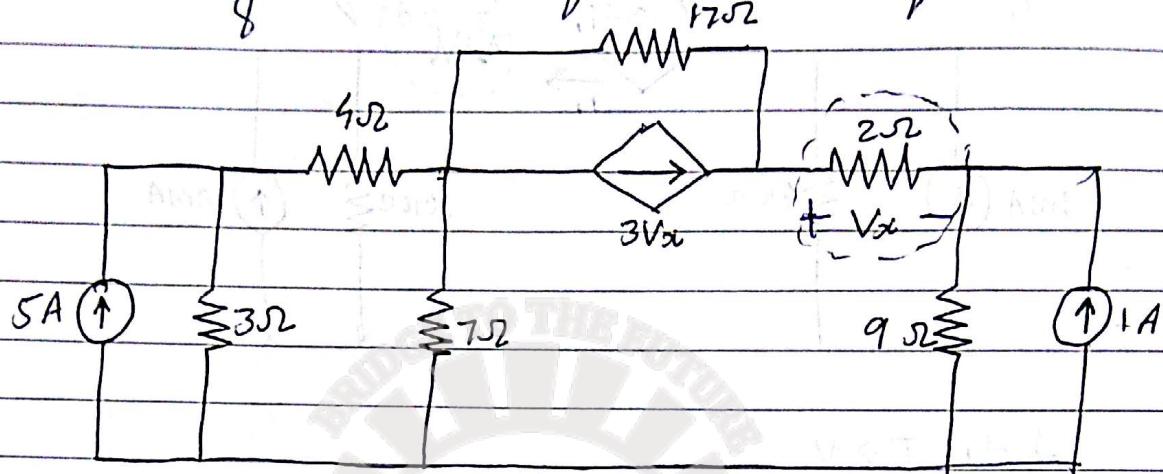
Q. Find the current through 2Ω resistor in the network shown using source transformation technique.



Apply $I \rightarrow V$


$$\begin{aligned} V &= IR = 5 \times 3 \\ V &= 15V_{\parallel} \end{aligned} \quad \begin{aligned} V &= IR = 1 \times 9 \\ V &= 9V_{\parallel} \end{aligned}$$
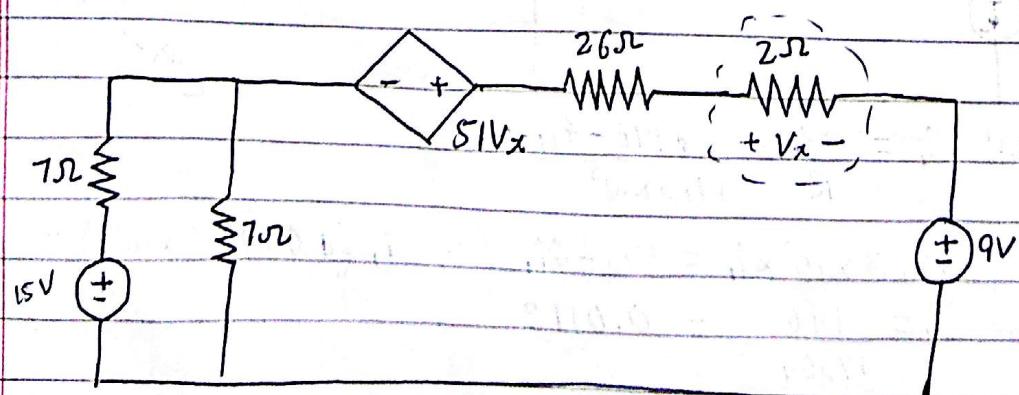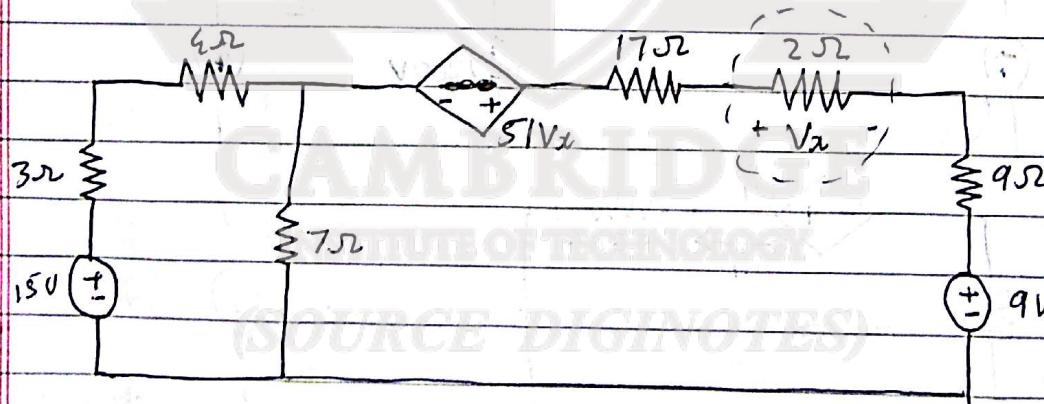
$$\begin{aligned} V &= IR \Rightarrow V = 3V_x \times 17 \\ V &= 51V_x \end{aligned}$$




Apply ~~$V \rightarrow I$~~ ,
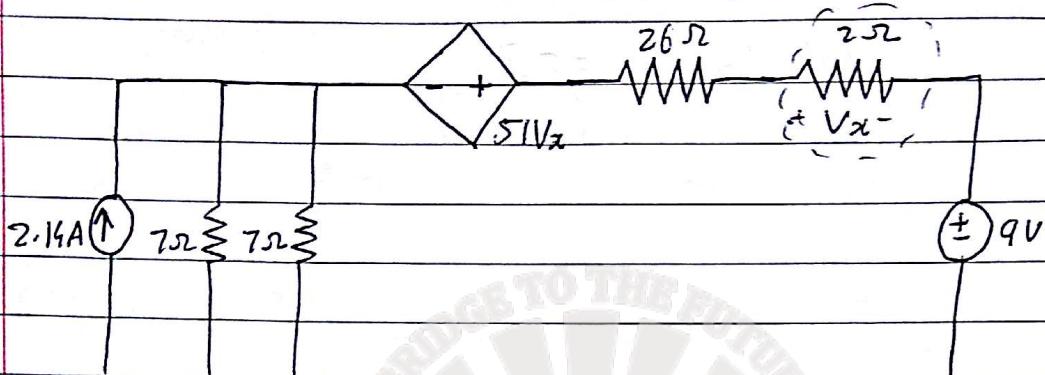
$$I = \frac{V}{R} = \frac{15}{7} = 2.14 A$$



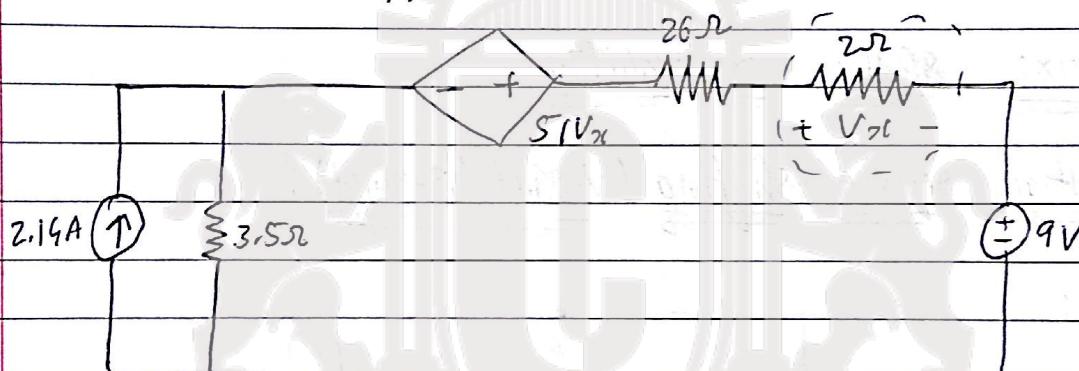
$$R_{eqn} = \frac{7 \times 7}{14} = 3.5 \Omega$$



Apply ~~$I \rightarrow V$~~ .

$$V = IR$$

$$V = 2.14 \times 3.5 = 7.49 V$$

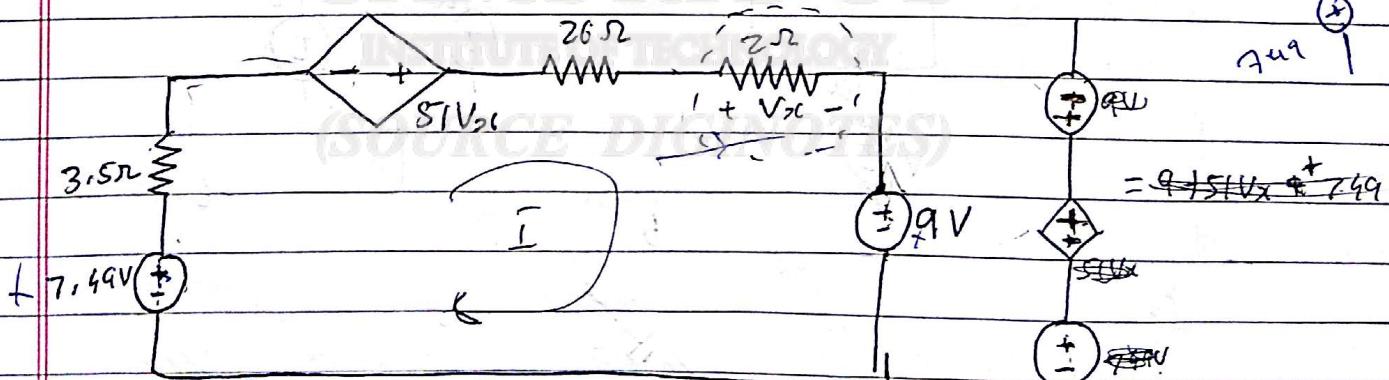

∴ Current through 2Ω resistor,

~~$$I_{2\Omega} = \frac{V}{R} = \frac{-7.49 - 5IVx + 9}{3.5} \quad (Vx = I \times 2 = 2I)$$~~

~~$$31.5I = 1.51 - 5IVx \quad (2I) \Rightarrow 31.5I = 1.51 - 102I$$~~

~~$$133.5I = 1.51 \Rightarrow I =$$~~

~~$$(-) \quad (-) \quad (+)$$~~

~~$$x 7.49 + 5IVx - 9V$$~~

\therefore Current through 2Ω resistor,

$$I = \frac{V}{R} = \frac{7.49 + 5IV_{2C} - 9}{31.5}$$

$$\text{but } V_{2C} = I_2 = 2A.$$


1/4 -

Q


Voltage Shifting or Mobility


1. Voltage source shifting (V-shift / E-shift):

Ex:

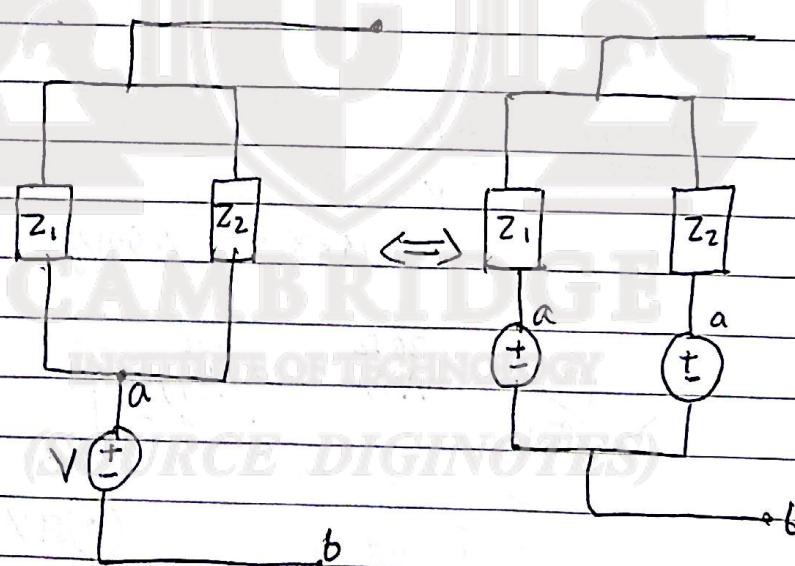


Ex:

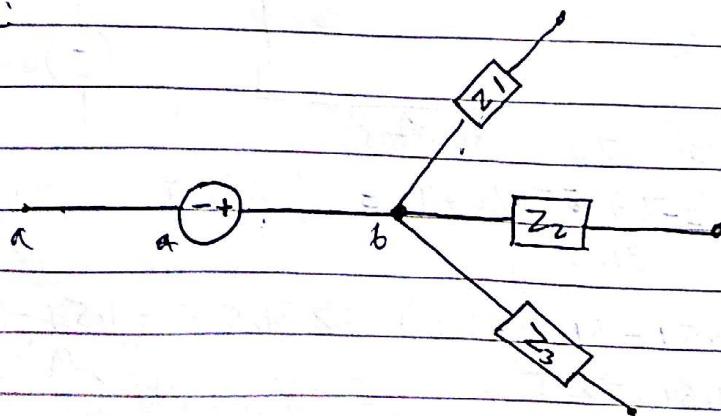

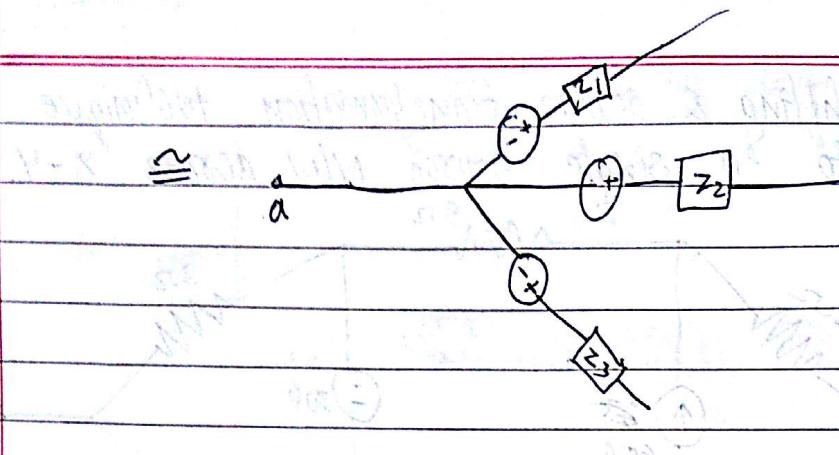


2. Current source shifting (I-shift):


Ex:

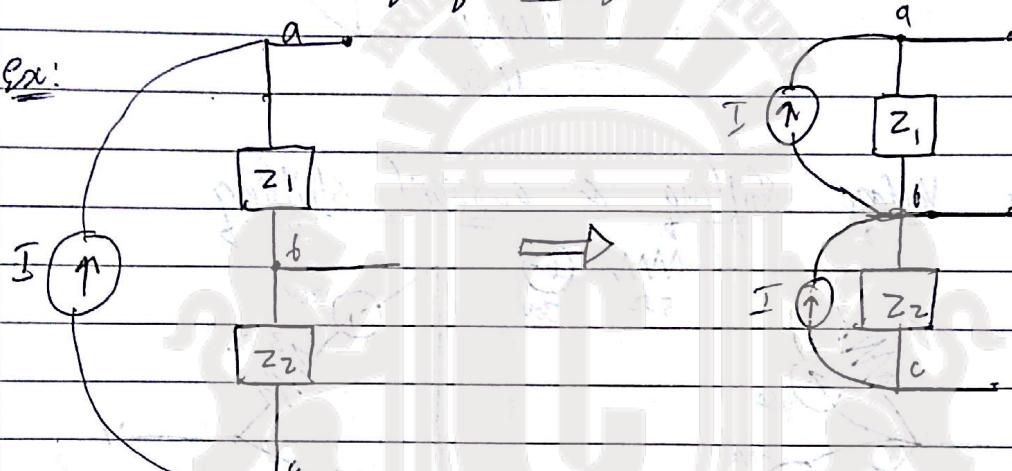


Ex:

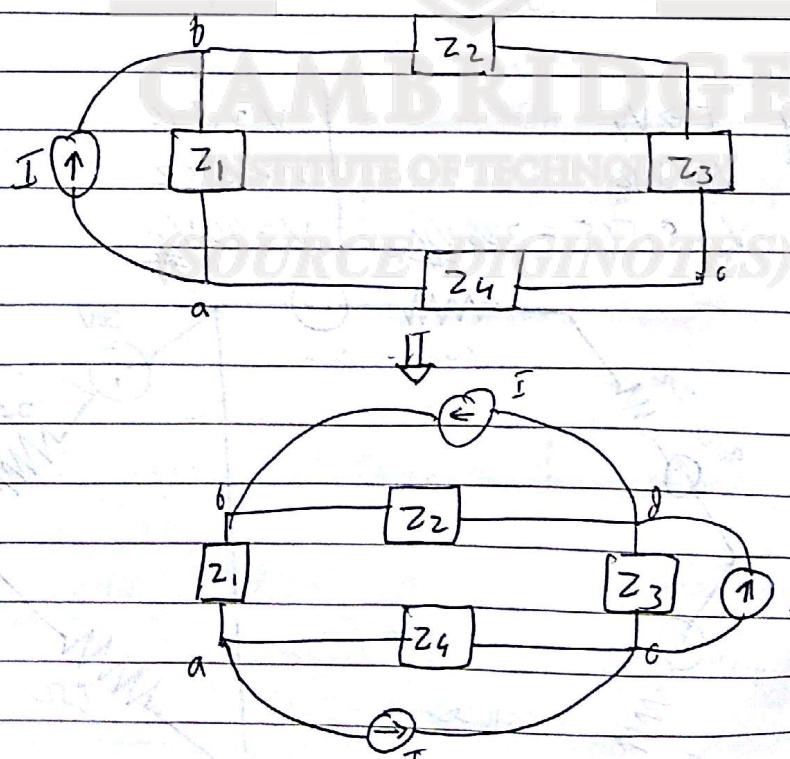

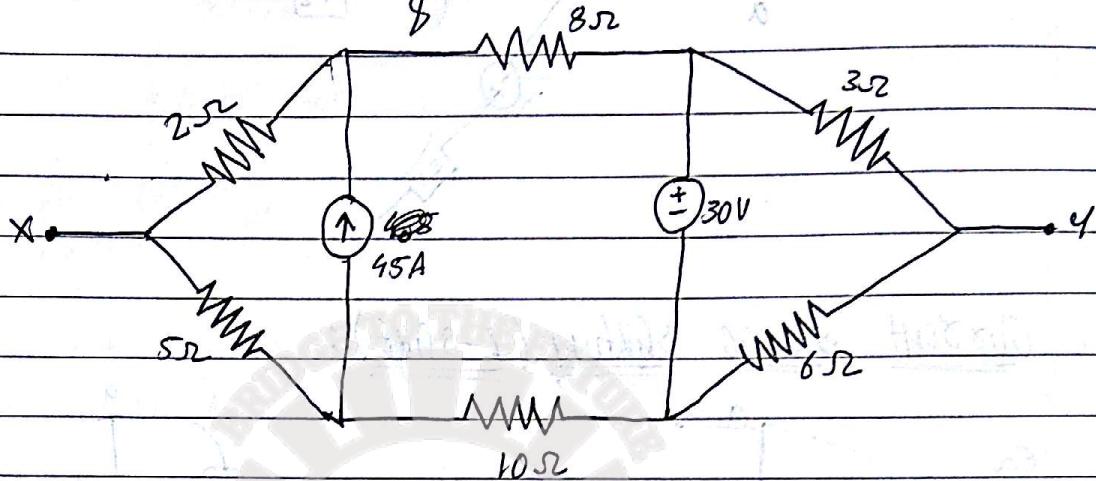Q. Using source shifting & source transformation technique
find the N.W across X-Y.



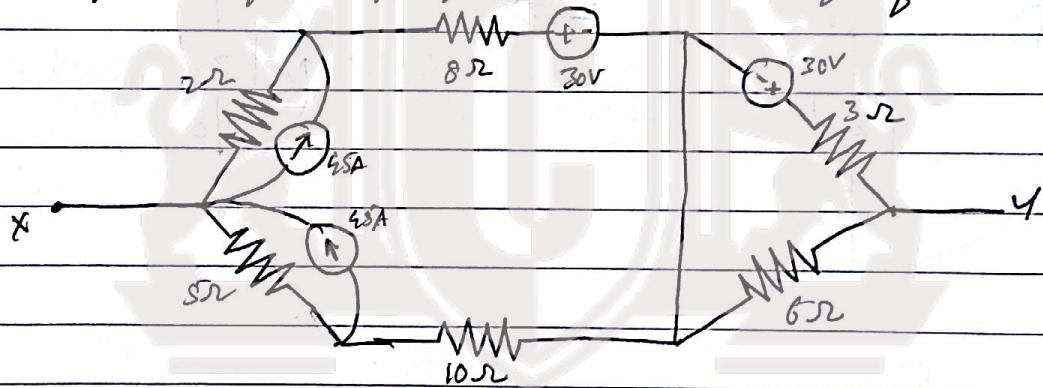Apply Voltage shifting & current shifting



Now Apply $I \rightarrow V$,


$$V = IR$$


$$V = 45 \times 5 = 225 \text{ V}$$

$$V = IR$$

$$V = 45 \times 2 = 90 \text{ V}$$

$$V = 90 \text{ V}$$



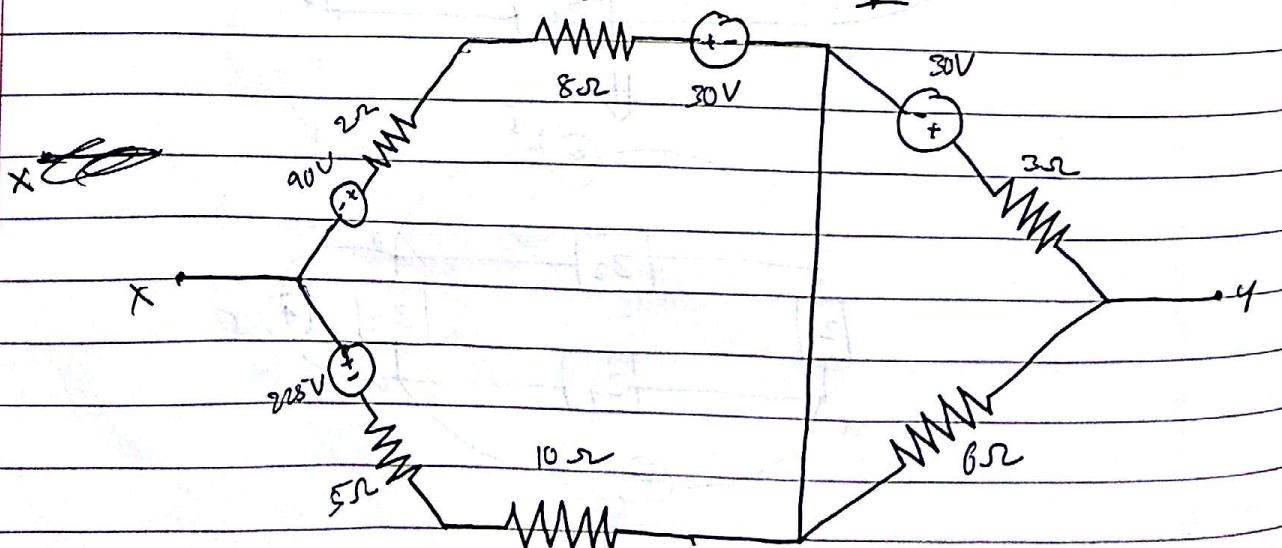


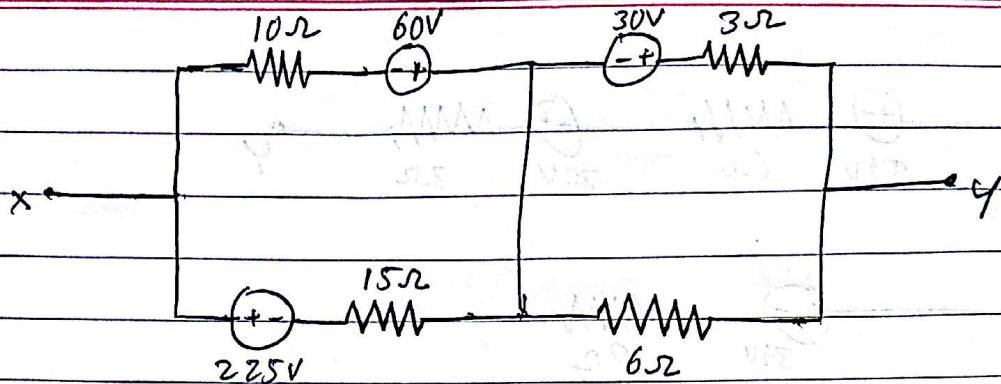

Apply $V \rightarrow I$, $I = \frac{V}{R} = \frac{60}{10} = 6A$ ~~4~~

$$I = \frac{V}{R} = \frac{22.5}{15} = 1.5A$$
 ~~4~~

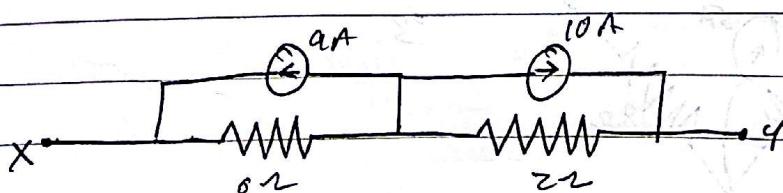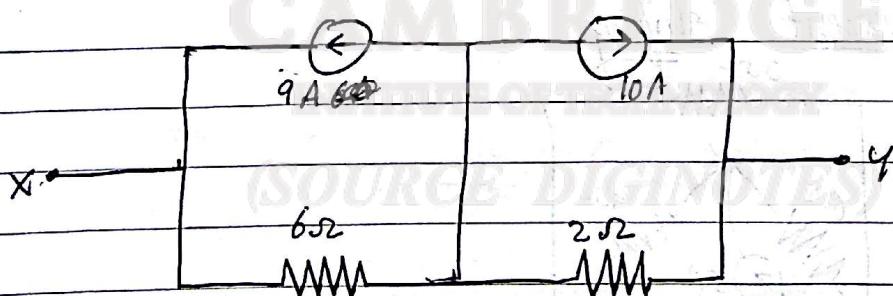
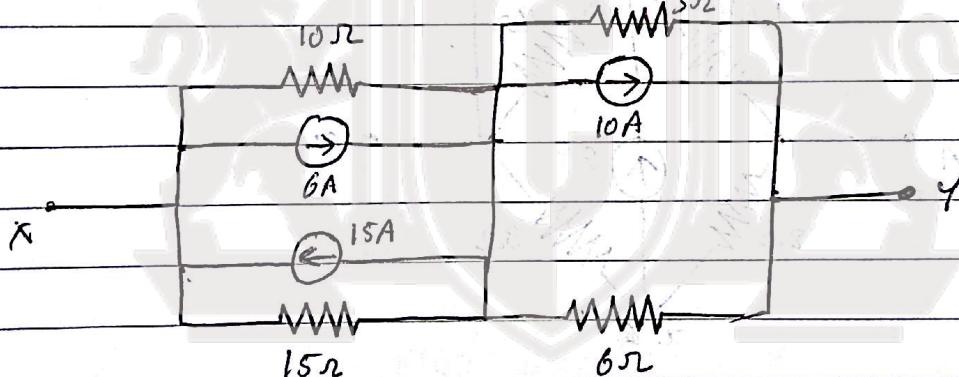
$$I = \frac{V}{R} = \frac{30}{3} = 10A$$
 ~~4~~




Now, apply $I \rightarrow V$

$$V = IR = 9 \times 6 = 54$$
 ~~0.9V~~


$$V = IR = 10 \times 2 = 20$$
 ~~V~~

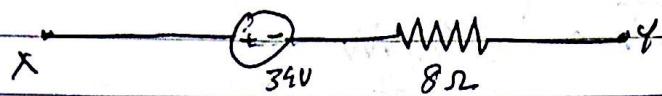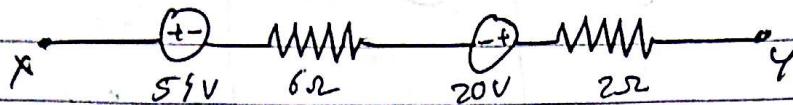

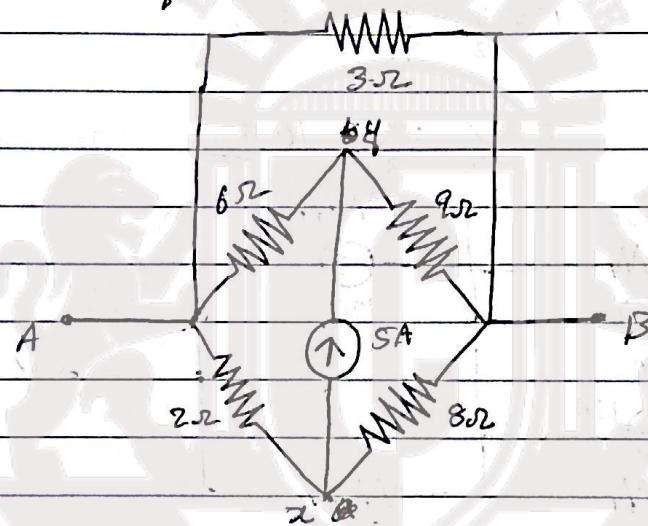Q. Find the voltage across the points A & B using source mobility concept and source transformation.




Apply current shifting

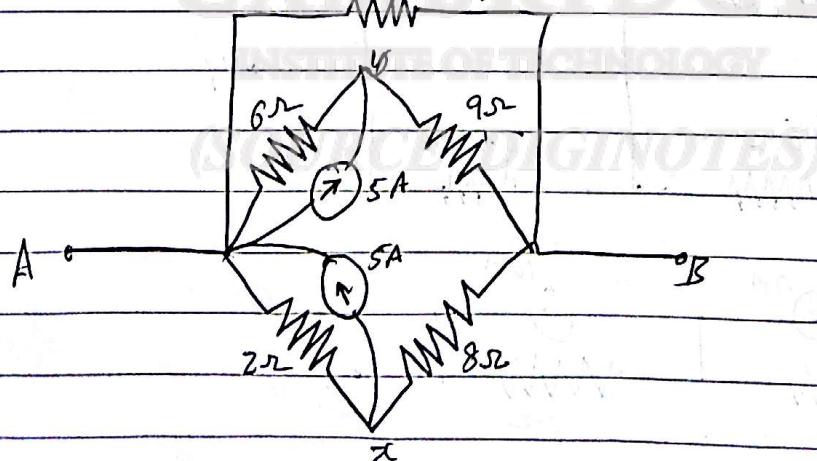

Now apply, $I \rightarrow V$: $V = I \times R = 5 \times 6 = 30V$.

$$V = I \times R = 5 \times 2 = 10V$$

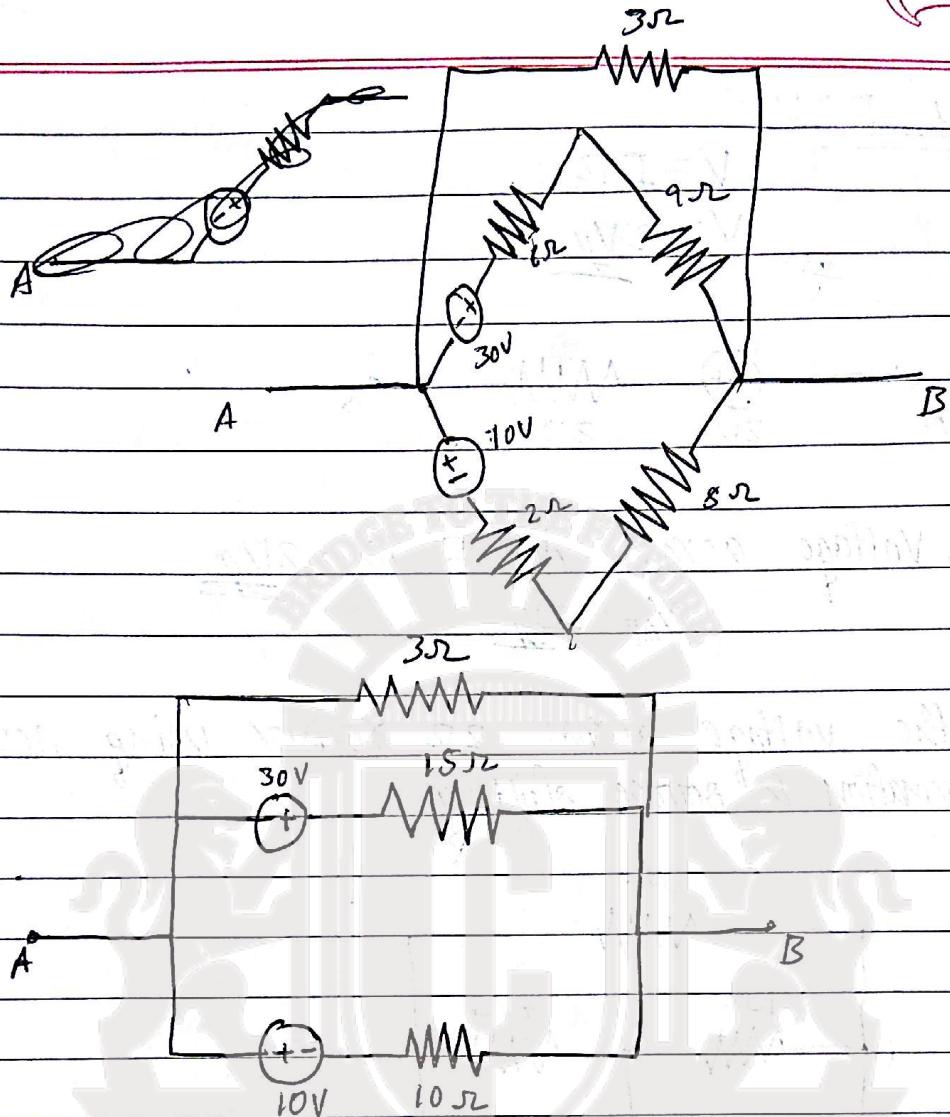


Apply Voltage to current transformation:

$$I = \frac{V}{R} = \frac{30}{15} = 2A \cancel{\text{if}}$$

$$\frac{I}{R_{eqv}} = \frac{1}{3} + \frac{1}{15} + \frac{1}{10} = \frac{1}{2}$$

$$R_{eqv} = 2 \Omega \cancel{\text{if}}$$

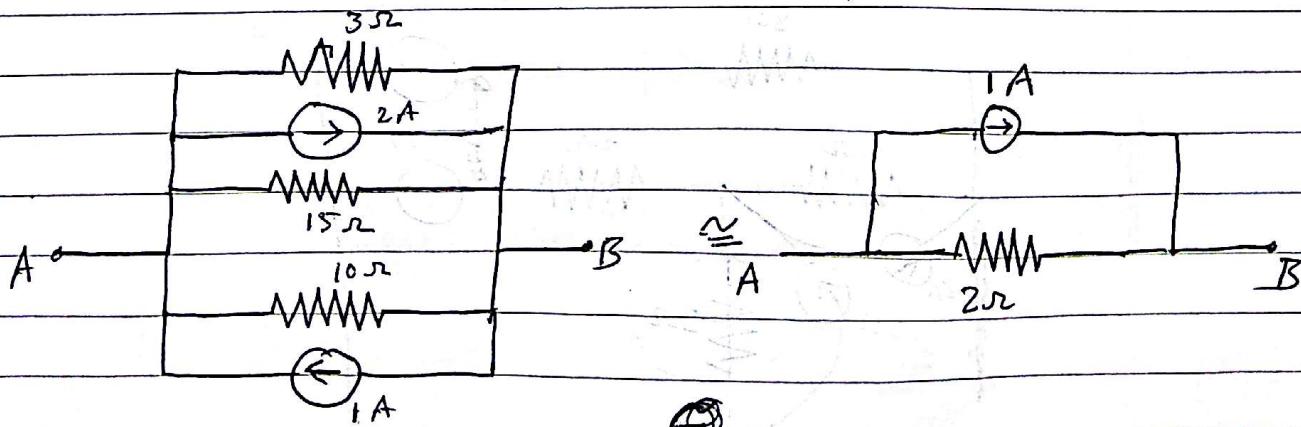
$$I = \frac{V}{R} = \frac{10}{10} = 1A \cancel{\text{if}}$$



Apply $I \rightarrow V$



$$V = IR$$

~~$V = 2V_L$~~

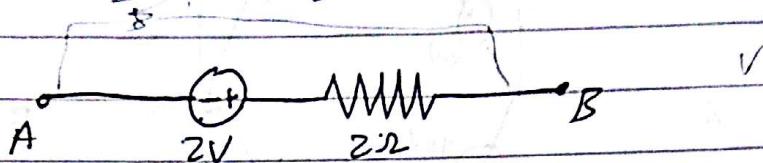
 \therefore Voltage across A & B is ~~$2V_L$~~



$$V_{AB} = \underline{2V_L}$$

** Q. Find the voltage across 2Ω resistor using source transformation & source shifting.

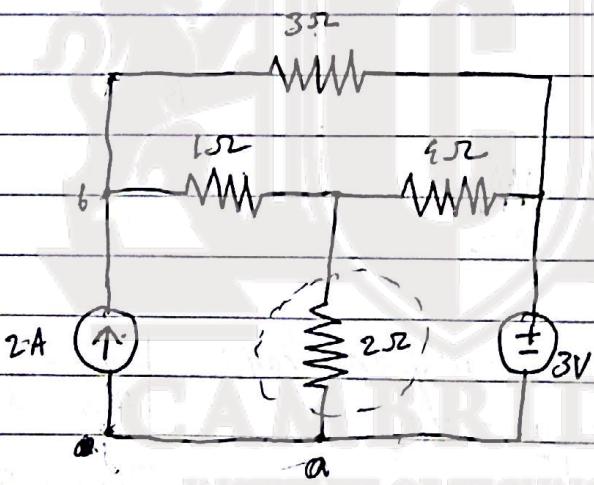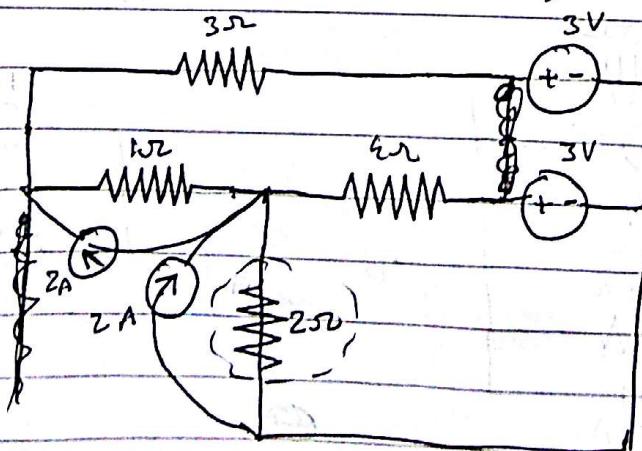
Apply current & voltage shifting

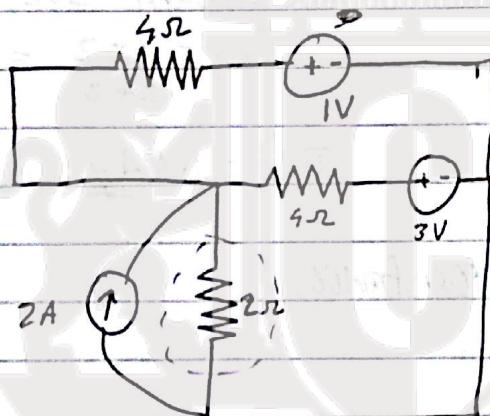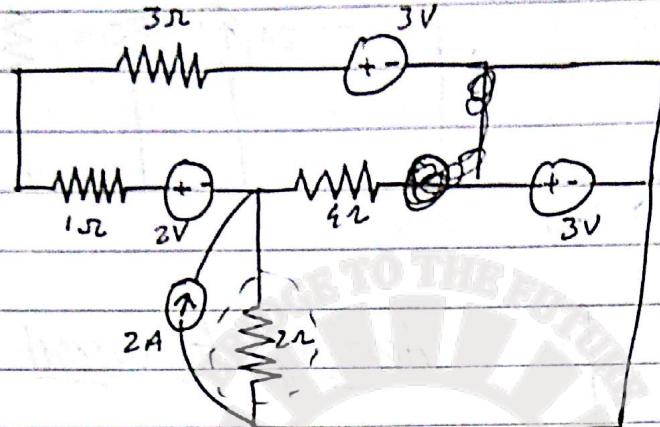
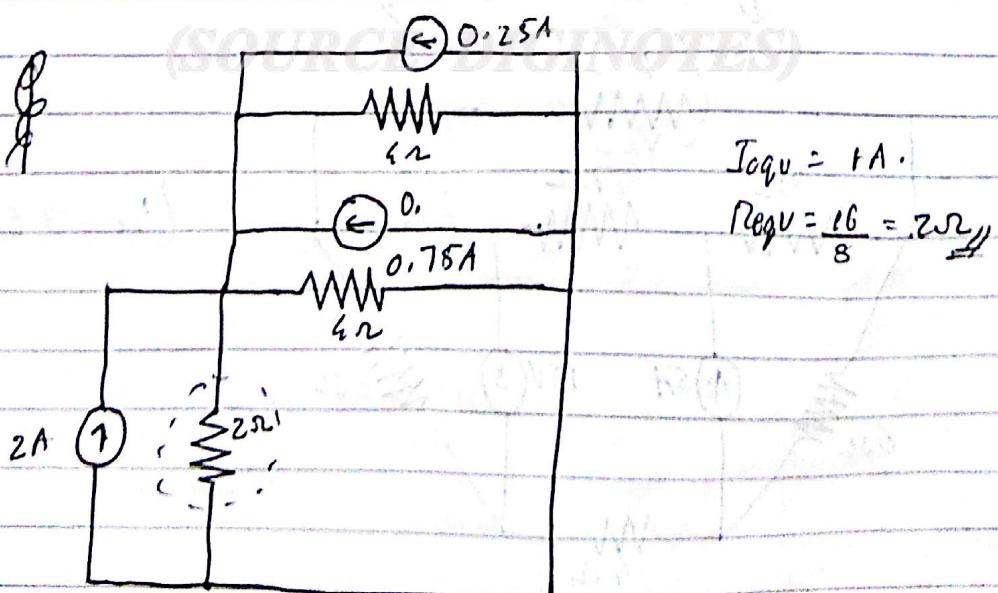
Now apply $I \rightarrow V$:



$$V = IR = 2 \times 1 = 2V$$



Now apply $V \rightarrow I$: $I = \frac{V}{R} = \frac{3}{4} = 0.75A$
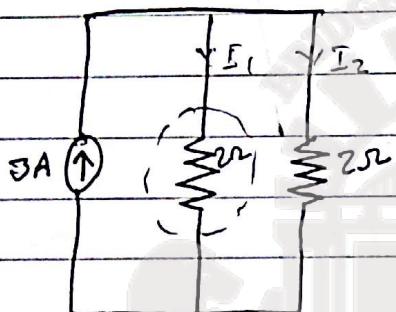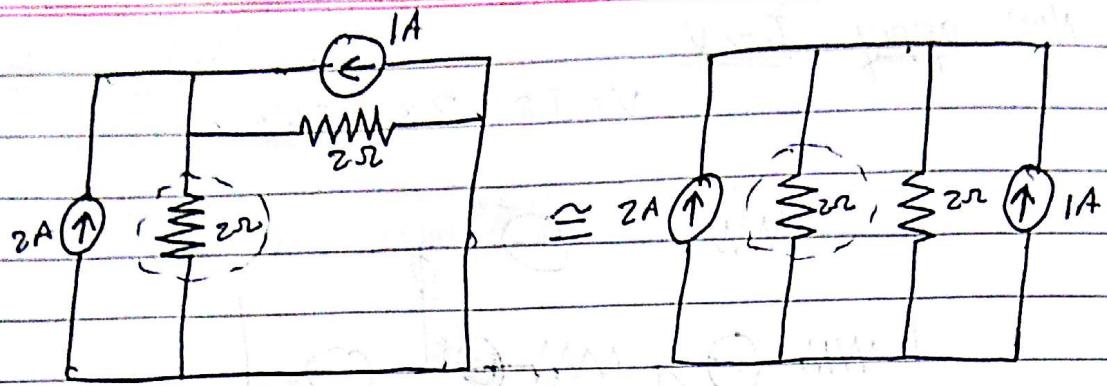
$$I = \frac{V}{R} = \frac{1}{4} = 0.25A$$





According to Current Division Rule

Current through 2Ω ,

$$I_{2\Omega} = \frac{3 \times 2}{2+2} = \frac{6}{4} = 1.5A$$

$$I_{2\Omega} = 1.5A$$


\therefore Voltage across 2Ω resistance,


$$V_{2\Omega} = I_1 \times R_2$$

$$V_{2\Omega} = 1.5 \times 2$$

$$V_{2\Omega} = 3V$$


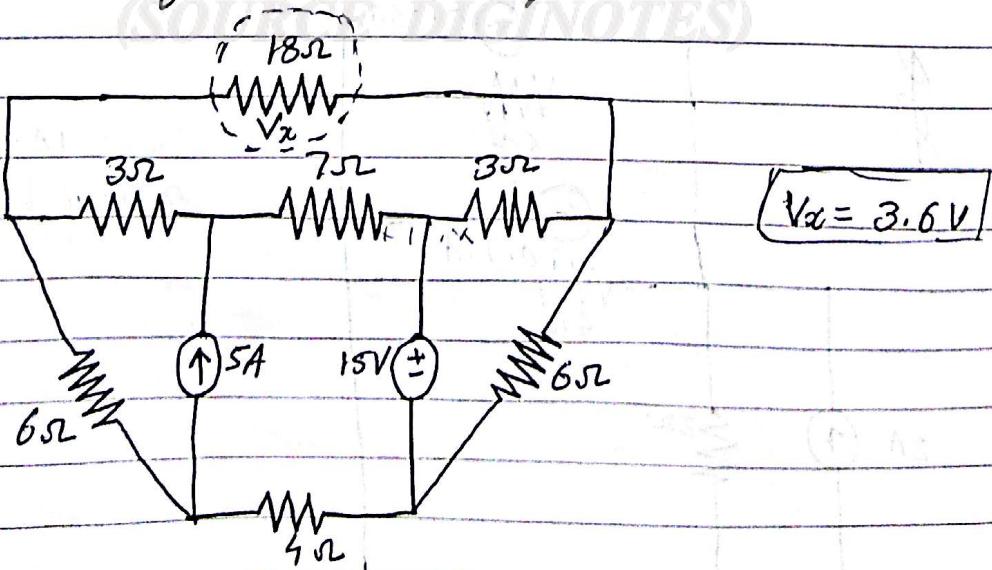
- Q. Find the voltage V_x using source shifting and source transformation techniques.



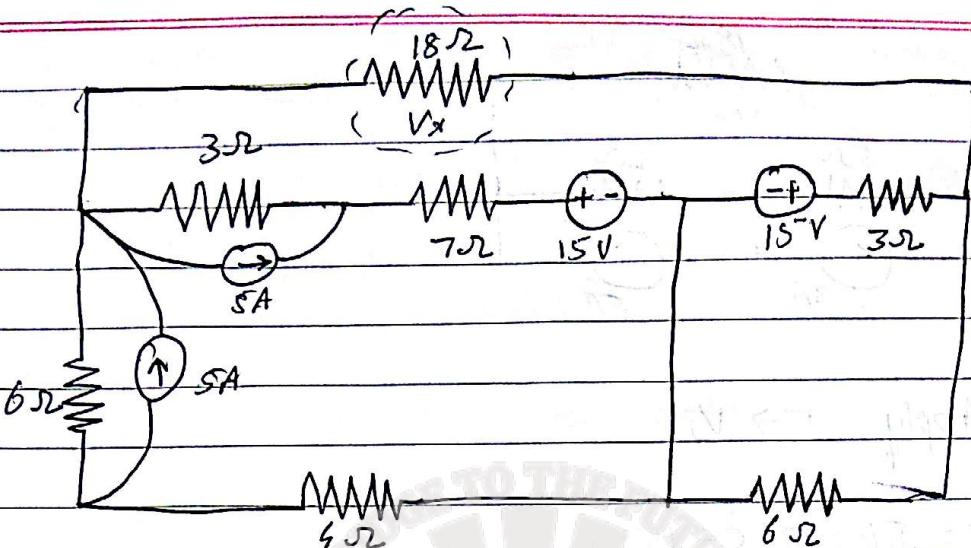

Apply $I \rightarrow V$: $V = IR = V = 5 \times 6 = 30V$


$$V = IR = 3 \times 5 = 15V$$

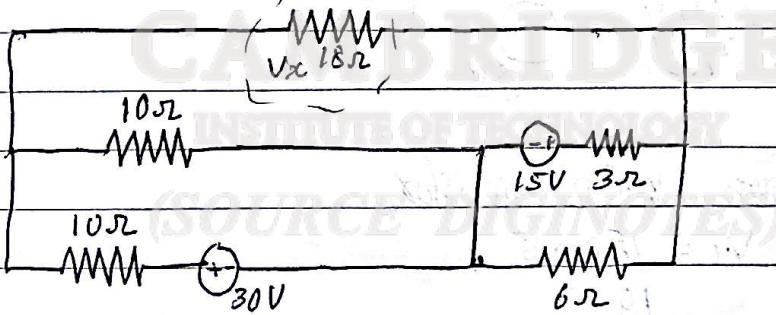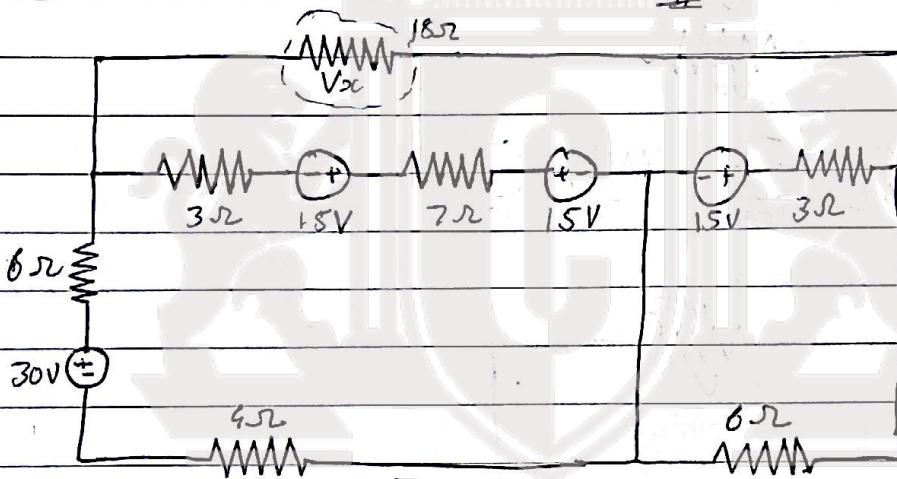


Apply $V \rightarrow I$:

$$I = \frac{V}{R} = \frac{30}{10} = 3A$$

$$I = \frac{15}{3} = 5A$$


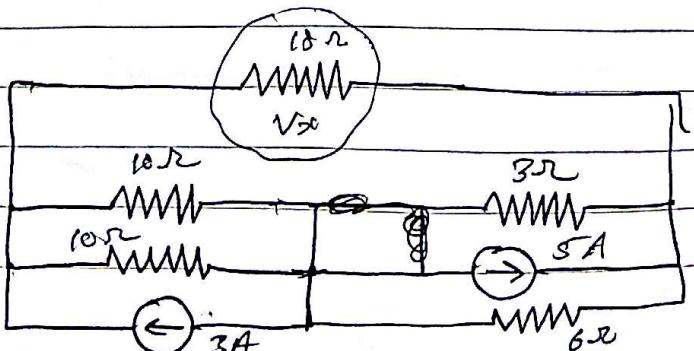


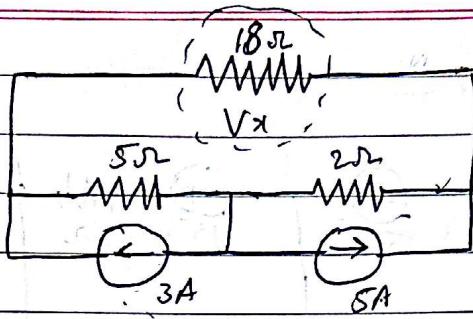

Apply $I \rightarrow V$,

$$V = IR = 3 \times 5 = 15 \text{ V}$$

$$V = IR = 5 \times 2 = 10 \text{ V}$$

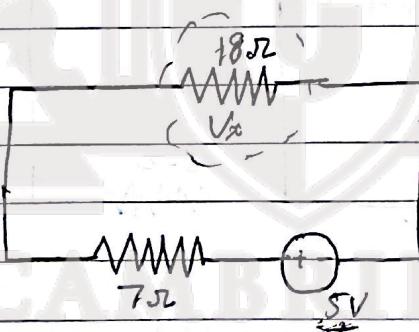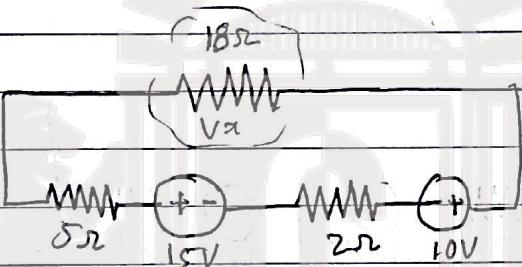


Voltage across 18Ω resistor,

$$V_x = \frac{18\Omega \times 5}{18 + 7}$$


$$V_x = 3.0 \text{ V}$$

Star \rightarrow Delta and Delta \rightarrow Star transformation:

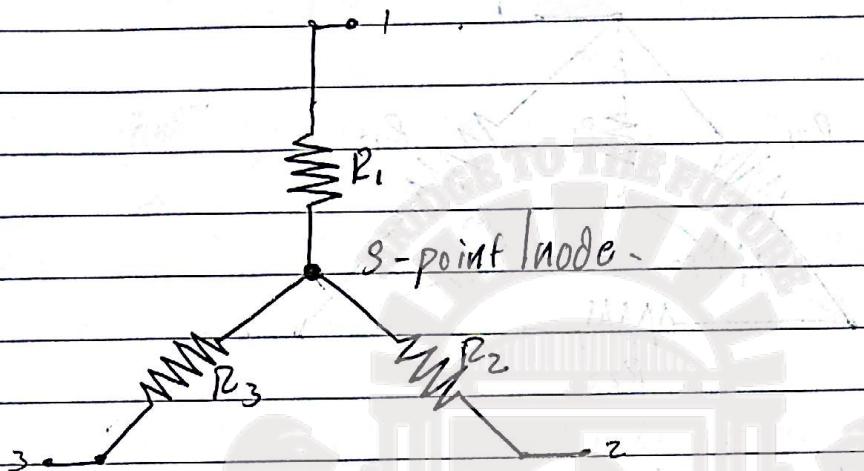- Three resistors are said to be connected in star connection when they form a node or junction.



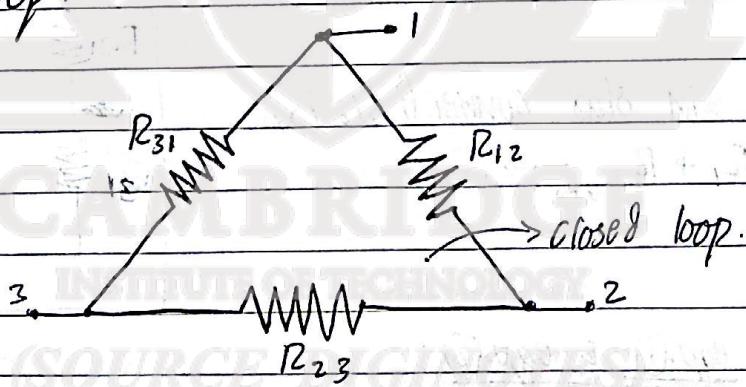
- Three resistances or impedances are said to be connected in delta connection when they form a closed loop.



- Star and Delta connections play a major role in NA. to find voltage across (or) current through the given element.

Star \rightarrow Delta Conversion & Delta \rightarrow Star Conversion

Consider the following Net;

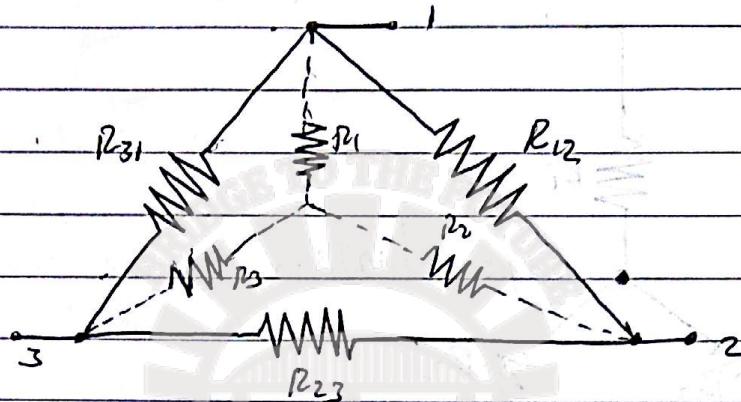


\rightarrow The equivalent resistance b/w the two terminals 1 & 2, when terminal 3 is absent or not connected is,

$$(R_{23} + R_{31}) \times R_{12} \quad \text{if } \cancel{R_{13}} \rightarrow \textcircled{1}$$

$R_{12} + R_{23} + R_{31}$ (Delta connection)

Similarly, in star connection, is,
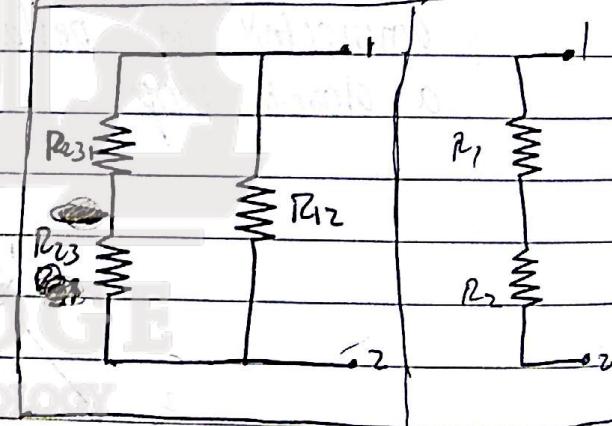
$$R_1 + R_2 \quad \text{if } \cancel{R_{31}} \rightarrow \textcircled{2}$$



Equate eqn. \textcircled{1} & eqn. \textcircled{2}:

$$(R_{23} + R_{31}) \times R_{12} = R_1 + R_2 \quad \text{if } \cancel{R_{13}} \rightarrow \textcircled{3}$$

$R_{12} + R_{23} + R_{31}$

Similarly, the equivalent resistance b/w the terminals 2 & 3 when terminal 1 is absent or not connected,

$$(R_{31} + R_{12}) \times R_{23} = R_2 + R_3 \quad \text{if } \cancel{R_{13}} \rightarrow \textcircled{4}$$

$R_{12} + R_{23} + R_{31}$

III'y, the equivalent resistance b/w the terminals 1 & 3 when terminal 2 is not connected (or) absent,

$$\frac{(R_{12} + R_{23}) \times R_{31}}{R_{12} + R_{23} + R_{31}} = R_1 + R_3 \cancel{\text{if}} \rightarrow \textcircled{3}.$$

Now add equations 3 and 5,

$$\frac{(R_{23} + R_{31}) \times R_{12} + (R_{12} + R_{23}) \times R_{31}}{R_{12} + R_{23} + R_{31}} = R_1 + R_2 + R_1 + R_3 \\ = 2R_1 + R_2 + R_3.$$

$$\frac{R_{12} R_{23} + R_{12} R_{31} + R_{31} R_{12} + R_{31} R_{23}}{R_{12} + R_{23} + R_{31}} = 2R_1 + R_2 + R_3$$

In place of $R_2 + R_3$, replace eqn \textcircled{3}

$$\Rightarrow \frac{R_{12} R_{23} + R_{12} R_{31} + R_{31} R_{12} + R_{31} R_{23}}{R_{12} + R_{23} + R_{31}} = 2R_1 + (R_{31} + R_{12}) \times R_{23}$$

$$\frac{R_{12} R_{23} + R_{12} R_{31} + R_{31} R_{12} + R_{31} R_{23}}{R_{12} + R_{23} + R_{31}} = 2R_1 + R_{23} R_{31} + R_{23} R_{12}$$

$$\frac{R_{12} R_{23} + 2R_{12} R_{31} + R_{31} R_{23} - R_{23} R_{31} - R_{23} R_{12}}{R_{12} + R_{23} + R_{31}} = 2R_1$$

$$\frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}} = R_1$$

$$\therefore \boxed{R_1 = \frac{R_{12} R_{31}}{R_{12} + R_{23} + R_{31}}} \cancel{\text{if}} \rightarrow \textcircled{6}.$$

Similarly: $\boxed{R_2 = \frac{R_{23} R_{12}}{R_{12} + R_{23} + R_{31}}} \cancel{\text{if}} \rightarrow \textcircled{7}.$

$$\boxed{R_3 = \frac{R_{31} R_{23}}{R_{12} + R_{23} + R_{31}}} \cancel{\text{if}} \rightarrow \textcircled{8}.$$

Now multiply the equations, 6 & 7, 7 & 8. & and 8 & 6.

$$R_1 \times R_2 = \frac{R_{12} R_{21}}{R_{12} + R_{23} + R_{31}} \times \frac{R_{23} \times R_{12}}{R_{12} + R_{23} + R_{31}} = \frac{R_{12}^2 R_{23} R_{31}}{(R_{12} + R_{23} + R_{31})^2} \cancel{\neq} \quad (9)$$

$$R_2 \times R_3 = \frac{R_{23} R_{12}}{(R_{12} + R_{23} + R_{31})^2} \times \frac{R_{31} R_{23}}{(R_{12} + R_{23} + R_{31})^2} = \frac{R_{23}^2 R_{12} R_{31}}{(R_{12} + R_{23} + R_{31})^2} \cancel{\neq} \quad (10)$$

$$R_1 \times R_3 = \frac{R_{12} R_{21}}{(R_{12} + R_{23} + R_{31})^2} \times \frac{R_{31} R_{23}}{(R_{12} + R_{23} + R_{31})^2} = \frac{R_{31}^2 R_{12} R_{23}}{(R_{12} + R_{23} + R_{31})^2} \cancel{\neq} \quad (11)$$

All eqns. 9, 10 & 11.

$$R_1 R_2 + R_2 R_3 + R_1 R_3 = \frac{R_{12}^2 R_{23} R_{31} + R_{23}^2 R_{12} R_{31} + R_{31}^2 R_{12} R_{23}}{(R_{12} + R_{23} + R_{31})^2}$$

$$R_1 R_2 + R_2 R_3 + R_1 R_3 = (R_{12} R_{23} R_{31}) (R_{12} + R_{23} + R_{31}) \\ (R_{12} + R_{23} + R_{31})^2$$

$$R_1 R_2 + R_2 R_3 + R_1 R_3 = \frac{R_{12} R_{23} R_{31}}{R_{12} + R_{23} + R_{31}}$$

$$\text{But } R_3 = \frac{R_{31} R_{23}}{R_{12} + R_{23} + R_{31}}$$

$$\therefore R_1 R_2 + R_2 R_3 + R_1 R_3 = \underline{R_{12}}, \underline{R_3}$$

$$\therefore R_{12} = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3}$$

$$R_{12} = \frac{R_1 R_2}{R_3} + \frac{R_2 R_3}{R_3} + \frac{R_1 R_3}{R_3}$$

$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

III^y,

$$R_{23} = \frac{R_2 + R_3 + R_2 R_3}{R_1}$$


$$R_{31} = \frac{R_3 + R_1 + R_2 R_3}{R_2}$$

III^y,


$$R_{23} = \frac{R_2 + R_3 + R_2 R_3}{R_1}$$

$$R_{31} = \frac{R_3 + R_1 + R_2 R_3}{R_2}$$


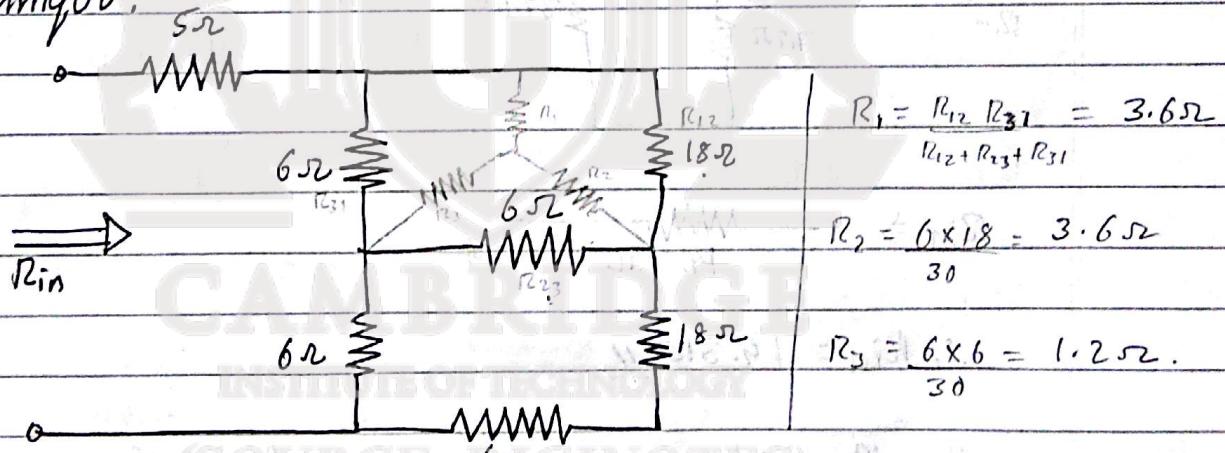
Q. Find the value of R_{in} using star-Delta conversion technique:



6Ω & 18Ω are in series.

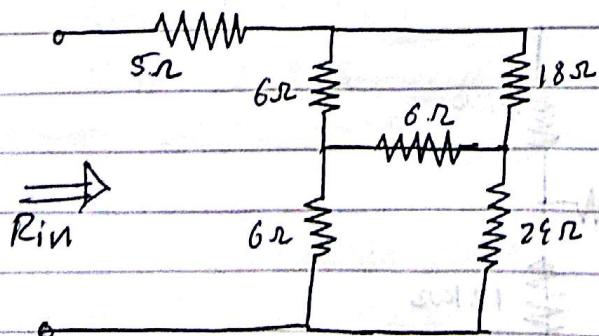


Apply $\Delta \rightarrow \star$

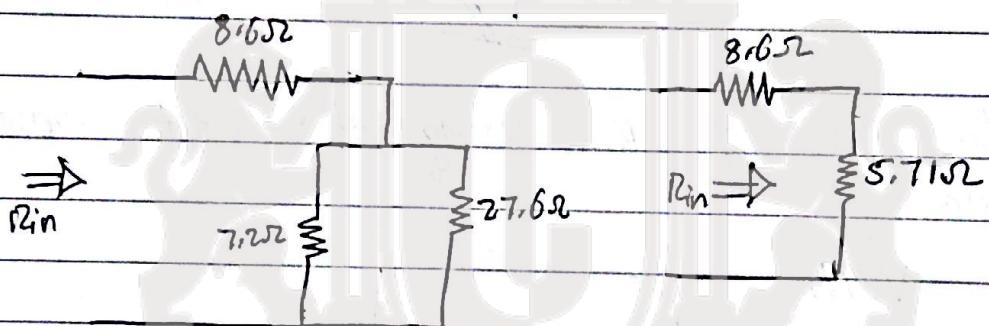
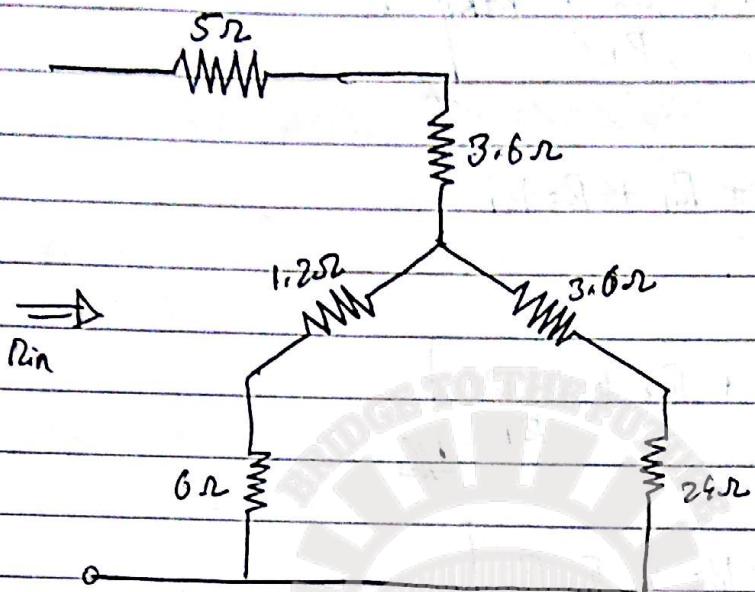


$$R_{in} \Rightarrow \frac{1}{\frac{1}{8.65} + \frac{1}{7.2}} = 5.71 \Omega$$

$$\therefore R_{in} = 5.71 \Omega$$

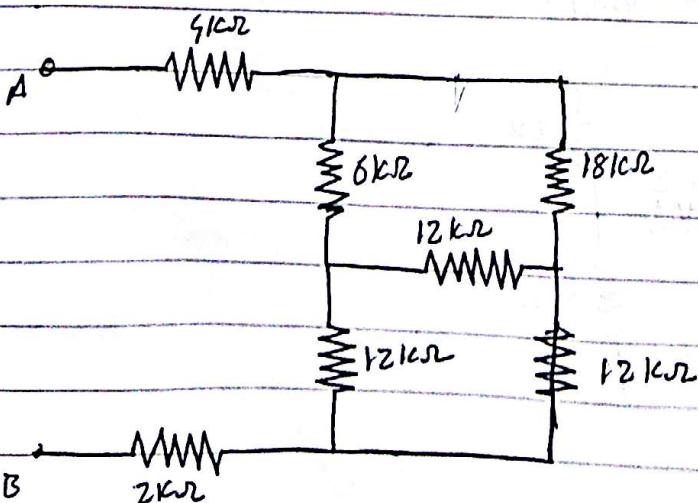HW.Q2 Find the value of R_{AB} using star-delta conversion.



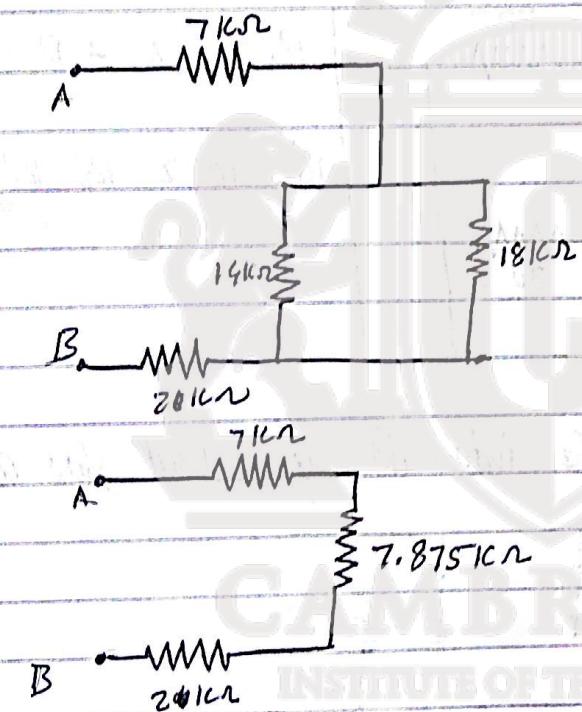
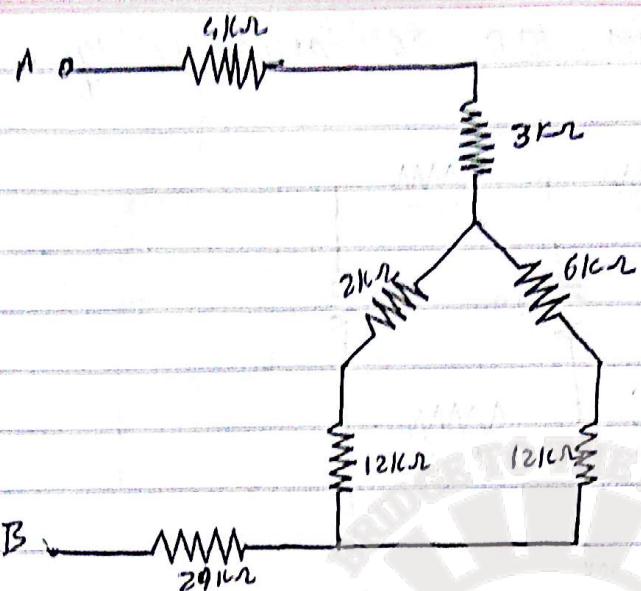


$$R_{AB} = 7k\Omega + 7.875k\Omega + 20k\Omega$$

$$R_{AB} = 14.875k\Omega + 20k\Omega$$

$$R_{AB} = 16.875k\Omega \cancel{+ 20k\Omega}$$

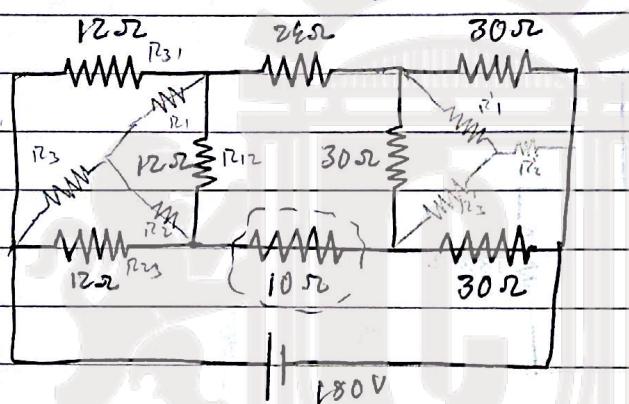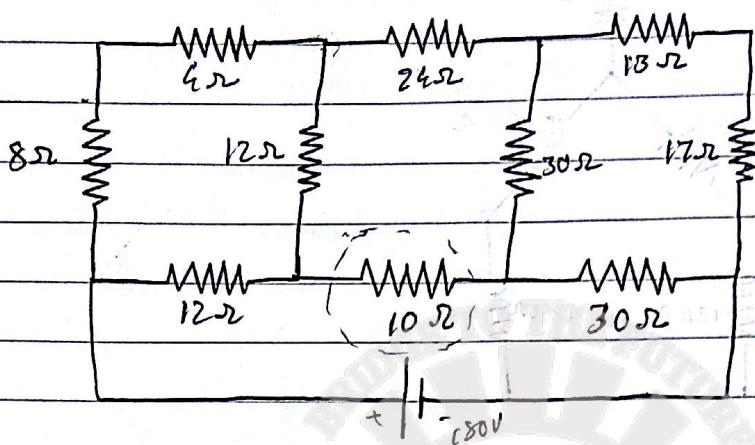
Q. Find the current in 10Ω resistance using star-delta conversion.




$$R_1 = 6\Omega \quad R_2 = R_3 = 12\Omega$$

$$R'_1 = 10\Omega \quad R'_2 = R'_3 = 30\Omega$$

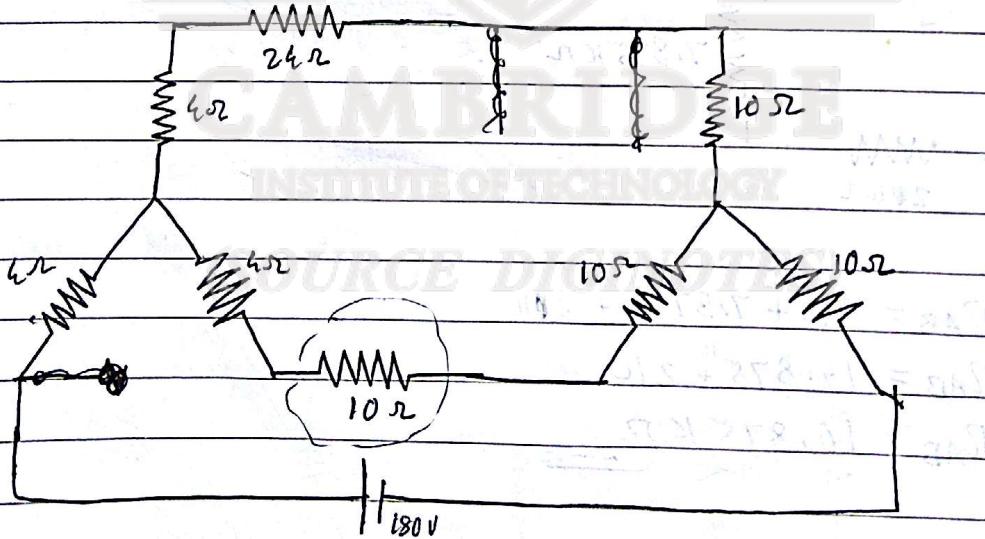Convert both the delta into its equivalent star connection.



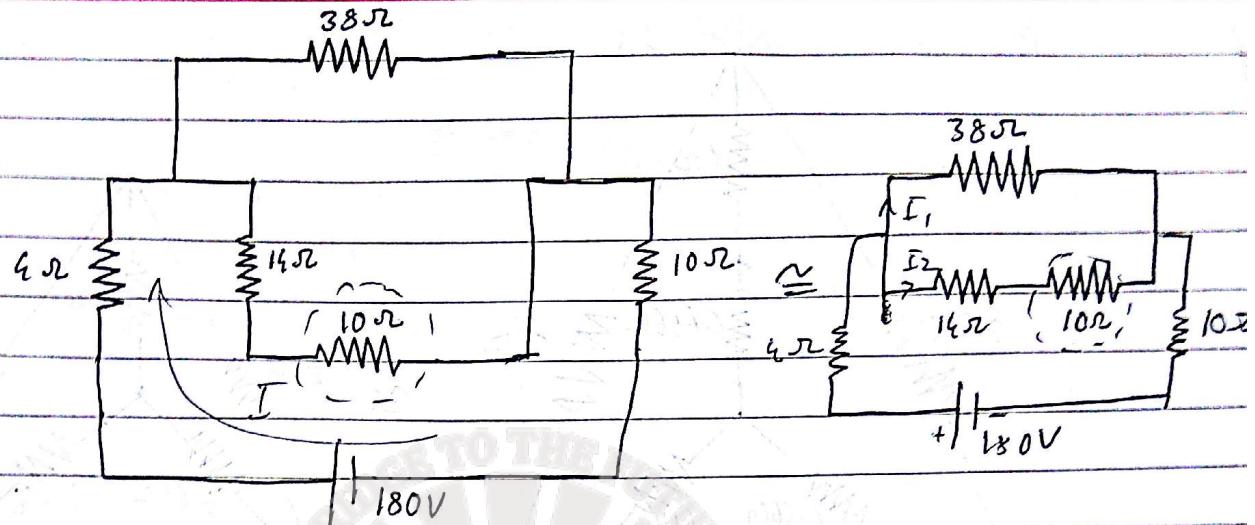

~~ITX~~ Now, Current, $I = \frac{V}{R_{eqv}} = \frac{180}{R_{eqv}}$

$$R_{eqv} = 4 + \frac{38}{14+38+10}$$

$$R_{eqv} = 28.75\Omega$$


$$\text{Current } I = \frac{180}{28.7} = 6.27A$$

Current through 10Ω resistor,



$$I_2 = I_{10\Omega} = \frac{10 \times 28.7}{38+24} = 6.27 \times \frac{38}{38+24}$$

$$I_2 = 3.84A$$

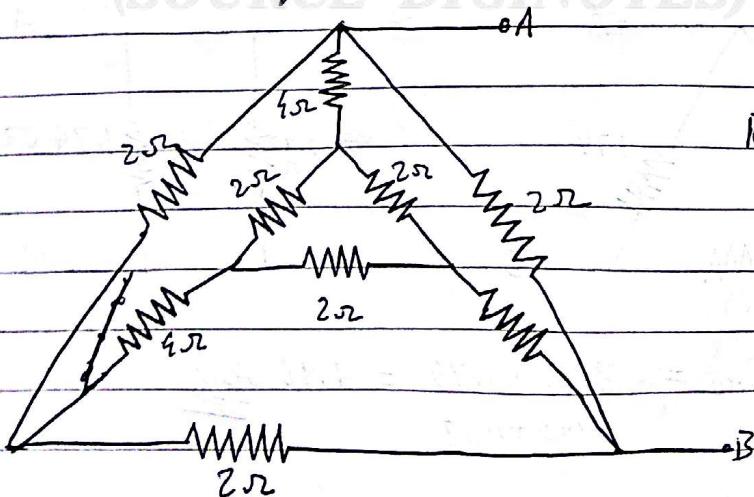Q. Find the value of R_{AB} in the NW using Y-Δ conversion.


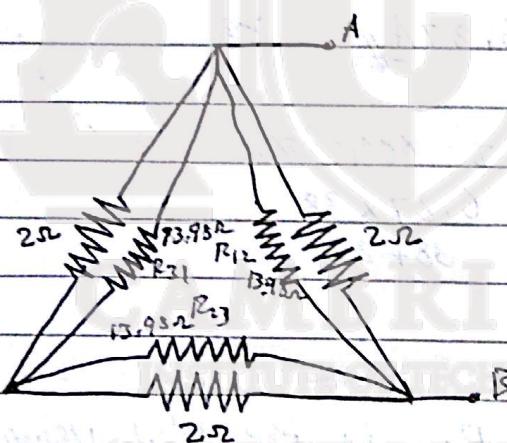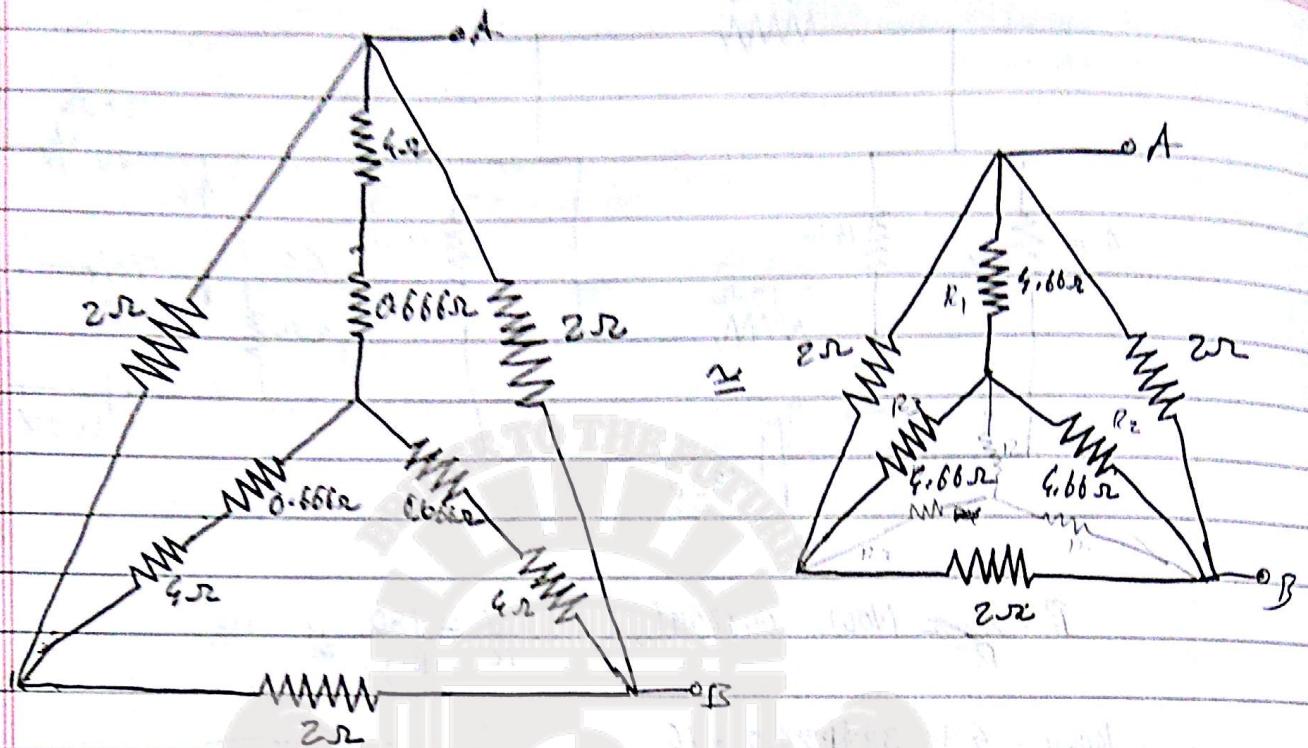
$$R_{AB} = \frac{2 \times 2}{2+2} = 0.6667\Omega$$




$$R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3}$$

$$R_{12} = 4.66 + 4.66 + \frac{4.66 \times 4.66}{4.66}$$


$$R_{12} = 13.98 \cancel{\Omega}$$
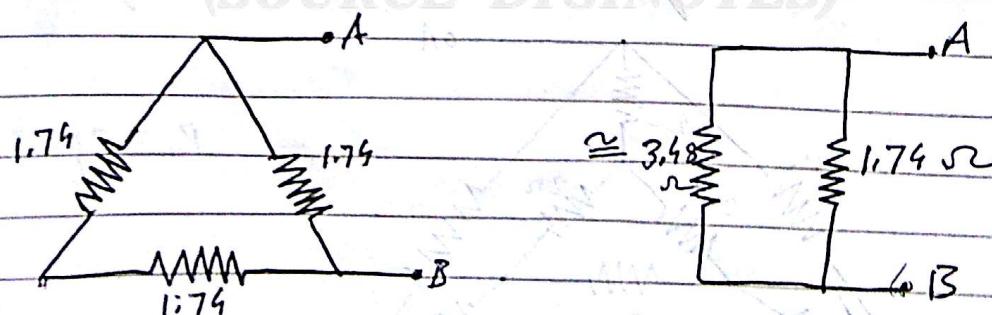
$$Req = \frac{2 \times 13.98}{2 + 13.98} = 1.74$$








$$R_{AB} = \frac{3.48 \times 1.74}{3.48 + 1.74} = 1.16 \cancel{\Omega}$$

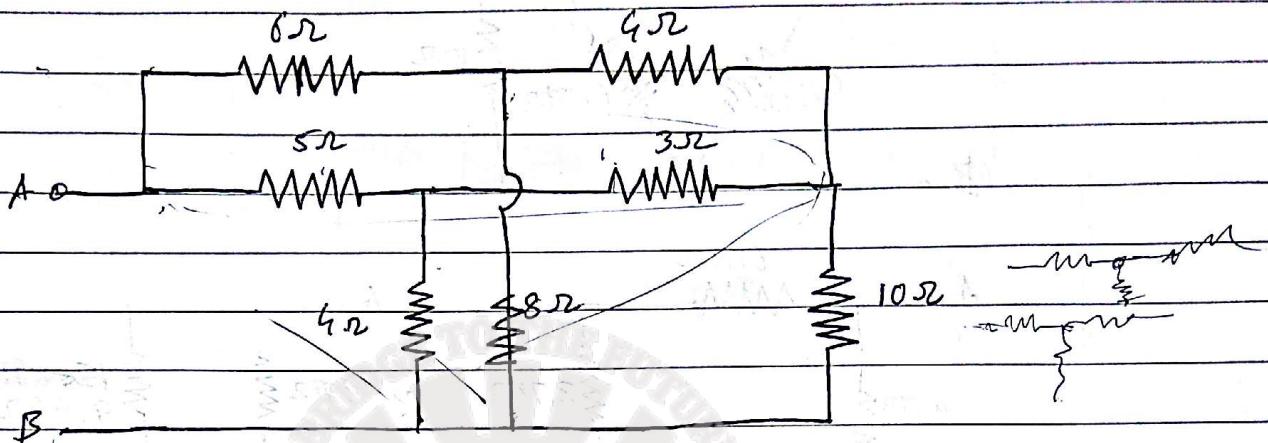Q. Find the value of the resistance R_{AB} in the Net shown.



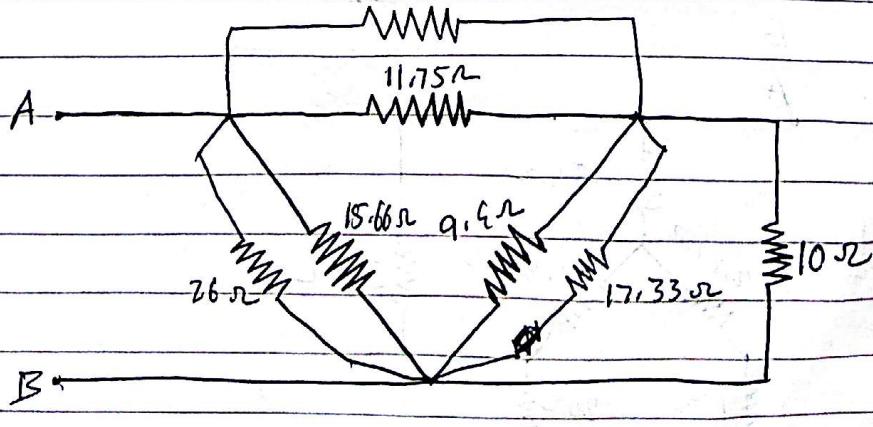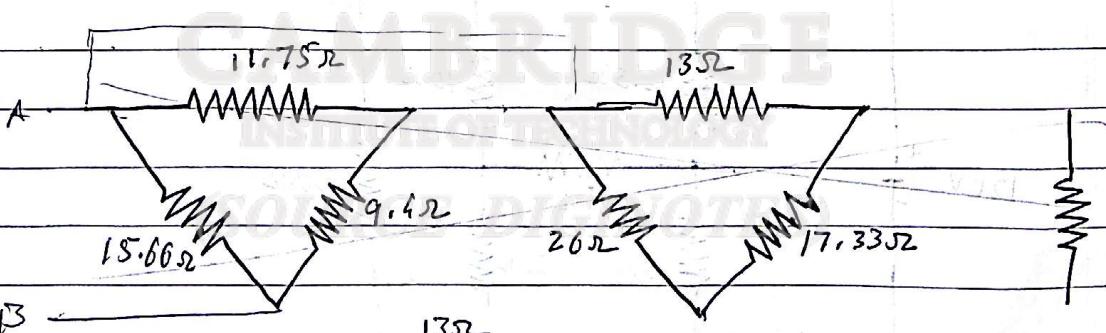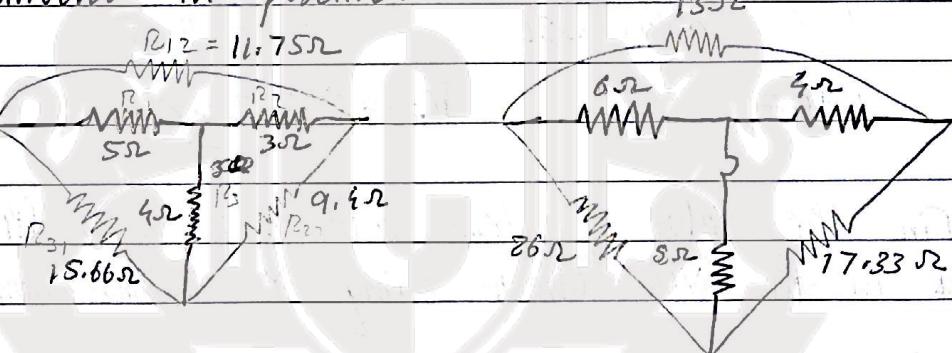Convert both the stars into equivalent delta which are connected in parallel -





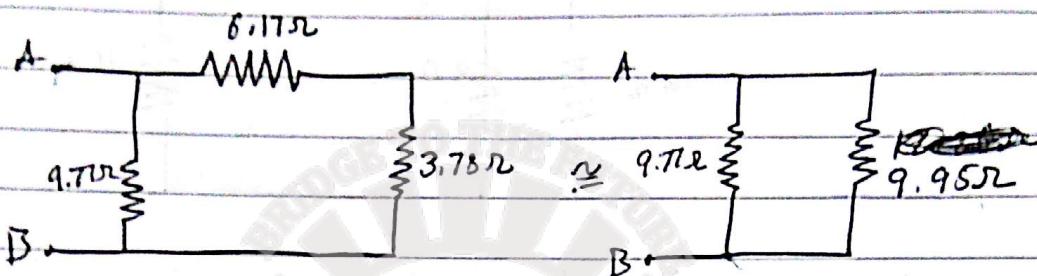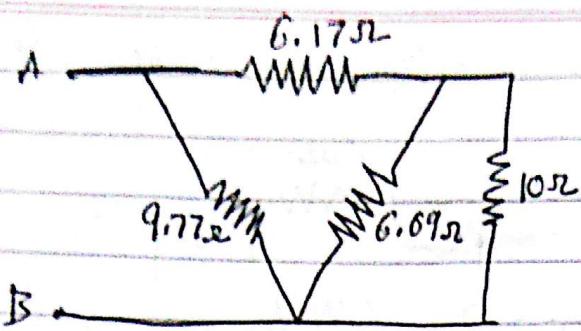


$$R_{AB} = \frac{9.77 \times 12.26}{9.77 + 12.26} \quad R_{AB} = \frac{9.77 \times 9.95}{9.77 + 9.95}$$

$$R_{AB} = \underline{\underline{9.9295\Omega}}$$

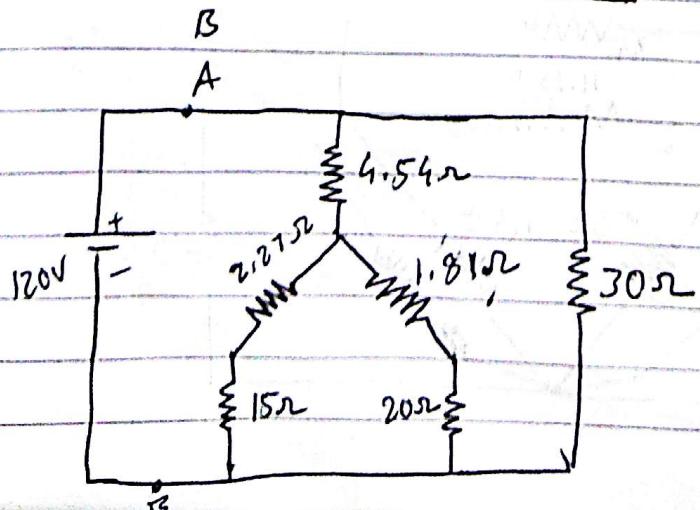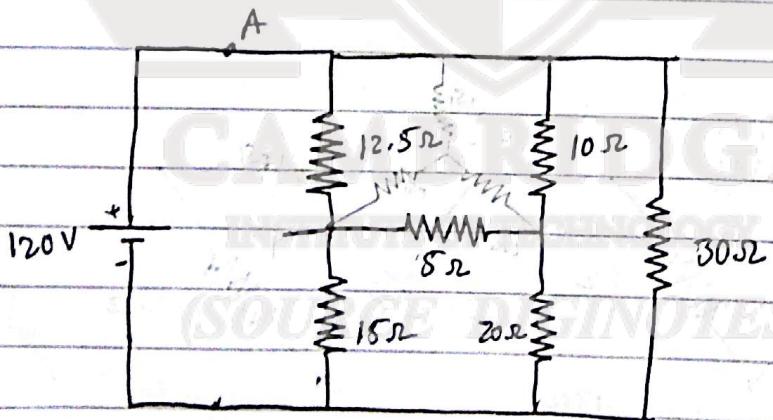Q. Find the value of R_{AB} and hence find the current I in the Δ shown using $Y-\Delta$ conversion technique.



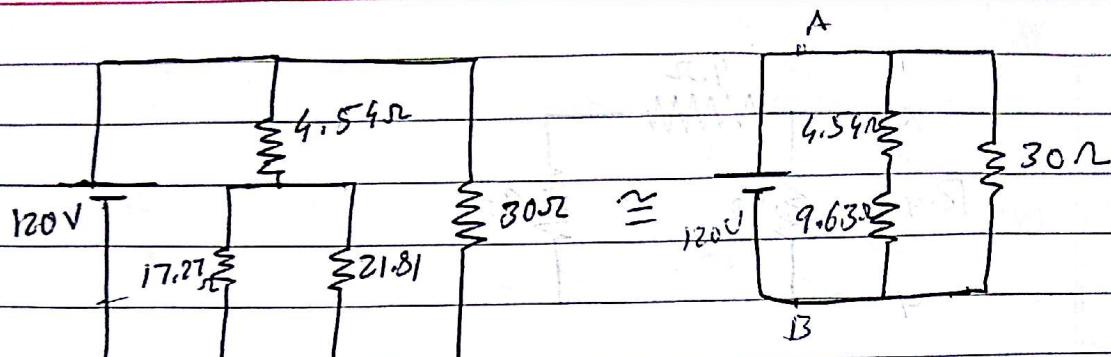



$$R_{AB} = 14.17 \parallel 30$$

$$R_{AB} = 9.62 \Omega \cancel{\parallel}$$

$$I = \frac{V}{R} = \frac{120}{9.62} = 12.47 \text{ A} \cancel{\parallel}$$

Q. Find the value of R_{xy} .

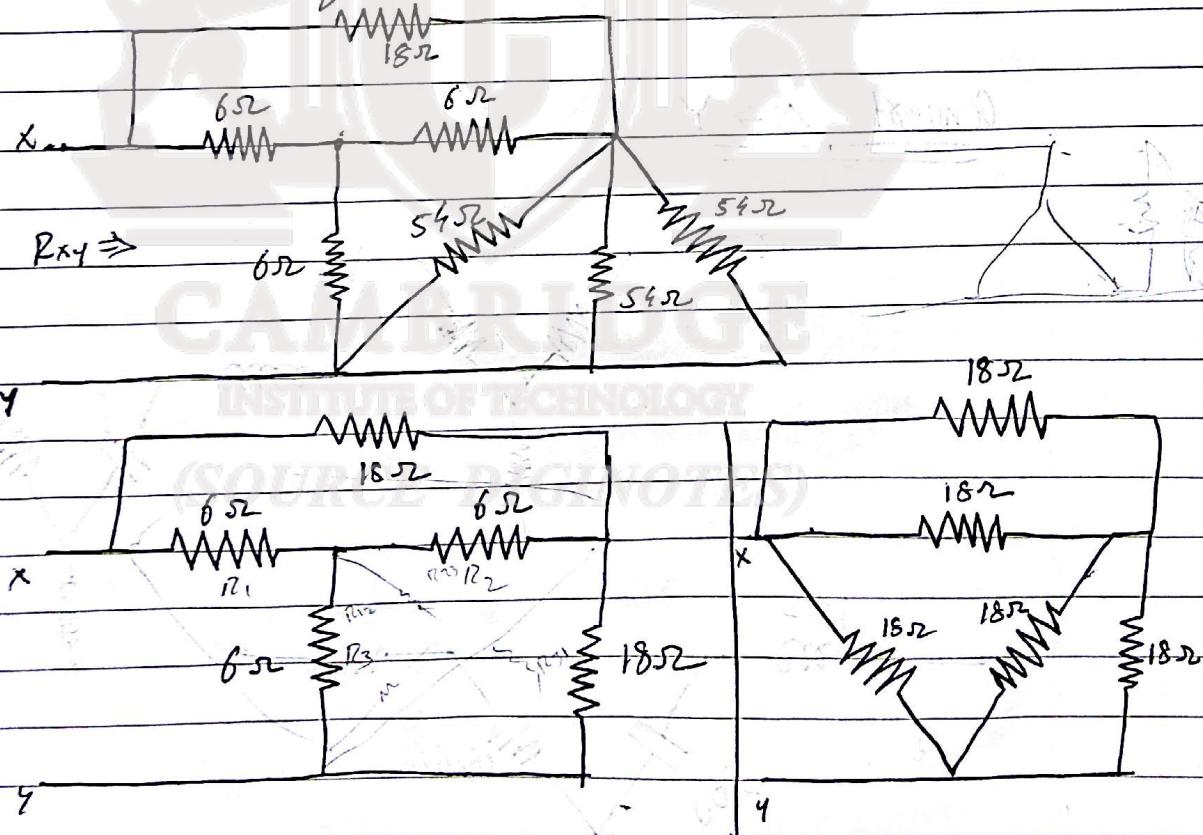


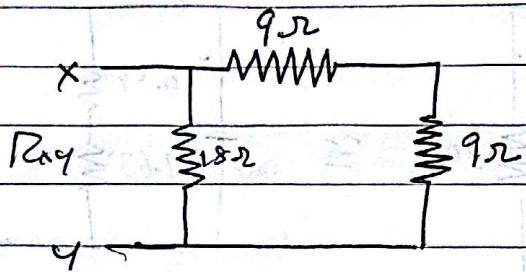


$$R_{xy} = 18\omega // 18\omega$$


$$R_{xy} = 9\omega //$$

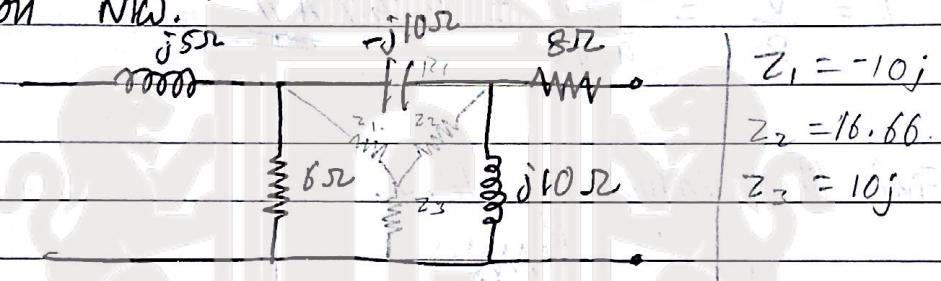Q. Convert the given N/w into single delta connection N/w.



Convert $\Delta \rightarrow Y$

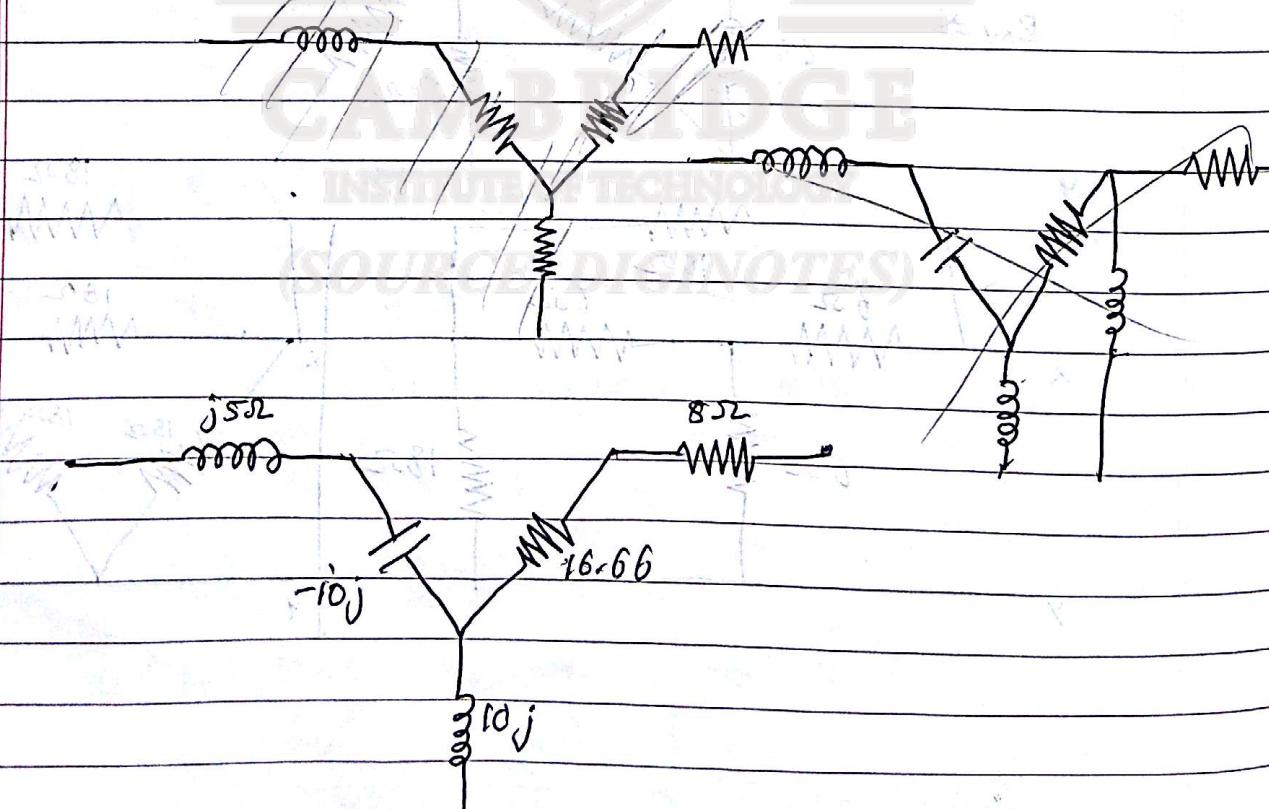

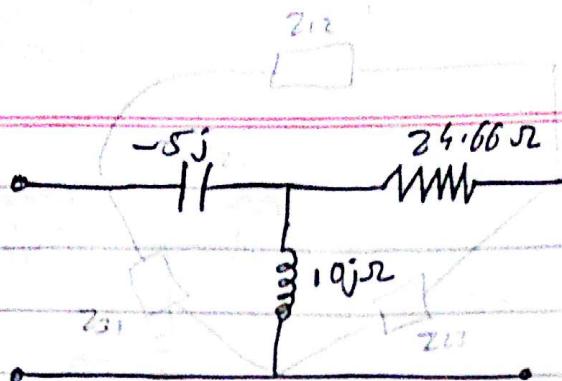


$$Z_{12} = 12.33 - 5j$$


$$Z_{23} = -24.66 + 10j$$


$$Z_{31} = \cancel{2.027}j \quad 2.027 + 5j$$

Convert $\gamma \rightarrow \Delta$:

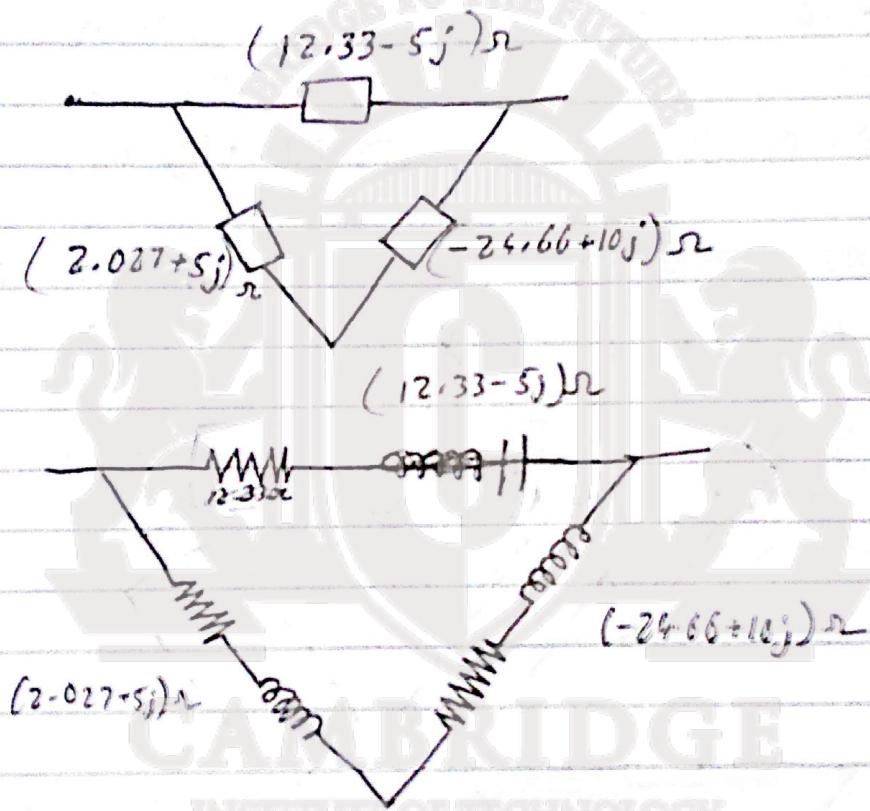

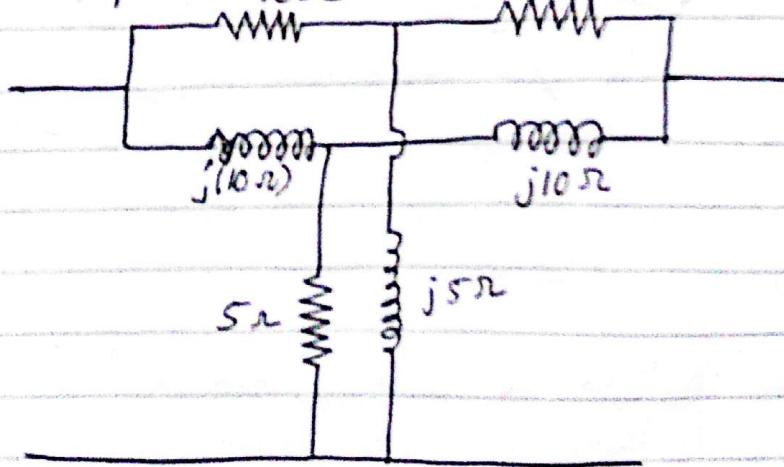* Q. Convert the given N/w info single Δ connected N/w.



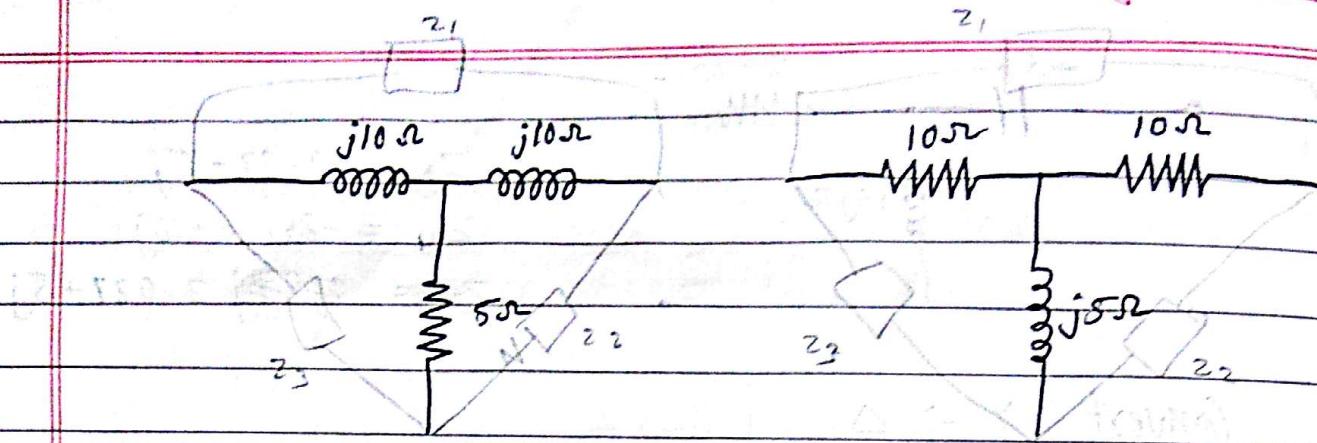

$$z_1 = -20 + 20j\omega\tau$$

$$z_2 = 10 + 10j\omega\tau$$


$$z_3 = 10 + 10j\omega\tau$$

$$z_1 = 20 - 20j\omega\tau$$

$$z_2 = 10 + 10j\omega\tau$$

$$z_3 = 10 + 10j\omega\tau$$

$$(20 - 20j)\Omega$$

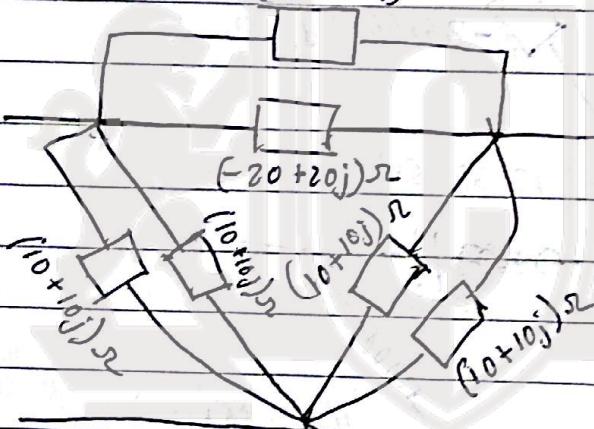


$$z_1 = (20 - 20j) \parallel (-20 + 20j)$$

$$z_1 = 0.$$


$$z_2 = 5 + 5j.$$

$$z_3 = 5 + 5j.$$

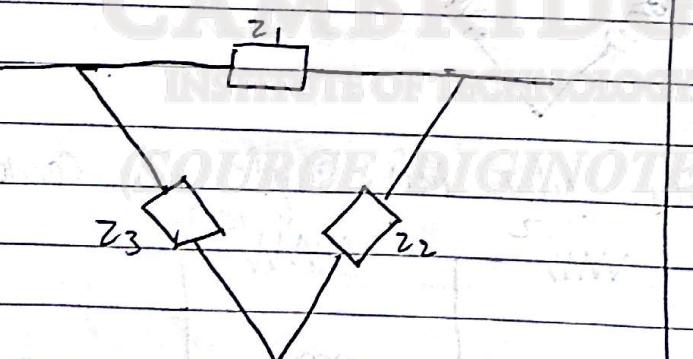

Loop or Mesh Analysis

Consider following circuit,

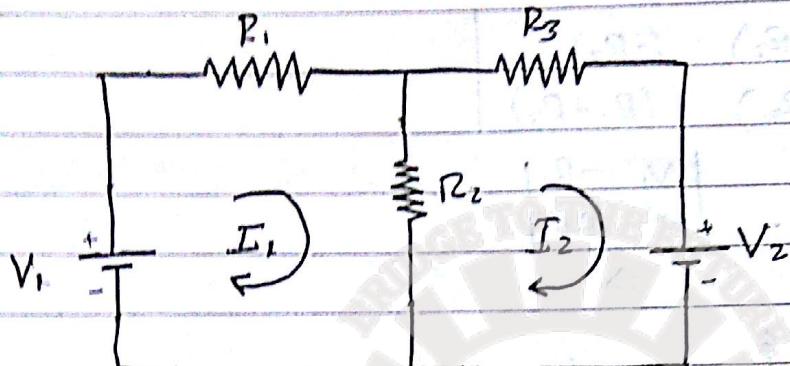

In the given N/W, there are two loops.

Name the loop currents as I_1, I_2 .

Assume the loop current directions in clockwise direction.

Now apply KVL to loop no. 1,

$$V_1 = I_1 R_1 + (I_1 - I_2) R_2 \cancel{\text{if}} \rightarrow \textcircled{1}$$

Now apply KVL to loop no. 2,

$$-V_2 = (I_2 - I_1) R_2 + I_2 R_3 \cancel{\text{if}} \rightarrow \textcircled{2}$$

$$[V] = [J][\gamma]$$

$$V_1 = I_1 (R_1 + R_2) - I_2 R_2$$

$$\begin{bmatrix} V_1 \\ -V_2 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \begin{bmatrix} R_1 + R_2 & -R_2 \\ -R_2 & R_2 + R_3 \end{bmatrix}$$

$$-V_2 = I_1 (R_2) + I_2 (R_2 + R_3)$$


In loop analysis, to find the loop currents, I_1 & I_2 , we have to apply Cramer's Rule. According to this rule,

$$\Delta = \begin{vmatrix} (R_1 + R_2) & (-R_2) \\ (-R_2) & (R_2 + R_3) \end{vmatrix}$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{\begin{vmatrix} V_1 & -R_2 \\ -V_2 & (R_2 + R_3) \end{vmatrix}}{\Delta}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{\begin{vmatrix} (R_1 + R_2) & V_1 \\ -R_2 & -V_2 \end{vmatrix}}{\Delta}$$

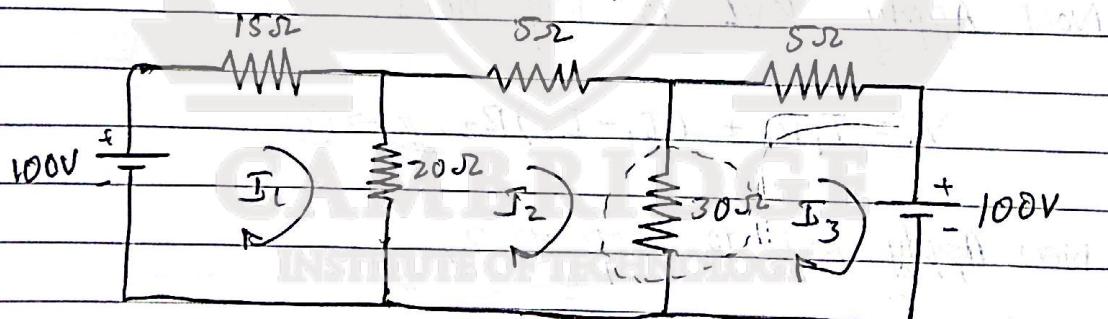Q. Find the current through 30Ω resistance in the network shown using loop analysis.



Assume three loop currents I_1, I_2 & I_3 in clockwise direction.

Apply KVL to Loop No: 1

$$100 = 15I_1 + 20(I_1 - I_2) + 0I_3$$

$$100 = I_1(15 + 20) - I_2(20) + 0I_3$$

$$100 = 35I_1 - 20I_2 + 0I_3 \rightarrow ①$$

Apply KVL to loop No. 2:

$$0 = 20(I_2 - I_1) + 5I_2 + (I_2 - I_3)30.$$

$$0 = I_2(20 + 5 + 30) - I_1(20) - I_3(30).$$

$$0 = -20I_1 + 55I_2 - 30I_3 \quad \underline{\underline{}} \rightarrow (2)$$

Apply KVL to loop No. 3:

$$-100 = I_3(30 + 5) - I_2(30) + 0I_1$$

$$-100 = 0I_1 - 30I_2 + 35I_3 \quad \underline{\underline{}} \rightarrow (3)$$

Now write all the 3 equation in matrix form.

$$[V] = [I][R]$$

$$\begin{bmatrix} 100 \\ 0 \\ -100 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} \begin{bmatrix} 35 & -20 & 0 \\ -20 & 55 & -30 \\ 0 & -30 & 35 \end{bmatrix}$$

Apply Cramer's Rule,

$$\Delta = \begin{vmatrix} 35 & -20 & 0 \\ -20 & 55 & -30 \\ 0 & -30 & 35 \end{vmatrix} = 35(55 \times 35 - 30 \times 30) + 20(-20 \times 35) + 0.$$

$$\Delta = 21875 \quad \underline{\underline{}}$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{100 \begin{vmatrix} -20 & 0 \\ 55 & -30 \end{vmatrix} + 20 \begin{vmatrix} 0 & 0 \\ -30 & 35 \end{vmatrix}}{21875}$$

$$I_1 = \frac{100(55 \times 35 - 30 \times 30) + 20(0 - 30 \times 100)}{21875} = \frac{42500}{21875} = 1.94 \quad \underline{\underline{}}$$

$$I_2 = \begin{vmatrix} 35 & 100 & 0 \\ -20 & 0 & -30 \\ 0 & -100 & 35 \end{vmatrix} = \frac{-35000}{21875} = -1.6 \text{ A}_{\text{A}}$$

21875

$$I_3 = \begin{vmatrix} 35 & -20 & 100 \\ -20 & 55 & 0 \\ 0 & -30 & -100 \end{vmatrix} = \frac{-92500}{21875} = -4.22 \text{ A}_{\text{A}}$$

21875


Current flowing through 3Ω resistance,

$$I_{30\Omega} = I_2 - I_3$$

$$I_{30\Omega} = -1.6 - (-4.22)$$

$$I_{30\Omega} = 2.62 \text{ A}_{\text{A}}$$

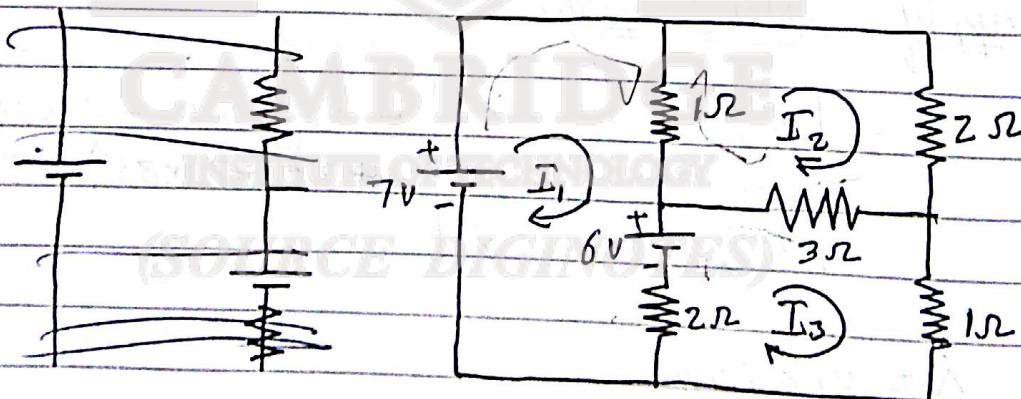- Q. Find all the loop currents using loop analysis for the N/W shown.



Apply KVL for loop-1:

$$3I_1 - I_2 - 2I_3 = 7 - 6$$

$$3I_1 - I_2 - 2I_3 = 1 \rightarrow \textcircled{1}$$

Apply KVL to loop-2:

$$-I_1 + 6I_2 - 3I_3 = 0 \cancel{\parallel} \rightarrow \textcircled{2}$$

Apply KVL to loop-3:

$$-2I_1 - 3I_2 + 6I_3 = 6 \cancel{\parallel} \rightarrow \textcircled{3}$$

$$[V] = [I][R]$$

$$\begin{bmatrix} 1 \\ 0 \\ -6 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} \begin{bmatrix} 3 & -1 & -2 \\ -1 & 6 & -3 \\ -2 & -3 & 6 \end{bmatrix}$$

Apply Cramer's Rule:


$$\Delta = \begin{vmatrix} 3 & -1 & -2 \\ -1 & 6 & -3 \\ -2 & -3 & 6 \end{vmatrix} = 39 \cancel{\parallel}$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{1 \begin{vmatrix} -1 & -2 \\ 6 & -3 \end{vmatrix}}{39} = \frac{117}{39} = 3A \cancel{\parallel}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{3 \begin{vmatrix} 1 & -2 \\ 0 & -3 \end{vmatrix}}{39} = \frac{78}{39} = 2A \cancel{\parallel}$$

$$I_3 = \frac{\Delta_3}{\Delta} = \frac{3 \begin{vmatrix} -1 & 1 \\ 6 & 0 \end{vmatrix}}{39} = \frac{117}{39} = 3A \cancel{\parallel}$$

Q. Find the loop currents.

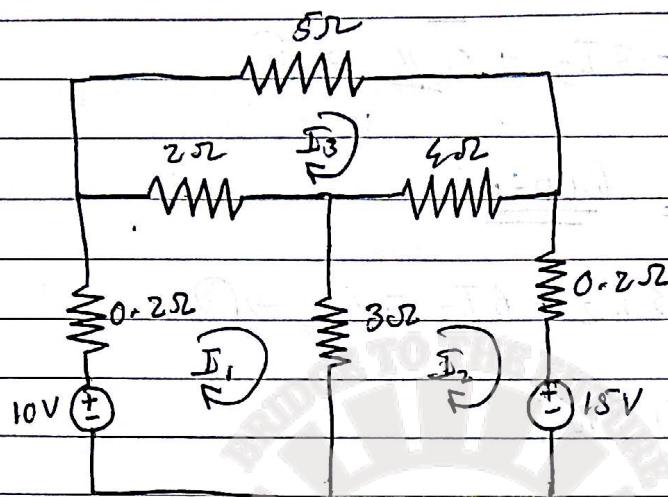

Apply KVL for loop-1:

$$5 \cdot 2 I_1 - 3 I_2 + 2 I_3 = 10 \quad \text{---} (1)$$

Apply KVL for loop-2:

$$-3 I_1 + 7 \cdot 2 I_2 - 4 I_3 = -15 \quad \text{---} (2)$$

Apply KVL for loop-3:

$$-2 I_1 - 4 I_2 + 11 I_3 = 0 \quad \text{---} (3)$$

[V] [I] [R]

$$\begin{bmatrix} 10 \\ -15 \\ 0 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} \begin{bmatrix} 5.2 & -3 & -2 \\ -3 & 7.2 & -4 \\ -2 & -4 & 11 \end{bmatrix}$$

Apply Cramer's Rule:


$$\Delta = \begin{vmatrix} 5, 2 & -3 & -2 \\ -3 & 7, 2 & -4 \\ -2 & -4 & 11 \end{vmatrix} = 152.84 \cancel{\text{A}}$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{1}{152.84} \begin{vmatrix} 10 & -3 & -2 \\ -15 & 7, 2 & -4 \\ 0 & -4 & 11 \end{vmatrix} = \frac{17}{152.84} = 0.111 \cancel{\text{A}}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{1}{152.84} \begin{vmatrix} 10 & 5, 2 & 10 & -2 \\ -3 & -15 & -4 & 11 \\ -2 & 0 & 11 & \end{vmatrix} = \frac{-388}{152.84} = -2.53 \cancel{\text{A}}$$


$$I_3 = \frac{\Delta_3}{\Delta} = \frac{1}{152.84} \begin{vmatrix} 5, 2 & -3 & 10 \\ -3 & 7, 2 & -15 \\ -2 & -4 & 0 \end{vmatrix} = \frac{-138}{152.84} = -0.902 \cancel{\text{A}}$$

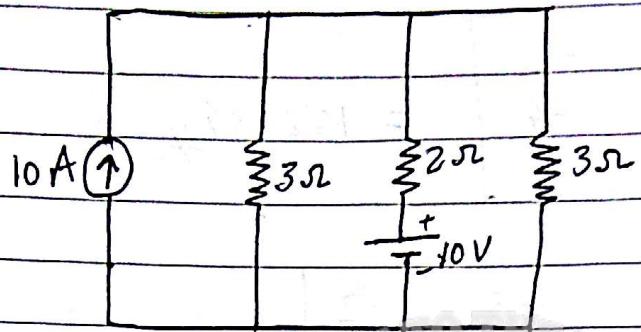Q- Find the mesh currents in the given ckt.



Apply $I \rightarrow V$:

$$V = IR = 30V$$

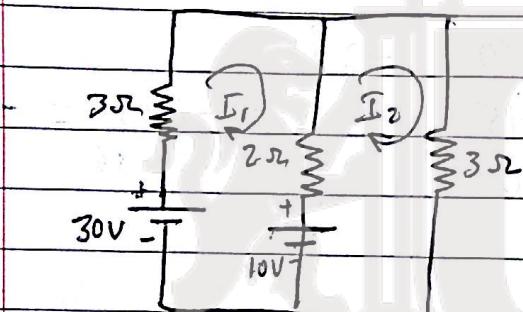

Apply $ICVL$ to loop-1:

~~$5I_1 - 2I_2 = 20V$~~ → ①

Apply $ICVL$ to loop-2:

$$-2I_1 + 5I_2 = 10V$$
 → ②

$$[V] = [I] [R]$$

$$\begin{bmatrix} 20 \\ 10 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \begin{bmatrix} 5 & -2 \\ -2 & 5 \end{bmatrix}$$

Apply Cramer's Rule)

0.11

-2.53


-0.9

$$\Delta = \begin{vmatrix} 5 & -2 \\ -2 & 5 \end{vmatrix} = 25 - 4 = 21$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{\begin{vmatrix} 20 & -2 \\ 10 & 5 \end{vmatrix}}{21} = \frac{100 + 20}{21} = 5.714 A$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{\begin{vmatrix} 5 & 20 \\ -2 & 10 \end{vmatrix}}{21} = \frac{50 + 40}{21} = 4.285 A$$

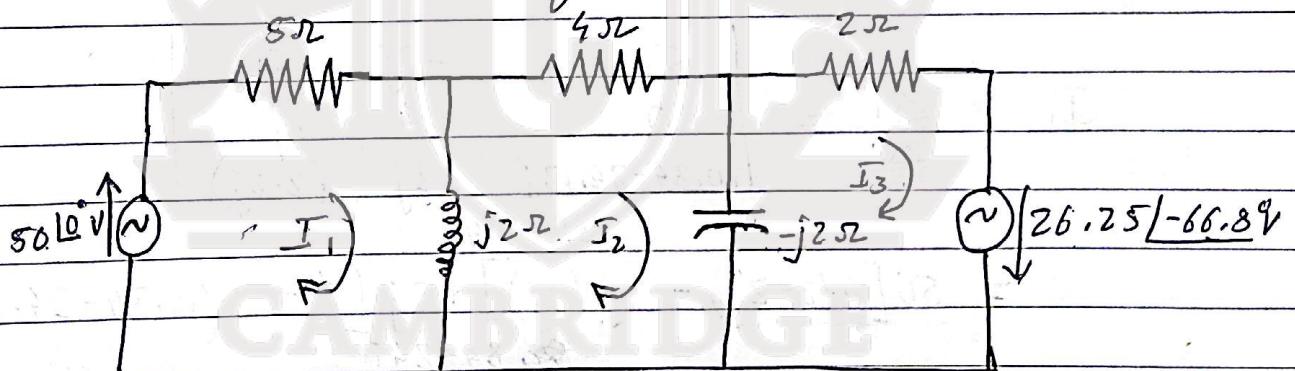Q. Find the current through 4Ω resistance in the NFA shown using loop analysis.



Apply KVL to loop-1:

$$50\angle 10^\circ = (5 + j2) I_1 - j2 I_2 + 0 I_3 \rightarrow ①$$

KVL to loop-2:

$$0 = -j2 I_1 + (4 + j2) I_2 - (4 + j2 - j2) I_2 - (-j2) I_3$$

$$0 = -j2 I_1 + 4 I_2 + j2 I_3 \rightarrow ②$$

KVL to loop-3:

$$26.25 \angle -66.8^\circ V = 0 I_1 + 2j I_2 + (2 - 2j) I_3 = 0 \rightarrow ③$$

$$(10.3409 - 24.12j)$$

$$[V] = [I] [R]$$

$$\begin{bmatrix} 50 & 0 \\ 0 & 10.34 - 24.12j \end{bmatrix}^2 \begin{bmatrix} I_1 \\ I_3 \end{bmatrix} = \begin{bmatrix} 5+2j & -2j & 0 \\ -2j & 4 & 2j \\ 0 & 2j & (2-2j) \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 5+2j & -2j & 0 \\ -2j & 4 & 2j \\ 0 & 2j & (2-2j) \end{vmatrix}$$

$$\Delta = (5+2j) [4(2-2j) - (2j)(2j)] + 2j [-2j(2-2j) - 0] + 0.$$

$$\Delta = 84 - 24j.$$

$$\Delta = 87.36 (-15.96)$$

$$I_1 = \frac{\Delta_1}{\Delta} = \begin{bmatrix} 50 & -2j & 0 \\ 0 & 4 & 2j \\ 10.34 - 24.12j & 2j & (2-2j) \end{bmatrix} \cdot \frac{1}{84 - 24j}$$

$$= \frac{50 [4(2-2j) - (2j)(2j)] + 2j [0 - 2j(10.34 - 24.12j)]}{84 - 24j}$$

$$= \frac{691.36 - 496.48j}{84 - 24j}$$

$$= 8.62 - 3.44j \text{ A}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \begin{bmatrix} 5+2j & 50 & 0 \\ -2j & 0 & 2j \\ 0 & 10.34 - 24.12j & (2-2j) \end{bmatrix} \cdot \frac{1}{84 - 24j}$$

$$\overline{I_2} = \frac{(5+2j)[0 - 2j(10.34 - 24.12j)] - 50[-2j(2-2j)]}{84-24j}$$

$$\overline{I_2} = \frac{0.16 + 0.12j}{84-24j}$$


$$I_2 = 1.383 \times 10^{-3} + 1.823 \times 10^{-3}j \text{ A}_{\text{H}}$$

$$I_2 = 2.289 \times 10^{-3} \angle 52.81^\circ \text{ A}_{\text{H}}$$

$$I_2 = 0.00228 \text{ A} \approx 0 \text{ A}_{\text{H}}$$

I_2 = current through 4Ω resistance.

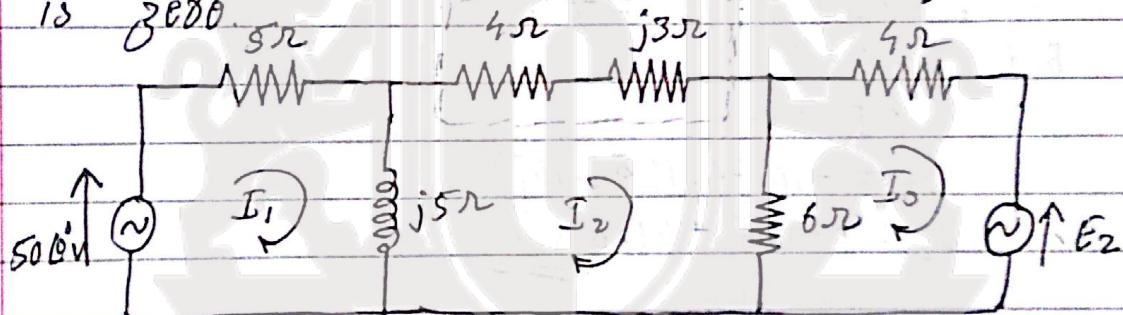*Q. Find the value of the voltage source, $V_2(E)$ in the NW shown such that current through $(4+j3)\Omega$ is zero.



According to the given data, current flowing through $(4+j3)\Omega$ is zero.

$$\therefore I_2 = 0$$

Apply KVL to loop 1,

$$(5+5j)I_1 - 5jI_2 + 0I_3 = 50 + 0j$$

~~$$\text{But } I_2 = 0, (5+5j)I_1 = 50 + 0j$$~~

~~Apply KCL to loop 2;~~

$$\text{But } I_2 = 0, (5+5j)I_1 = 50$$

$$I_1 = \frac{50}{5+5j} = 5-5j \text{ A}_{\text{H}}$$

Apply KVL to loop -2,

$$-j5(\Delta_1) + (10+j8) I_2 - 6 I_3 = 0$$

But $I_2 = 0$,

$$\Rightarrow -j5(\Delta_1) - 6 I_3 = 0 \quad \cancel{\text{if}} \rightarrow ① -$$

$$-6 I_3 = +j8(\Delta_1)$$

$$-6 I_3 = +j5(5-5j)$$

$$-6 I_3 = +25-25j$$

$$I_3 = -4.16 + 4.16j \quad \cancel{\text{if}}$$

Apply KVL to loop -3,

$$10 I_3 - 6 I_2 + 0 \Delta_1 = -E_2$$

But $I_2 = 0$


$$10 I_3 = -E_2$$

$$E_2 = -10(-4.16 + 4.16j)$$

$$E_2 = +41.6 + 41.6j \quad \cancel{\text{if}}$$

$$E_2 = 58.83 \angle 45^\circ V \quad \cancel{\text{if}}$$

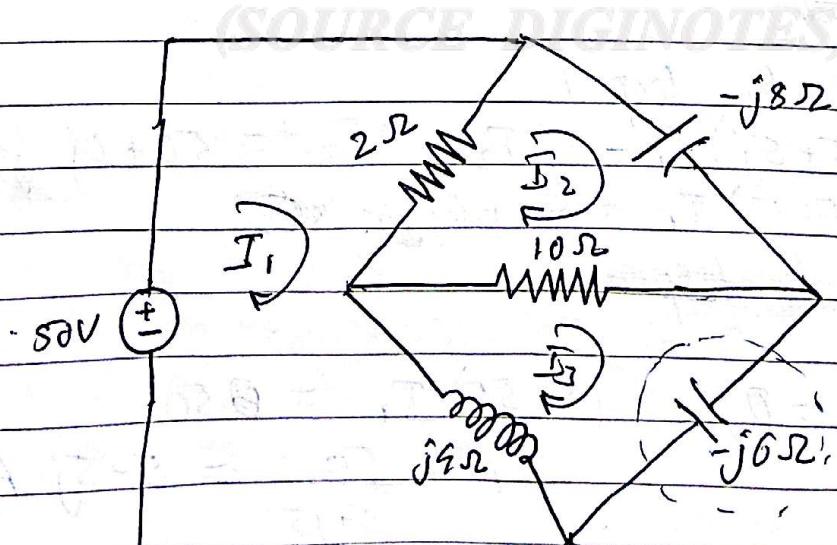Q. Find the current through $-j6\Omega$ in the net shown.



Apply KVL to loop-1:

$$(2+j4)I_1 - 2I_2 - j4(I_3) = 50 \cancel{\parallel} \rightarrow ①.$$

Apply KVL to loop-2:

$$-2I_1 + (12-j8)I_2 - 10I_3 = 0 \cancel{\parallel} \rightarrow ②.$$

Apply KVL to loop-3:

$$-j4I_1 - 10I_2 + (10-j2)I_3 = 0 \cancel{\parallel} \rightarrow ③.$$

$$[V] = [J][R]$$

$$\begin{bmatrix} 50 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} \begin{bmatrix} 2+j4 & -2 & -j4 \\ -2 & (12-j8) & -10 \\ -j4 & -10 & (10-j2) \end{bmatrix}$$

Current through $-j6\Omega$ is I_3 .

\therefore To find I_3 ,

$$\Delta = \begin{vmatrix} 2+j4 & -2 & -j4 \\ -2 & (12-j8) & -10 \\ -j4 & -10 & (10-j2) \end{vmatrix} \cancel{\parallel}$$

$$\Delta = (2+j4) \cancel{(②+③)} \rightarrow [(12-j8)(10-j2) - 100]$$

$$+ 2[-2(10-j2) - 10(j4)] - j4[20 + (j4)(12-j8)]$$

$$\Delta = (424 - 192j) + (-40 - 72j) + (192 - 208j)$$

$$\Delta = 576 - 672j \cancel{\parallel}$$

~~754~~

$$I_3 = \frac{\Delta_3}{\Delta} = \begin{vmatrix} 2+j4 & -2 & 50 \\ -2 & (12-j8) & 0 \\ -j4 & -10 & 0 \end{vmatrix} / 876 - 472j$$

$$= \frac{50(+20+4j(12-8j)) - (0+0j)}{876-472j}$$


$$= \frac{2600+2400j}{876-472j}$$

$$I_3 = 0.6878 + 4.7057j \text{ A}$$

$$I_3 = 4.78 \angle 82.04^\circ \text{ A}$$

Super-Mesh Analysis:

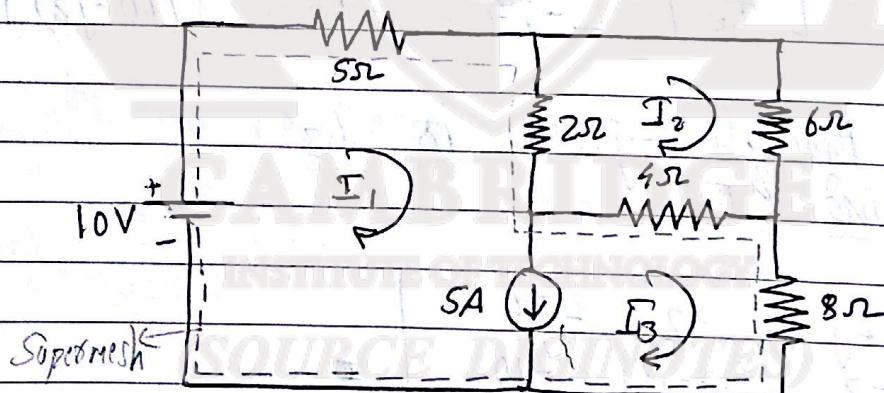1. Using mesh analysis find the values of loop currents in the N/W shown.



Super mesh concept appears when there is a ideal current source in btw any two loops.

In the given N/W, there is a ideal current source 5A btw loop 1 & loop 3.

$$\therefore I_1 - I_3 = 5A \quad \text{①}$$

∴ loops 1 and 3 becomes supermesh.

Apply KVL to Supermesh:

$$6I_1 - 2\bar{I}_2 + 12I_3 - 4\bar{I}_3 = 10$$

$$7I_1 - 6\bar{I}_2 + 12\bar{I}_3 = 10 \quad \text{---} (2)$$

Apply KVL to loop-2:

$$-2\bar{I}_1 + 12\bar{I}_2 - 4\bar{I}_3 = 0 \quad \text{---} (3)$$

$$[V] = [I][R]$$

$$\begin{bmatrix} S \\ 10 \\ 0 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} \begin{bmatrix} 1 & 0 & -1 \\ 7 & -6 & 12 \\ -2 & 12 & -4 \end{bmatrix}$$

Apply Cramer's Rule:


$$\Delta = \begin{vmatrix} 1 & 0 & -1 \\ 7 & -6 & 12 \\ -2 & 12 & -4 \end{vmatrix} = -192$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{\begin{vmatrix} 5 & 0 & -1 \\ 10 & -6 & 12 \\ 0 & 12 & -4 \end{vmatrix}}{-192} = \frac{-720}{-192} = 3.75 A$$

$$\bar{I}_2 = \frac{\Delta_2}{\Delta} = \frac{\begin{vmatrix} 1 & 5 & -1 \\ 7 & 10 & 12 \\ -2 & 0 & -4 \end{vmatrix}}{-192} = \frac{-40}{-192} = 0.2083 A$$

$$\bar{I}_3 = \frac{\Delta_3}{\Delta} = \frac{\begin{vmatrix} 1 & 0 & 5 \\ 7 & -6 & 10 \\ -2 & 12 & 0 \end{vmatrix}}{-192} = \frac{240}{-192} = -1.25 A$$

Q. Find the loop currents.

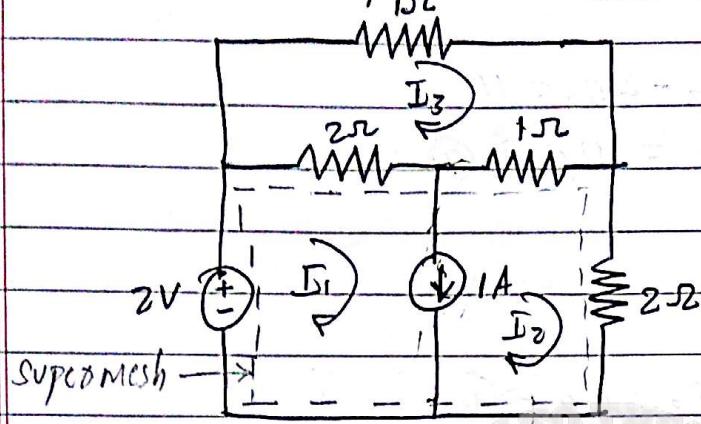

This problem is under supermesh concept because there is a ideal current source IA b/w the loops 1 & 2.

$$\therefore I_1 - I_2 = IA \rightarrow \textcircled{1}$$

Apply KVL to supermesh,

$$2I_1 + 3I_2 - 3I_3 = 2 \rightarrow \textcircled{2}$$

Apply KVL to loop-3,

$$-2I_1 - I_2 + 4I_3 = 0 \rightarrow \textcircled{3}$$

$$[V] = [I][B]$$

$$\begin{bmatrix} 1 \\ 2 \\ 0 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} \begin{bmatrix} 1 & -1 & 0 \\ 2 & 3 & -3 \\ -2 & -1 & 4 \end{bmatrix}_{3 \times 3}$$

Apply Cramer's Rule,


$$\Delta = \begin{vmatrix} 1 & -1 & 0 \\ 2 & 3 & -3 \\ -2 & -1 & 4 \end{vmatrix} = \cancel{111}$$

$$I_1 = \frac{\Delta_1}{\Delta} = \begin{vmatrix} 1 & -1 & 0 \\ 2 & 3 & -3 \\ 0 & -1 & 4 \end{vmatrix} = \frac{17}{11} = 1.54 A \cancel{\text{II}}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \begin{vmatrix} 1 & 1 & 0 \\ 2 & 2 & -3 \\ -2 & 0 & 4 \end{vmatrix} = \frac{6}{11} = 0.5454 A \cancel{\text{II}}$$

$$I_3 = \frac{\Delta_3}{\Delta} = \begin{vmatrix} 1 & -1 & 1 \\ 2 & 3 & 2 \\ -2 & -1 & 0 \end{vmatrix} = \frac{10}{11} = 0.909 A \cancel{\text{II}}$$

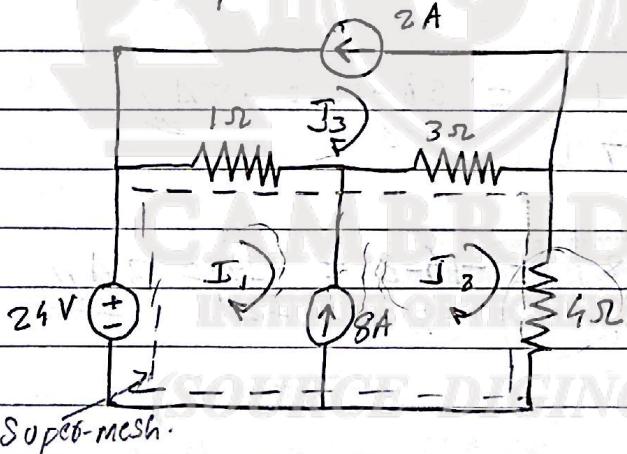Q. Find the power in 4Ω resistance in the NW shown.



There is an ideal current source 8A flowing loops 1 & 2.
 $\therefore -I_1 + I_2 = 8 \cancel{\text{A}} \rightarrow \textcircled{1}$

2A current source is at the perimeter (boundary) of the NW,

$$\therefore 0 - I_3 = 2A$$

$$I_3 = -2A \cancel{\text{A}}$$

Apply KVL for super-mesh.

$$I_1 + 7I_2 - 4I_3 = 24$$

$$I_1 + 7I_2 - 4(-2) = 24$$

$$I_1 + 7I_2 = 24 + 8$$

$$I_1 + 7I_2 = 16 \quad \text{---} (2)$$

$$[V] = [I][R]$$

$$\begin{bmatrix} 8 \\ 16 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \begin{bmatrix} -1 & 1 \\ 1 & 7 \end{bmatrix}$$

Applying Cramer's Rule,

$$\Delta = \begin{vmatrix} -1 & 1 \\ 1 & 7 \end{vmatrix} = -7 - 1 = -8$$

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{\begin{vmatrix} 8 & 1 \\ 16 & 7 \end{vmatrix}}{-8} = \frac{56 - 16}{-8} = -5A$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{\begin{vmatrix} -1 & 8 \\ 1 & 16 \end{vmatrix}}{-8} = \frac{-16 - 8}{-8} = +24 = 3A$$

$$I_3 = -2A$$

Now, power in ϵ_{SR} resistance,

$$P_{\epsilon SR} = I^2 R$$


$$P_{\epsilon SR} = I_2^2 \times 4$$

$$P_{\epsilon SR} = (3)^2 \times 4$$

$$P_{\epsilon SR} = 9 \times 4$$

$$P_{\epsilon SR} = 36 \text{ Watts}$$

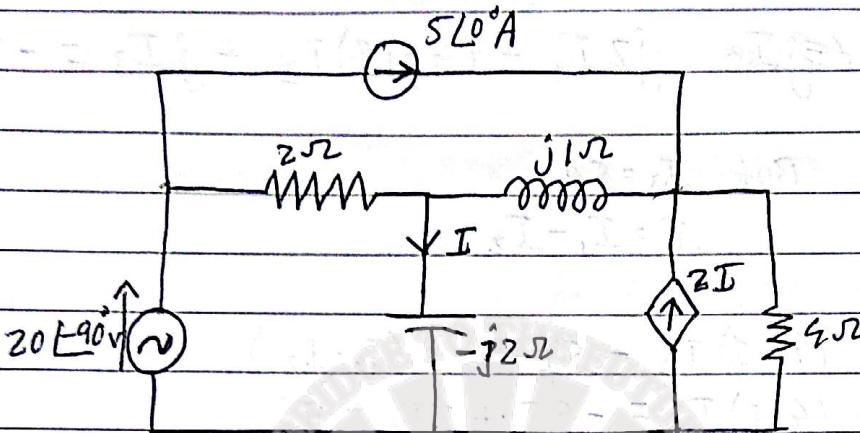Q. Find the value of current I in the N/C shown.




Convert current source into voltage source.

$$V = 5I_2$$

$$V = 2I \times 5$$

$$V = 8I V_{II}$$

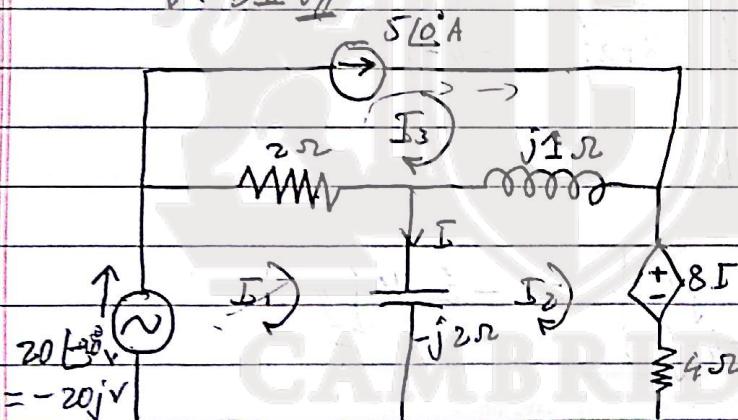

There is an ideal current source here.

There is a $5\angle 0^\circ$ current at the perimeter of the N/C.

$$0 + I_3 = 5\angle 0^\circ$$

$$I_3 = 5\angle 0^\circ$$

$$I_3 = 5A$$

Apply KVL to loop no. 1

$$(2 - 2j)I_1 + j2I_2 - 2I_3 = 20\angle 90^\circ$$

$$(2 - j2)I_1 + j2I_2 - 10 = -20j$$

$$(2 - j2)I_1 + j2I_2 = 10 + 20j \rightarrow \text{D}$$

Apply LCV to loop no. 2.

$$\cancel{j_2 I_1 + j_3} \quad j_2 I_1 + (4-j_1) I_2 - j_3 I_3 = -8 I$$

$$\text{But } I_3 = 5A$$

$$I = I_1 - I_2$$

$$j_2 I_1 + (4-j_1) I_2 - 5j = -8(I_1 - I_2)$$

$$j_2 I_1 + (4-j) I_2 = -8 I_1 + 8 I_2 + 5j$$

$$(8+8j) I_1 + (-4-j) I_2 = 5j \rightarrow ②$$

$$[V] = [S][R]$$

$$\begin{vmatrix} 10-20j \\ 8j \end{vmatrix} = \begin{vmatrix} I_1 & 2-2j & j_2 \\ I_2 & 8+2j & -4-j \end{vmatrix}$$

Apply Crammer's Rule,

$$\Delta = \begin{vmatrix} 2-2j & j_2 \\ 8+2j & -4-j \end{vmatrix} = -6-10j$$

$$I_1 = \frac{\Delta_1}{\Delta} = \begin{vmatrix} 10-20j & j_2 \\ 8j & -4-j \end{vmatrix} = -50+70j$$

$$I_1 = -2.9411 - 6.7647j$$

$$I_1 = 7.3763 \angle -113.49^\circ$$

$$I_2 = \frac{\Delta_2}{\Delta} = \begin{vmatrix} 2-2j & 10-20j \\ 8+2j & 5j \end{vmatrix} = -110+150j$$

$$I_2 = -6.176 - 14.705j A$$

$$I_2 = 15.98 \angle -112.78^\circ A$$

$$\underline{I} = I_1 - I_2$$


$$\underline{I} = -2.9411 - 6.764j - (-6.176 - 14.705j)$$

$$\underline{I} = 3.2349 + 7.941j \cancel{A}$$

(Q8)

$$\underline{I} = 8.574 \angle 67.83^\circ \cancel{A}$$

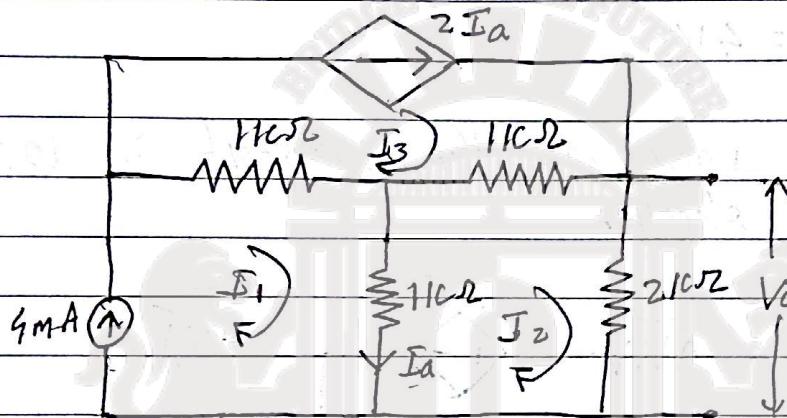- a. Find the value of V_o in the NW shown.



$4mA$ is at the perimeter.

$$\therefore I_1 = 4mA \cancel{A}$$

III, $2I_a$ current source is at the perimeter of loop 3.

$$\therefore I_3 = 2I_a \cancel{A}$$

~~$I_3 = 2I_a$~~ But $I_a = I_1 - I_2$

$$I_3 = 2(I_1 - I_2)$$

$$I_3 = 2I_1 - 2I_2 \cancel{A}$$

$$I_3 =$$

Apply KVL to loop no-2:

~~$-1kI_1 + 4kI_2 - 1kI_3 = 0$~~

$$-1k \times 4m + 4kI_2 - 1k(2I_1 - 2I_2) = 0$$

$$-4 + 4kI_2 - 2kI_1 + 2kI_2 = 0$$

$$-4 + 6kI_2 - 2k \times 4m = 0 \Rightarrow$$

$$6k\bar{I}_2 = 4 \div 3$$

$$6k\bar{I}_2 = 12$$

$$\bar{I}_2 = 2mA_{II}$$


Voltage across V_0 is given by,

$$V_0 = \bar{I}_2 \times R_{222}$$

$$V_0 = 2m \times 2k$$

$$V_0 = 4V_{II}$$

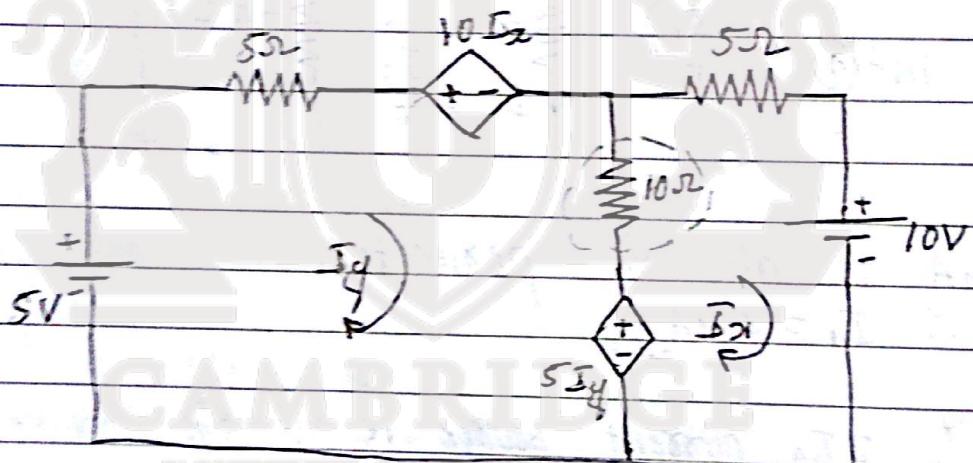- Q- Find the value of the current in 10Ω in the NW shown.



Apply KVL to loop no-1:

$$\bar{I}_y(5+10) - \bar{I}_x(10) = 5 - 10\bar{I}_x - 5\bar{I}_y$$

$$15\bar{I}_y - 10\bar{I}_x = 5 - 10\bar{I}_x - 5\bar{I}_y$$

$$20\bar{I}_y = 5$$

$$\bar{I}_y = \frac{5}{20} = \frac{1}{4}$$

$$\bar{I}_y = 0.25A_{II}$$

Apply $10VU$ to loop No - 2:

$$15I_{2L} - 10I_y = -10 + 5I_y$$

$$15I_{2L} - 15I_y = -10$$

$$15I_{2L} = -10 + 15(0.25)$$

$$15I_{2L} = -10 + 3.75$$


$$15I_{2L} = -6.25$$

$$I_{2L} = -0.416 A \cancel{\parallel}$$

Current in 10Ω resistance is,

$$\begin{aligned} I_{10\Omega} &= I_y - I_{2L} \\ &= 0.25 - (-0.416) \\ &= 0.666 A \cancel{\parallel} \end{aligned}$$

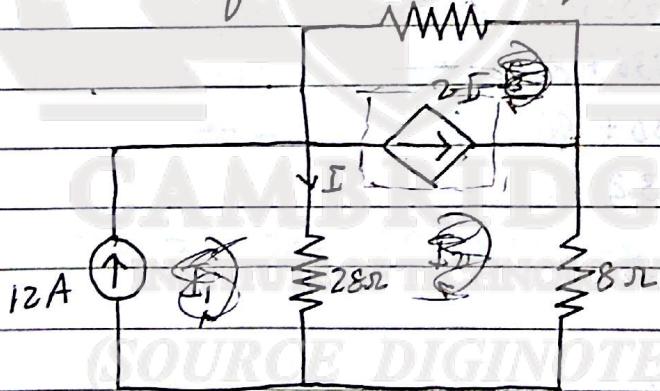Q. Find the value of the dependent source in the given N/w using mesh analysis.



$$I_1 = 12A \cancel{\parallel}$$

Apply $I \rightarrow V$.


Apply $10VU$ to loop - 2.

$$V = IR = 2I \times 4$$

$$V = 8I \cancel{\parallel}$$

* 12A is ~~at~~ at the perimeter.

$$I_1 = 12A \cancel{\parallel}$$

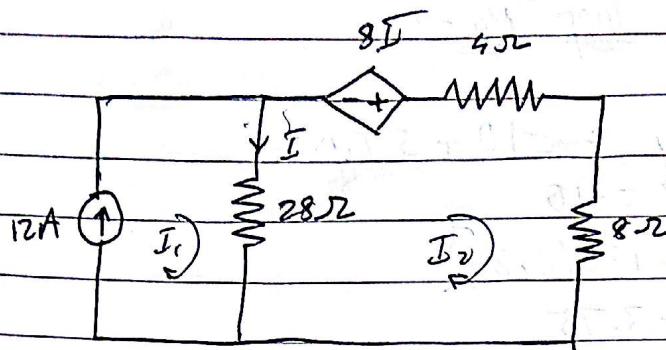

Apply KVL to loop-2

$$-28I_1 + 40I_2 = +8I \quad \text{---} \quad (1)$$

$$-28(I_2) + 40I_2 = 8I$$

$$-38I_2 + 40I_2 = 8I$$

$$\text{But } I = I_1 - I_2$$

$$+40I_2 = 38I_2 + 8(I_1 - I_2)$$

$$40I_2 = 38I_2 + 8I_1 - 8I_2$$

$$8I_2 + 40I_2 = 38I_2 + 8(I_2) \quad \text{---} \quad (2)$$

$$48I_2 = 336 + 96$$

$$48I_2 = 432$$

$$I_2 = 9A \quad \text{---} \quad (3)$$

$$I = I_1 - I_2$$

$$I = 12 - 9$$

$$I = 3A \quad \text{---} \quad (4)$$


Dependent source, $2I = 6A \quad \text{---} \quad (5)$

- Q. For the following mesh equations construct the circuit diagram.

$$11I_1 - 5I_2 = 50$$

$$-5I_1 + 27I_2 - 4I_3 = 0.$$

$$-4I_2 + 8I_3 = 0.$$

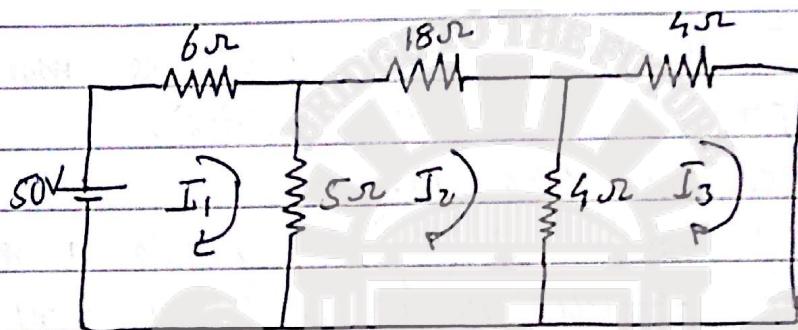


- Q. For the following matrix arrangement, in loop analysis, construct the circuit.


$$\begin{bmatrix} 5+j5 & -j5 & 0 \\ -j5 & 8+j8 & -6 \\ 0 & -6 & 10 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 30\text{ }10^\circ \\ 0 \\ -20\text{ }10^\circ \end{bmatrix}$$

The loop equations are;

$$(5+j5)I_1 - j5I_2 = 30\text{ }10^\circ$$


$$(-j5)I_1 + (8+j8)I_2 - 6I_3 = 0.$$
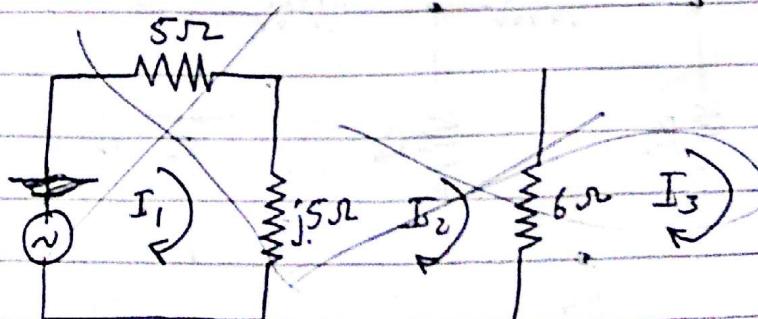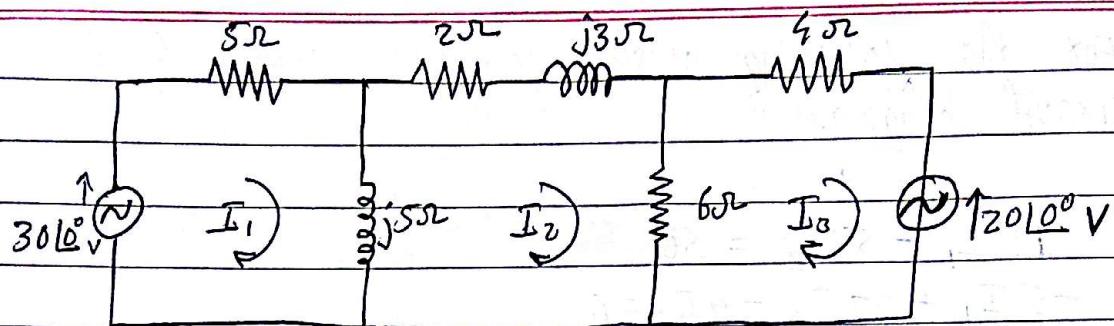
$$0I_1 - 6I_2 + 10I_3 = -20\text{ }10^\circ$$




Node Analysis:

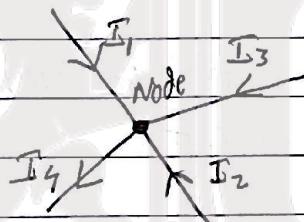
- If two or more branches meeting at a common point is called node (junction).
- KCL is applied for node analysis.
- According to KCL, total current entering into a node is equal to total sum of current leaving away from the node.



According to KCL,

$$I_1 + I_2 + I_3 = I_4$$

- Consider the following circuit.

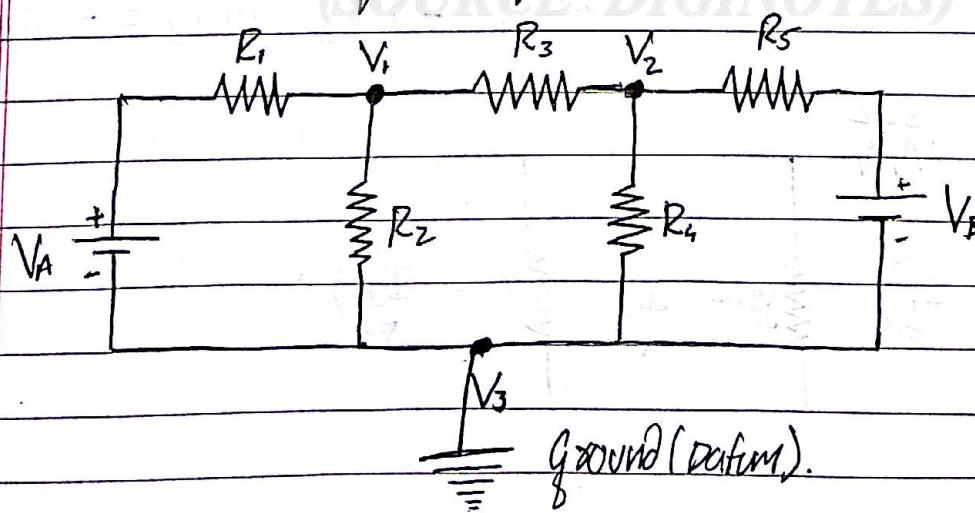

Apply KCL to node V_1 :

$$V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - V_2 = \frac{V_A}{R_1} \quad \# \rightarrow \textcircled{1}$$

Apply KCL to node-2 (V_2):

$$V_2 \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right) - \frac{V_1}{R_3} = \frac{V_B}{R_5}$$

$$-V_1 \left(\frac{1}{R_3} \right) + V_2 \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right) = \frac{V_B}{R_5} \quad \# \rightarrow \textcircled{2}$$


Represent eqn. $\textcircled{1}$ & $\textcircled{2}$ in matrix form,

$$\begin{bmatrix} \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} & -\frac{1}{R_3} \\ -\frac{1}{R_3} & \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} V_A/R_1 \\ V_B/R_5 \end{bmatrix}$$

Note:

In node analysis, no. of equations are 1 less than no. of equations in loop analysis.

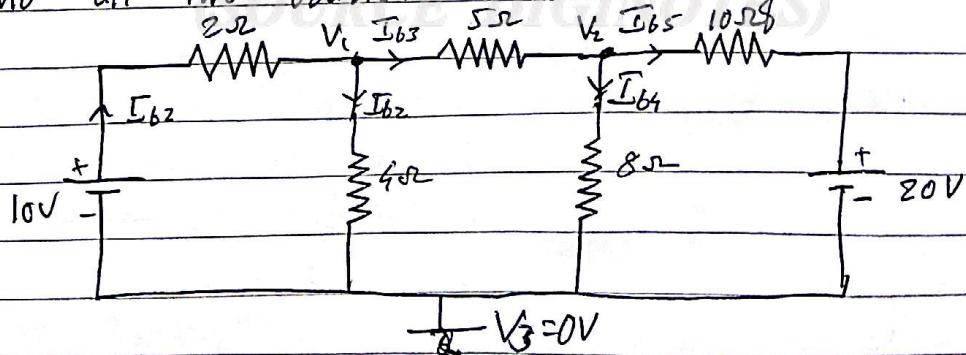Q. Find all the branch currents using ~~loop~~ node analysis.



$$V_1 \left(\frac{1}{2} + \frac{1}{5} + \frac{1}{4} \right) = \frac{V_2}{5} = 5$$

$$V_1 (0.5 + 0.25 + 0.2) - V_2 (0.2) = 5$$

$$V_1 (0.95) - V_2 (0.2) = 5 \quad \# \rightarrow \textcircled{1}$$

$$-\frac{V_1}{5} + V_2 \left(\frac{1}{10} + \frac{1}{5} + \frac{1}{8} \right) = \frac{20}{10} = 2.$$

$$-0.2V_1 + V_2 (0.425) = 2 \cancel{\text{ // }} \rightarrow (2).$$

$$V_1 = 6.941 V_{\cancel{1}}$$

$$V_2 = 7.978 V_{\cancel{1}}$$

$$\begin{bmatrix} 0.95 & -0.2 \\ -0.2 & 0.425 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 5 \\ 2 \end{bmatrix}$$

$$\Delta = 0.363 \cancel{1}$$

$$V_1 = \begin{vmatrix} 5 & -0.2 \\ 2 & 0.425 \end{vmatrix} \div \Delta$$

CAMBRIDGE

INSTITUTE OF TECHNOLOGY

(SOURCE-DIGINOTES)

The branch currents are,

$$I_{b1} = \frac{10 - V_1}{2} = \frac{10 - 6.99}{2} = 1.53 A \text{ (→)}$$


$$I_{b2} = \frac{V_1 - V_3}{2} = \frac{6.99 - 0}{2} = 1.785 A \text{ (→)}$$

$$I_{b3} = \frac{V_1 - V_2}{5} = \frac{6.99 - 7.97}{5} = -0.206 A \text{ (←) opp.}$$

$$I_{b4} = \frac{V_2 - V_3}{8} = \frac{7.97 - 0}{8} = 0.996 A \text{ (→)}$$

$$I_{b5} = \frac{V_2 - 20}{10} = \frac{7.97 - 20}{10} = -1.203 A \text{ (←) opp.}$$

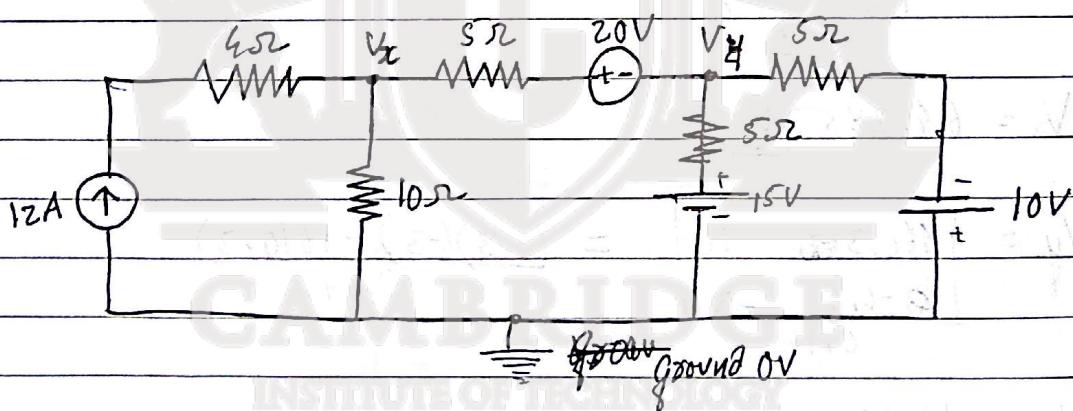Q. Find the node voltages V_x and V_y in the NW shown.



Apply KCC to node V_{20} ,

Note: (Since, 4Ω is in series with 12A current source, it has no significance.
 $\therefore 4\Omega$ is neglected.)

$$V_x \left[\frac{1}{10} + \frac{1}{5} \right] - V_y \left[\frac{1}{5} \right] = 12 + \frac{20}{5}$$

$$0.3V_x - 0.2V_y = 16 \text{ → } ①$$

Apply KCL to node V_y :

$$V_y \left[\frac{1}{5} + \frac{1}{5} + \frac{1}{5} \right] - V_x \left[\frac{1}{5} \right] = \frac{-20}{5} + \frac{15}{5} - \frac{10}{5}$$

$$-0.2V_x + 0.6V_y = -3 \quad \text{---} \rightarrow \textcircled{E},$$

$$\begin{bmatrix} 0.3 & -0.2 \\ -0.2 & 0.6 \end{bmatrix} \begin{bmatrix} V_x \\ V_y \end{bmatrix} = \begin{bmatrix} 1.6 \\ -3 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 0.3 & -0.2 \\ -0.2 & 0.6 \end{vmatrix}$$

$$\Delta = 0.14$$


$$V_x = \frac{1}{\Delta} \begin{vmatrix} 1.6 & -0.2 \\ -3 & 0.6 \end{vmatrix} = \frac{1.6(0.6) - (-0.2)(-3)}{0.14}$$

$$V_x = 6.42857 V$$

$$V_y = \frac{(0.3)(-3) + 1.6(-0.2)}{0.14} = \frac{(0.3)(-3) + 1.6(-0.2)}{0.14}$$

$$V_y = 16.42 V$$

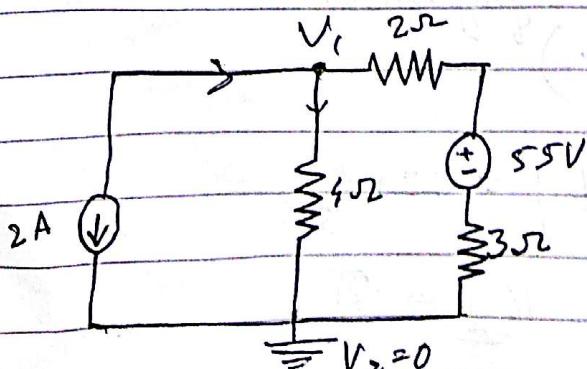Q. Find the power delivered by 2A current source in the NW shown.



Apply KCL to node V_1 :

$$V_1 \left[\frac{1}{4} + \frac{1}{5} \right] = -2 + \frac{55}{5}$$

$$0.45 V_1 = 9$$

$$V_1 = 20 \text{ V}$$


\therefore Power delivered by 2A current source,

$$P_{2A} = V_1 I$$

$$P_{2A} = 20 \times 2$$

$$P_{2A} = 40 \text{ Watts}$$

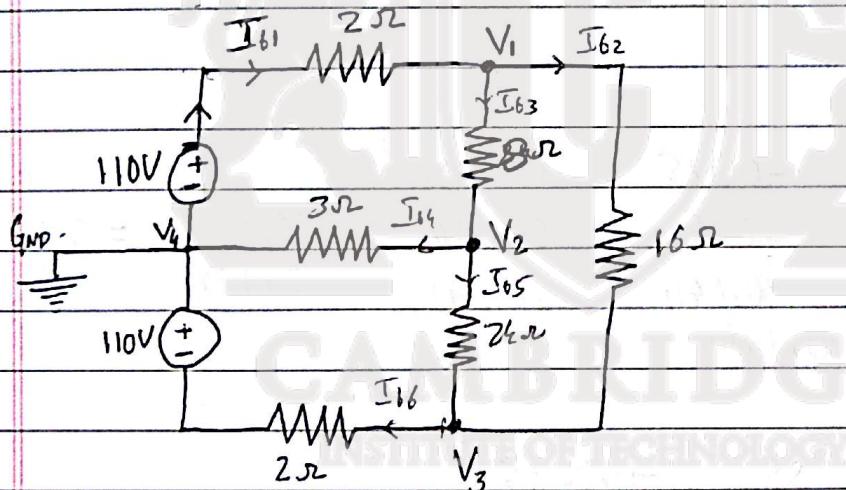Q. Find all the branch currents in the NW shown.



Apply KCL to node V_1 :

$$V_1 \left[\frac{1}{2} + \frac{1}{8} + \frac{1}{16} \right] - V_2 \left[\frac{1}{8} \right] - V_3 \left[\frac{1}{16} \right] = \frac{110}{2}$$

$$0.6875 V_1 - 0.125 V_2 - 0.0625 V_3 = 55 \rightarrow ①$$

Apply KCL to node V_2 :

$$V_2 \left[\frac{1}{8} + \frac{1}{3} + \frac{1}{24} \right] - V_1 \left[\frac{1}{8} \right] - V_3 \left[\frac{1}{24} \right] = 0$$

$$-0.125 V_1 + 0.5 V_2 - 0.0416 V_3 = 0 \rightarrow ②$$

Apply KCL to node V_3 :

$$V_3 \left[\frac{1}{2} + \frac{1}{16} + \frac{1}{24} \right] - V_2 \left[\frac{1}{24} \right] - V_1 \left[\frac{1}{16} \right] = \frac{-110}{2}$$

$$-0.0625 V_1 - 0.0416 V_2 + 0.6091 V_3 = -55 \rightarrow (3).$$

$$\begin{vmatrix} V_1 & 0.6875 & -0.125 & -0.0625 \\ V_2 & -0.125 & 0.5 & -0.0416 \\ V_3 & -0.0625 & -0.0416 & 0.6091 \end{vmatrix} = \begin{bmatrix} 55 \\ 0 \\ -55 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 0.6875 & -0.125 & -0.0625 \\ -0.125 & 0.5 & -0.0416 \\ -0.0625 & -0.0416 & 0.6091 \end{vmatrix}$$

$$\Delta = 0.1944$$

$$V_1 = \begin{vmatrix} 55 & -0.125 & -0.0625 \\ 0 & 0.5 & -0.0416 \\ -55 & -0.0416 & 0.6091 \end{vmatrix} = 14.5128 = 74.6834 V$$

0.1944

$$V_2 = \begin{vmatrix} 0.6875 & 55 & -0.0625 \\ -0.125 & 0 & -0.0416 \\ -0.0625 & -55 & 0.6091 \end{vmatrix} = 2.2935 = 11.7978 V$$

0.1944

$$V_3 = \begin{vmatrix} 0.6875 & -0.125 & 55 \\ -0.125 & 0.5 & 0 \\ -0.0625 & -0.0416 & -55 \end{vmatrix} = -16.0421 = -82.5212 V$$

0.1944

$$I_{b1} = \frac{110 - V_1}{2} = \frac{110 - 74.6544}{2} = 17.67 A_{\parallel}$$

$$I_{b2} = \frac{V_1 - V_3}{16} = \frac{74.65 + 82.521}{16} = 9.823 A_{\parallel}$$


$$I_{b3} = \frac{V_1 - V_2}{8} = \frac{74.65 - 11.79}{8} = 7.8575 A_{\parallel}$$

$$I_{b4} = \frac{V_2 - V_3}{8} = \frac{11.7978}{3} = 3.9326 A_{\parallel}$$

$$I_{b5} = \frac{V_2 - V_3}{24} = 3.929 A_{\parallel}$$

$$I_{b6} = \frac{V_3 - (-110)}{2} = \frac{-82.5212 + 110}{2} = 13.7394 A_{\parallel}$$

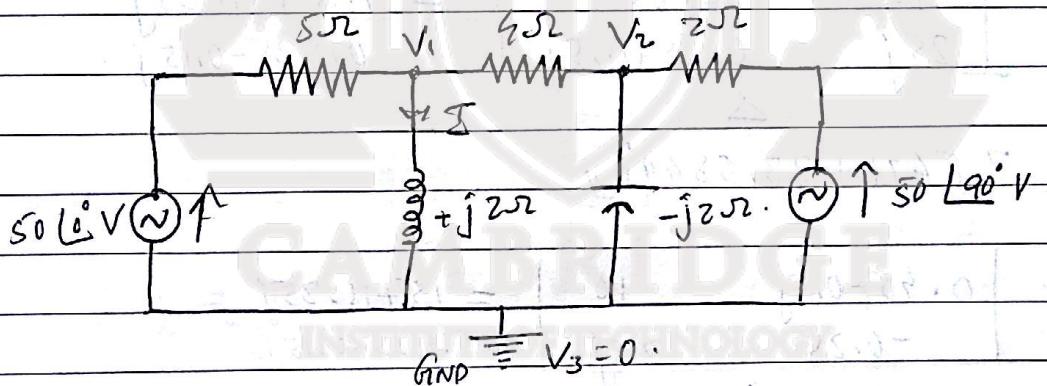Q. Find the value of current I in the N/W shown using node analysis.



Apply KCL to node V_1 :

$$V_1 \left[\frac{1}{5} + \frac{1}{4} + \frac{1}{j2} \right] - V_2 \left[\frac{1}{4} \right] = \frac{50 \angle 0^\circ}{5} = 50 + 0j$$

$$V_1 [0.45 - 0.5j] - 0.25 V_2 = 10_{\parallel}$$

Apply KCL to node V₂:

$$V_2 \left[\frac{1}{\frac{1}{4}} + \frac{1}{2} - \frac{1}{j2} \right] - V_1 \left[\frac{1}{4} \right] = \frac{50 \angle 90^\circ}{2}$$

~~$$-0.25V_1 + V_2 [0.75 + 0.5j] = 25j$$~~

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \begin{bmatrix} 0.45 - 0.5j & -0.25 \\ -0.25 & 0.75 + 0.5j \end{bmatrix} = \begin{bmatrix} 10 \\ 25j \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 0.45 - 0.5j & -0.25 \\ -0.25 & 0.75 + 0.5j \end{vmatrix}$$

$$\Delta = 0.525 - 0.15j$$

$$V_1 = \begin{vmatrix} 10 & -0.25 \\ 25j & 0.75 + 0.5j \end{vmatrix} = \frac{7.5 + 11.25j}{0.525 - 0.15j}$$

$$V_1 = 7.5471 + 23.5849j$$

$$V_2 = \begin{vmatrix} 0.45 - 0.5j & 10 \\ -0.25 & 25j \end{vmatrix} = \frac{15 + 11.25j}{0.525 - 0.15j} =$$


$$V_2 = 20.754 + 27.358j$$

$$I = \frac{V_1 - V_2}{j2} = \frac{(7.5471 + 23.5849j) - 0}{j2}$$


$$I = 11.7924 - 3.7735j$$

$$I = 12.3815 \angle -17.75^\circ A$$

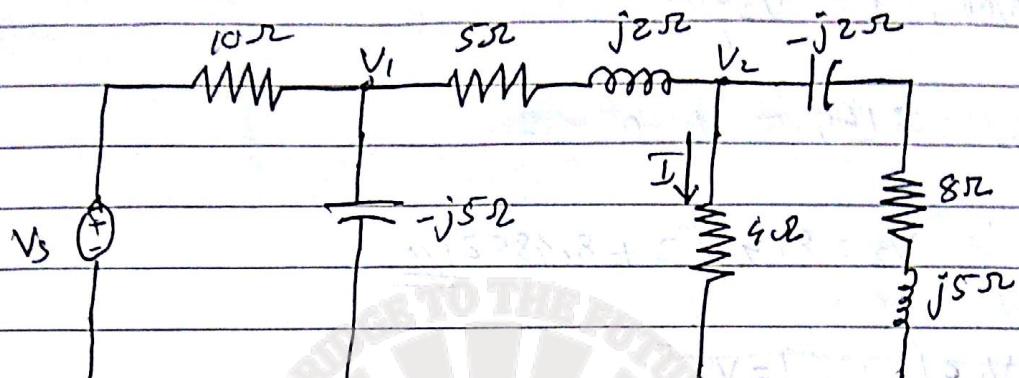Q. Find the value of V_s in the N/w shown such that current $I = 3\angle 45^\circ A$ Using node analysis.



$$\text{GND} \equiv V_3 = 0$$

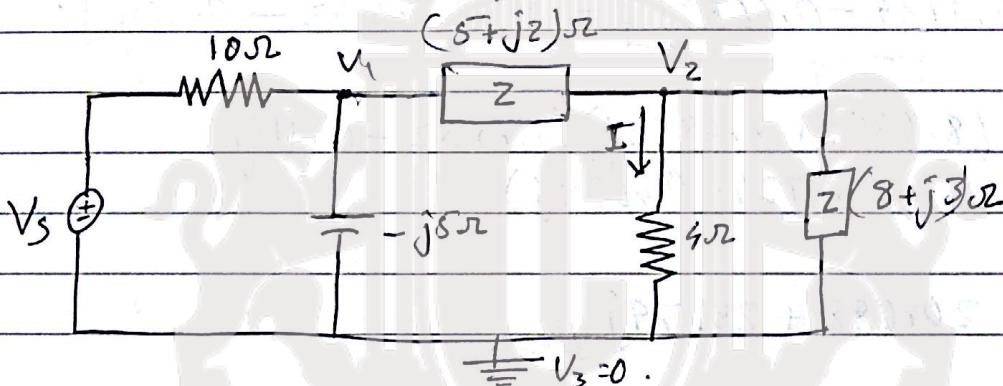

$$\equiv V_3 = 0$$

Apply KCL to node V_1 :

$$V_1 \left[\frac{1}{10} - \frac{1}{j5} + \frac{1}{5+j2} \right] - V_2 \left[\frac{1}{5+j2} \right] = \frac{V_s}{10}$$

$$[0.2724 + 0.1310j] V_1 - (0.1724 - 0.0689j) V_2 = \frac{V_s}{10} = 0.1 V_s \quad \rightarrow \textcircled{1}$$

Apply KCL to node V_2 :

$$V_2 \left[\cancel{\frac{1}{5+j2}} + \frac{1}{4} + \frac{1}{8+j3} \right] - V_1 \left[\frac{1}{5+j2} \right] = 0$$

$$[0.532 - 0.110j] V_2 - (0.1724 - 0.0689j) V_1 = 0 \rightarrow \textcircled{2}$$

~~$V_1 = V_2 - V_3$~~

Now, $\angle = V_2 - V_3$

$$3145^\circ = V_2 - 0$$

$$V_2 = 8.4852 + 8.4852j$$

$$V_1 \bullet \left[\frac{1}{5+j2} \right] = V_2$$

F-DOM (7)

$$V_1 [0.1724 - 0.0689j] = V_2 [0.532 - 0.110j] -$$

$$V_1 = \frac{(8.4852 + 8.4852j)(0.532 - 0.110j)}{(0.1724 - 0.0689j)}$$

(8)

$$V_1 = 20.088 + 28.79j$$

$$[0.2724 + 0.1310j] V_1 - (0.1724 - 0.0689j) V_2 = 0.1 V_s$$

$$(0.1) V_s = [0.2724 + 0.1310j] [20.088 + 28.79j] - [0.1724 - 0.0689j] [8.4852 + 8.4852j]$$

~~$0.1 V_s = -3674.9245 + 7650.4729j$~~

~~$V_s = -3674.9245 + 7650.4729j$~~


~~$V_s = 84873.320 \angle 115.65^\circ$~~

~~$0.1 V_s = -0.3469 + 9.59j$~~

~~$V_s = -3.469 + 98.9j$~~ (08)

~~$V_s = 96.0197 \angle 92.071$~~

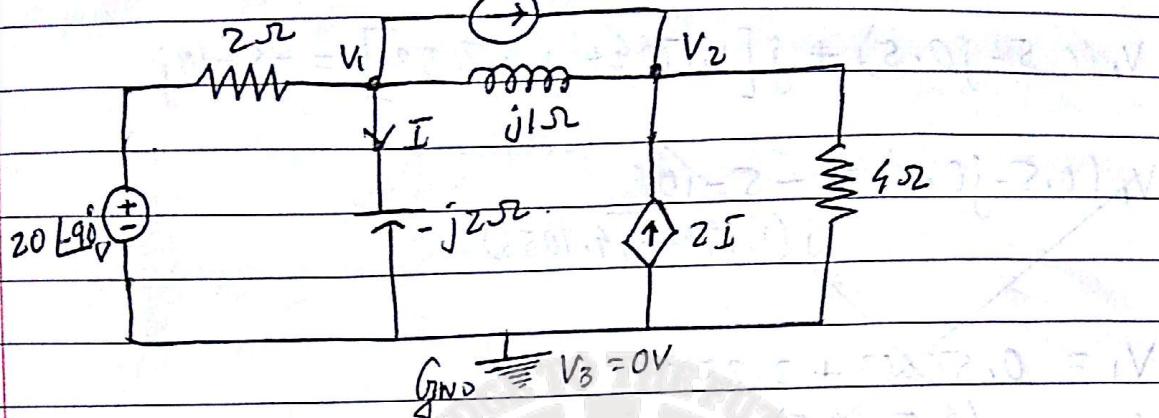Q. Find the value of current I using node analysis.



Apply KCL to node V_1 :

$$V_1 \left[\frac{1}{2} + \frac{1}{-2j} + \frac{1}{j1\Omega} \right] - V_2 \left[\frac{1}{j1\Omega} \right] = \frac{20 \angle -90^\circ}{2} - 5 \angle 10^\circ$$

$$(0.5 - 0.5j) V_1 - V_2 (-j) = -5 - 10j$$

$$(0.5 - 0.5j) V_1 + j V_2 = -5 - 10j \quad \underline{\underline{I}}$$

Apply KCL to node V_2 :

$$V_2 \left[\frac{1}{j} + \frac{1}{4} \right] - V_1 \left[\frac{1}{j} \right] = 5 \angle 10^\circ + 2 \angle 0^\circ$$

$$(0.25 + j) V_2 - V_1 = 5 + 2 \angle 10^\circ$$

$$\therefore V_1(j) + (0.25 - j)V_2 = 5 + 2 \left(\frac{V_1}{-j2} \right) = 5 + V_1 j$$

$$(0.25 - j)V_2 = 5$$

$$V_2 = \frac{5}{0.25 - j}$$

$$V_2 = 1.1764 + 4.7058j \quad \underline{\underline{V_2}}$$

$$V_2 = 4.85 \angle 75.96^\circ \quad \underline{\underline{V_2}}$$

Substitute V_2 in eqn ①,

$$V_1(0.5 - j0.5) + j[1.1764 + j4.7058] = -5 - 10j$$

~~$$V_1(0.5 - j0.5) = \frac{-5 - 10j}{j(1.1764 + j4.7058)}$$~~

~~$$V_1 = \frac{0.50003 + 2.25004j}{(0.5 - j0.5)}$$~~

~~$$V_1 = -1.750 + 2.750j \underline{\underline{V_F}}$$~~

~~$$V_1 = -3.289 \angle 122.47^\circ \underline{\underline{V_F}}$$~~

$$V_1(0.5 - j0.5) = -0.2942 - 11.1764j$$

~~$$\underline{\underline{V_F}} = 10.8822 - 11.4706j \underline{\underline{V_F}}$$~~

~~$$V_F = 15.811 \angle -46.50^\circ \underline{\underline{V_F}}$$~~


$$I_r = \frac{V_F}{-j2} = +5.7353 + 5.4411j \quad \underline{\underline{A_F}}$$

~~$$17.9056 \angle 53.5^\circ \underline{\underline{A_F}}$$~~

$$I = 17.9056 \angle 53.5^\circ \underline{\underline{A_F}}$$

77° 28'

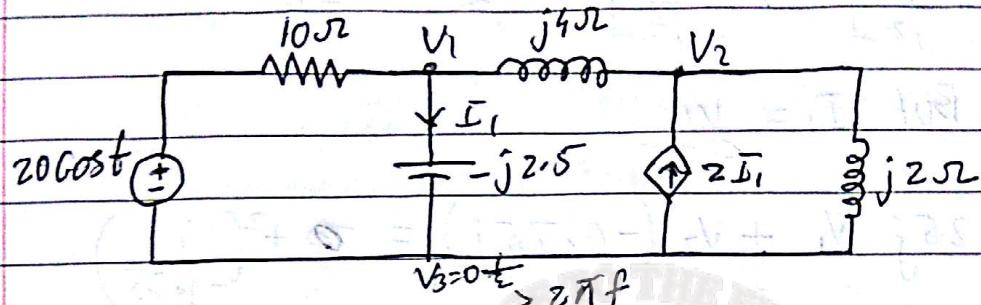Q. Find the value of the current I_1 in the NW shown using Node analysis.



$$V(t) = A \sin(\omega t + \phi)$$

\hookrightarrow Amplitude \rightarrow Phase Angle

$$A \cos \phi$$

$$20 \cos t \Rightarrow A = 20; \omega = 1; \phi = 0.$$

~~$20 \cos t = 20 \cos 0$~~

Apply KCL to V_1 :

$$V_1 \left[\frac{1}{10} + \frac{1}{j4} - \frac{1}{2j5} \right] - V_2 \left[\frac{1}{j4} \right] = \frac{20}{10}$$

$$(0.35 + 0.4j)V_1 - (0.25)V_2 = 20 \quad \text{--- (1)}$$

Apply KCL to V_2 :

$$V_2 \cancel{\left(\frac{1}{j4} \right)}$$

Apply KCL to V_1 :

$$V_1 \left[\frac{1}{10} + \frac{1}{j4} - \frac{1}{j2-5} \right] - V_2 \left[\frac{1}{j4} \right] = \frac{20}{10}$$

$$(0.1 + 0.15j)V_1 + (0.25j)V_2 = 2 \quad \text{--- (2)}$$

Apply KCL to node V_2 :

$$V_2 \left[\frac{1}{j5} + \frac{1}{j2} \right] - V_1 \left[\frac{1}{j5} \right] = 0 + 2I_1$$

$$\text{But } I_1 = \frac{V_1}{-j2.5}$$

~~$$0.25j V_1 + V_2 (-0.75j) = 0 + \left(\frac{V_1}{-j2.5} \right)$$~~

$$0.25j V_1 - 0.75j V_2 = 0 + 2V_1 = 0$$

$$(0.25j + \frac{2}{j2.5}) V_1 - 0.75j V_2 = 0.$$

~~$$-0.55 \cancel{j} V_1 - 0.75j V_2 = 0.$$~~

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \begin{bmatrix} 0.1 + 0.15j \\ \cancel{0.25j} \\ -7.75j \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 0.1 + 0.15j & 0.25j \\ -7.75j & -0.75j \end{vmatrix}$$

$$\Delta = -1.825 - 0.075j \cancel{\neq}$$

$$V_1 = \frac{1}{\Delta} \begin{vmatrix} 2 & 0.25j \\ 0 & -0.75j \end{vmatrix} = -1.5j$$

$$\Delta = -1.825 - 0.075j$$

$$V_1 = 18.97 \angle 18.45^\circ$$

$$I_1 = 7.89 \angle 108.4^\circ$$

$$(0.1 + 0.15j)V_1 + (0.25j)V_2 = 2 \cancel{\text{A}}$$

$$(-0.55j)V_1 - 0.75jV_2 = 0.$$

$$\Delta = \begin{vmatrix} 0.1 + 0.15j & 0.25j \\ -0.55j & -0.75j \end{vmatrix}$$

$$\Delta = -0.025 - 0.075j \cancel{\text{A}}$$

$$V_1 = \begin{vmatrix} 2 & 0.25j \\ 0 & -0.75j \end{vmatrix} \cancel{\Delta}$$

$$V_1 = \frac{-1.5j}{-0.025 - 0.075j}$$

$$V_1 = 18 + 6i \cancel{\text{V}}$$

$$V_1 = 18.473 \angle 18.48^\circ \cancel{\text{V}}$$

$$i + I_1 = \frac{V_1}{-j2.5} = \frac{18+6i}{-j2.5}$$

$$I_1 = -2.4 + 7.2j$$


$$I_1 = 7.58 \angle 108.4^\circ \cancel{\text{A}}$$

i. Current I_1 in time domain ~~is~~ is I_1 ,

$$I_1 = 7.58 \cos(t + 108.4^\circ) \cancel{\text{A}}$$

Super-Node Analysis:

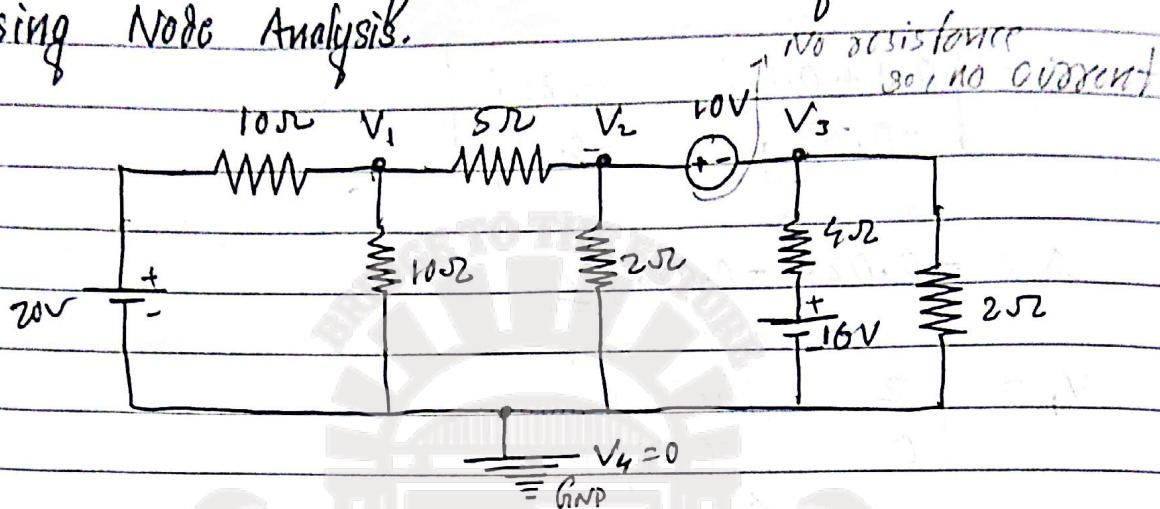- a. Find the value of I_{SR} in the given NW using Node Analysis.



10V voltage source is connected b/w the nodes V_2 and V_3 . Therefore, $V_2 - V_3$ forms a super node.

Therefore, $V_2 - V_3 = 10 \text{ V} \rightarrow \textcircled{1}$.

Apply 100V to node V_1 :

$$V_1 \left[\frac{1}{10} + \frac{1}{10} + \frac{1}{5} \right] - V_2 \left[\frac{1}{5} \right] = \frac{20}{10}$$

$$0.4V_1 - 0.2V_2 = 2 \rightarrow \textcircled{2}$$

Now apply 100V to supernode $V_2 - V_3$,

$$V_2 \left[\frac{1}{5} + \frac{1}{2} \right] + V_3 \left[\frac{1}{5} + \frac{1}{2} \right] - V_1 \left[\frac{1}{5} \right] = \frac{16}{5}$$

$$-0.2V_1 + 0.7V_2 + 0.75V_3 = 3.2 \rightarrow \textcircled{3}$$

$$\rho \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} \begin{bmatrix} 0 & 1 & -1 \\ 0.4 & -0.2 & 0 \\ -0.2 & 0.7 & 0.75 \end{bmatrix} = \begin{bmatrix} 10 \\ 2 \\ 4 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 0 & 1 & -1 \\ 0.4 & -0.2 & 0 \\ -0.2 & 0.7 & 0.75 \end{vmatrix} = -0.54$$

$$V_3 = \frac{1}{\Delta} \begin{vmatrix} 0 & 1 & 10 \\ 0.4 & -0.2 & 2 \\ -0.2 & 0.7 & 4 \end{vmatrix} = \frac{0.4}{-0.54} = -0.740$$

$$V_3 = -0.740$$


Current across 4Ω resistance,

$$I_{4\Omega} = \frac{V_3 - 16}{4} = -0.740 - 16$$

$$I_{4\Omega} = -4.185 A \quad I_{4\Omega} = \frac{16 - V_3}{4} = \frac{16 - (-0.740)}{4}$$

$$I_{4\Omega} = 4.185 A$$

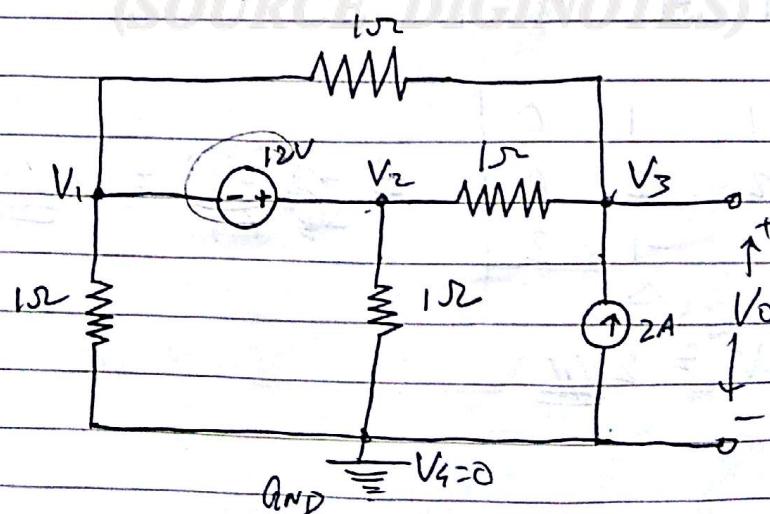Q. Find the value of V_0 in the circuit shown:



12 V voltage source is connected b/w the 2 nodes V_1 & V_2

$$V_2 - V_1 = 12 \text{ V} \rightarrow \textcircled{1}$$

Apply KCL to node $V_1 - V_2$:

$$V_1 \left[\frac{1}{1} + \frac{1}{1} \right] + V_2 \left[\frac{1}{1} + \frac{1}{1} \right] - V_3 \left[\frac{1}{1} \right] - V_3 \left[\frac{1}{1} \right] = 0$$

$$2V_1 + 2V_2 - 2V_3 = 0 \rightarrow \textcircled{2}$$

Apply KCC to node V_3 :

$$V_3 \left[\frac{1}{1} + \frac{1}{1} \right] - V_1 \left[\frac{1}{1} \right] - V_2 \left[\frac{1}{1} \right] = 2$$

$$-V_1 - V_2 + 2V_3 = 2 \rightarrow \textcircled{3}$$


$$\begin{bmatrix} 0 & -1 & 1 & 0 \\ 2 & 2 & -2 & 0 \\ -1 & -1 & 2 & 2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 2 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} -1 & 1 & 0 \\ 2 & 2 & -2 \\ -1 & -1 & 2 \end{vmatrix} = -4$$

$$V_3 = \frac{\begin{vmatrix} 0 & -1 & 1 \\ 0 & 2 & -2 \\ 2 & -1 & 2 \end{vmatrix}}{\Delta} = \frac{0 + 8}{-4} = 2 \text{ V}$$

$$\therefore V_0 = V_3 = 2 \text{ V}$$

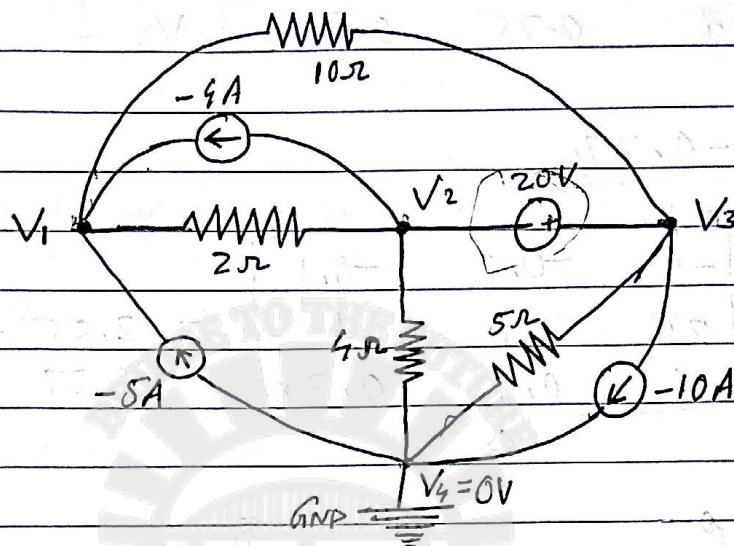Q. Find all the node voltages V_1 , V_2 and V_3 using
node analysis.



Apply KCL to node V_1 :

$$V_1 \left[\frac{1}{2} + \frac{1}{10} \right] - V_2 \left[\frac{1}{2} \right] - V_3 \left[\frac{1}{10} \right] = -5 - 8.$$

$$0.6V_1 - 0.5V_2 - 0.1V_3 = -13 \rightarrow ①$$

Q. There is a 20V voltage source b/w the nodes V_2 and V_3 .

$$\therefore V_3 - V_2 = 20 \rightarrow ②$$

$V_2 - V_3$ forms a super-node.

Apply KCL to this super-node,

$$V_2 \left[\frac{1}{2} + \frac{1}{5} \right] + V_3 \left[\frac{1}{5} + \frac{1}{10} \right] - V_1 \left[\frac{1}{2} \right] - V_1 \left[\frac{1}{10} \right] = 4 + 10$$

$$-0.6V_1 + 0.75V_2 + 0.3V_3 = 14 \rightarrow ③$$

$$\begin{bmatrix} 0.6 & -0.5 & -0.1 \\ 0 & -1 & 1 \\ -0.6 & 0.75 & 0.3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} -9 \\ 20 \\ 14 \end{bmatrix}$$


$$\Delta = -0.27$$

$$V_1 = \frac{\begin{vmatrix} -9 & -0.5 & -0.1 \\ 20 & -1 & 1 \\ 14 & 0.75 & 0.3 \end{vmatrix}}{\Delta} = \frac{-2.55}{-0.27} = 9.44 V$$

$$V_2 = \frac{\begin{vmatrix} 0.6 & -9 & -0.1 \\ 0 & 20 & 1 \\ -0.6 & 14 & 0.3 \end{vmatrix}}{\Delta} = \frac{-0.6}{-0.27} = 2.22 V$$

$$V_3 = \frac{\begin{vmatrix} 0.6 & -0.5 & -9 \\ 0 & -1 & 20 \\ -0.6 & 0.75 & 14 \end{vmatrix}}{\Delta} = \frac{-6}{-0.27} = 22.22 V$$

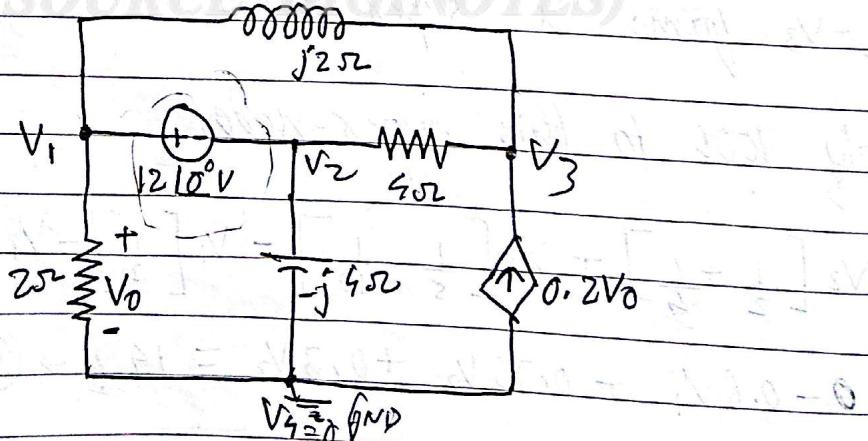Q. Find the value of V_o in the NLR shown.



$12 \angle 0^\circ V$ voltage source is b/w the nodes V_1 and V_2 .
 $\therefore V_1 - V_2$ forms the super-node.

Apply KCL to this super-node:

$$V_1 \left[\frac{1}{2} + \frac{1}{j2} \right] + V_2 \left[\frac{1}{4} + \frac{1}{-j4} \right] - V_3 \left[\frac{1}{4} \right] - V_3 \left[\frac{1}{j2} \right] = 0.$$

$$[0.5 - 0.5j] V_1 + [0.25 + 0.25j] V_2 - [0.25] V_3 - [0.25j] V_3 = 0.$$

$$[0.5 - 0.5j] V_1 + [0.25 + 0.25j] V_2 + [-0.25 + 0.5j] V_3 = 0 \quad \text{--- (1)}$$

$$\bullet V_1 - V_2 = 12 \angle 0^\circ$$

$$V_1 - V_2 = 12 \angle 0^\circ \rightarrow \text{--- (2)}$$

Apply KCL to node V_3 :

$$V_3 \left[\frac{1}{4} + \frac{1}{j2} \right] - V_2 \left[\frac{1}{4} \right] - V_1 \left[\frac{1}{j2} \right] = 0.2 V_0$$

$$0.5j V_1 - 0.25 V_2 + [0.25 - 0.5j] V_3 = 0.2 V_0.$$

According to the given problem $V_0 = V_1$

~~At node V_1~~

$$\therefore 0.5j V_1 - 0.25 V_2 + [0.25 - 0.5j] V_3 = 0.2 V_1$$

$$0.5j V_1 - 0.2 V_1 - 0.25 V_2 + [0.25 - 0.5j] V_3 = 0.2 V_1$$

$$[0.5j - 0.2] V_1 - 0.25 V_2 + [0.25 - 0.5j] V_3 = 0.2 V_1$$

$$[-0.2 + 0.5j] V_1 - 0.25 V_2 + [0.25 - 0.5j] V_3 = 0.2 V_1 \quad \text{--- (3)}$$

$$\begin{bmatrix} 0.5 - 0.5j & 0.25 + 0.25j & -0.25 + 0.5j \\ 1 & -1 & 0 \\ -0.2 + 0.5j & -0.25 & 0.25 - 0.5j \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 12 \\ 0 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 0.5 - 0.5j & 0.25 + 0.25j & -0.25 + 0.5j \\ 1 & -1 & 0 \\ -0.2 + 0.5j & -0.25 & 0.25 - 0.5j \end{vmatrix}$$

$$\Delta = (-0.25 + 0.5j) [(-0.25) - (-1)(-0.2 + 0.5j)] + (0.25 - 0.5j) [(0.5 - 0.5j)(-1) - (0.25 + 0.25j)]$$

$$\Delta = -0.1375 - 0.35j$$

$$\Delta = -0.2 + 0.0875j$$

$$V_1 = \begin{vmatrix} 0 & 0.25 + 0.25j & -0.25 + 0.5j \\ 12 & -1 & 0 \\ 0 & -0.25 & 0.25 - 0.5j \end{vmatrix} \Delta$$

$$V_1 = -12 [(0.25 + 0.25j)(0.25 - 0.5j) - (-0.25)(-0.25 + 0.5j)]$$

~~V₁~~

Δ

$$V_1 = \frac{-1.5 - 0.75j}{-0.2 + 0.0875j}$$

$$V_1 = 4.918 + 5.901j$$

$$V_1 = 7.6822 \angle 50.19^\circ V_A$$


$$\therefore V_0 = 4.918 + 5.901j V_{A\text{ (as)}}$$

$$V_0 = 7.6822 \angle 50.19^\circ V_A$$

Q. For the following nodal equations construct the N/w.

$$V_1 \left[\frac{1}{5} + \frac{1}{j2} + \frac{1}{j2} \right] - V_2 \left[\frac{1}{j2} \right] = \frac{50 \angle 0^\circ}{5} \rightarrow ①.$$

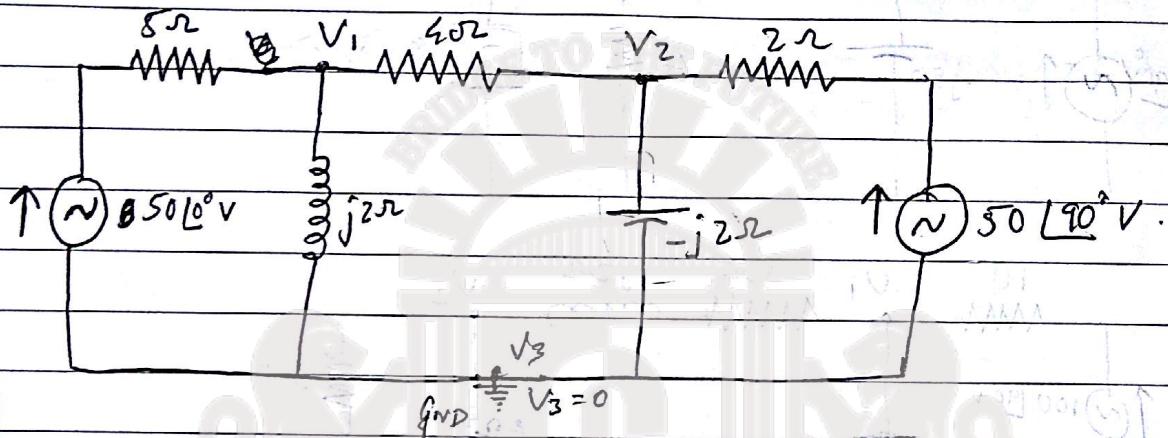
$$- V_1 \left[\frac{1}{j2} \right] + V_2 \left[\frac{1}{j2} + \frac{1}{2} + \frac{1}{-j2} \right] = \frac{50 \angle 90^\circ}{2} \rightarrow ②.$$



Q. For the following nodal equations, develop the ckt.

$$V_1 \left[\frac{1}{1} + \frac{1}{j} + \frac{1}{0.5} \right] - V_2 \left[\frac{1}{0.5} \right] = \frac{15}{1} \rightarrow ①.$$
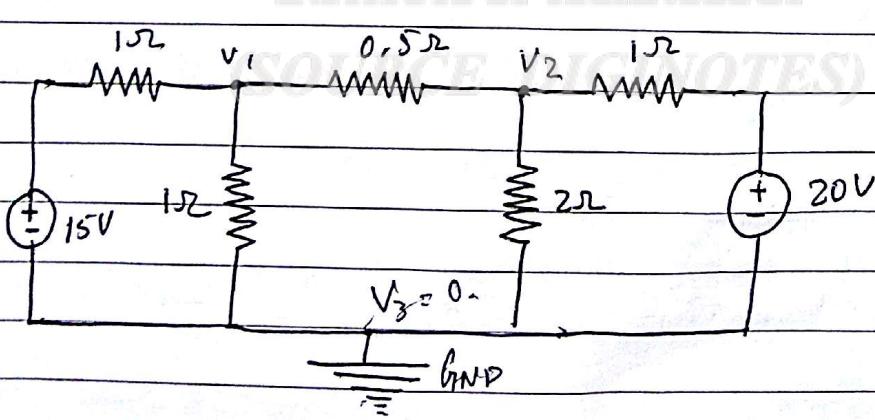
$$- V_1 \left[\frac{1}{0.5} \right] + V_2 \left[\frac{1}{0.5} + \frac{1}{2} + \frac{1}{1} \right] = \frac{20}{1} \rightarrow ②.$$



Q. $V_1 \left[\frac{1}{10} + \frac{1}{-j5} + \frac{1}{5+j2} \right] - V_2 \left[\frac{1}{5+j2} \right] = \frac{100}{10} e^{j90^\circ} \rightarrow ①.$

$-V_1 \left[\frac{1}{(5+j2)} \right] + V_2 \left[\frac{1}{5+j2} + \frac{1}{4} + \frac{1}{8+j3} \right] = 0 \rightarrow ②.$

