
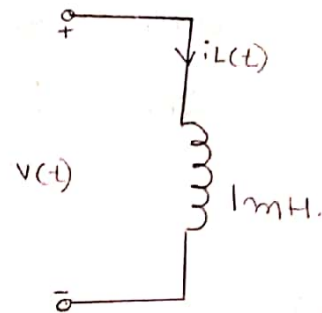


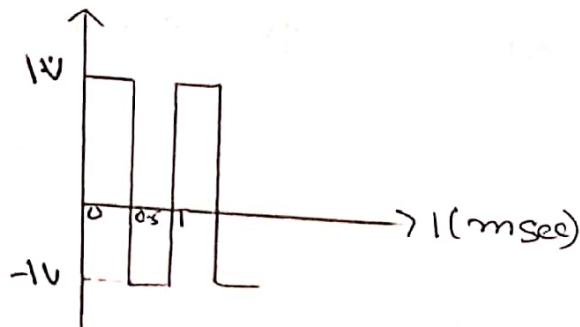
1. A square waveform as shown in figure is applied across 1mH. ideal inductor. The current through inductor is a



current through an inductor is given by,

$$i_L(t) = \frac{1}{L} \int_0^t v(t) dt$$

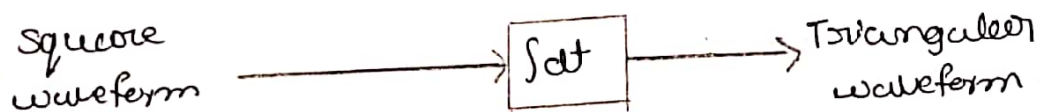So current through inductor is the integration of the applied voltage across the inductor.




The square wave can be written as,

$$v(t) = u(t) - 2u(t-0.5) + 2u(t-1) - \dots$$


Integrating the voltage to get current through the inductor,
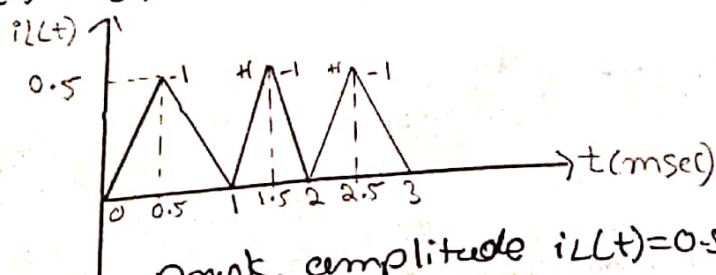
$$i_L(t) = r(t) - 2r(t-0.5) + 2r(t-1) - \dots$$




peak. amplitude  $i_L(t) = 0.5 \text{ Amp.}$

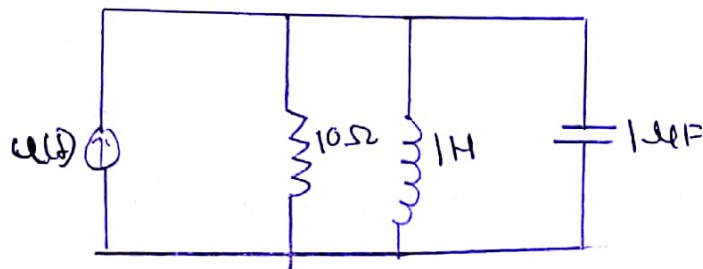2. A  $10\Omega$  resistor, a  $1H$  inductor and  $1\mu F$  capacitor are connected in parallel. The combination is driven by a unit step current. Under the steady state condition, the source current flows through. ....



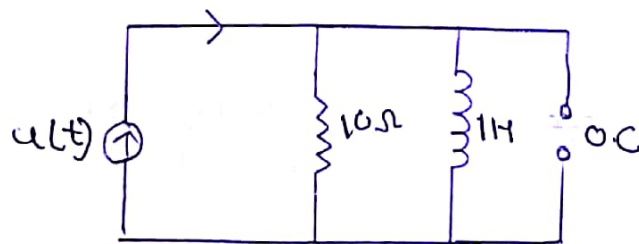Under steady state condition, inductor behaves as a short circuit and capacitor behaves as an open circuit.



Hence, the source current flows through the inductor only.

3. If the Laplace transform of the voltage across a capacitor of value of  $\frac{1}{2}F$  is  $V_C(s) = \frac{s+1}{s^3+s^2+s+1}$ , the value of current through the capacitor at  $t=0^+$  is

Given:  $C = \frac{1}{2}F$ ,  $V_C(s) = \frac{s+1}{s^3+s^2+s+1}$

For capacitor,  $x_C = \frac{1}{Cs} = \frac{1}{\frac{1}{2}s} = \frac{2}{s}$

Transform voltage of capacitor is given by,

3

$$V_C(s) = I_C(s) X_C$$

$$I_C(s) = \frac{V_C(s)}{X_C} = \frac{(s+1)s}{(s^3+s^2+s+1)2}$$

The value of current at  $t=0^+$ , means it is the initial value.

By initial theorem,

$$i_C(0^+) = \lim_{s \rightarrow \infty} s I_C(s)$$


$$i_C(0^+) = \lim_{s \rightarrow \infty} \frac{s \times s(s+1)}{2(s^3+s^2+s+1)}$$


$$i_C(0^+) = \lim_{s \rightarrow \infty} \frac{s^2(s+1)}{2(s^3+s+1)(s+1)}$$

$$i_C(0^+) = \lim_{s \rightarrow \infty} \frac{s^3(1+\frac{1}{s})}{2s^3(1+\frac{1}{s^2})s(1+\frac{1}{s})}$$

$$i_C(0^+) = \frac{1}{2+0} = \frac{1}{2} \text{ A}$$

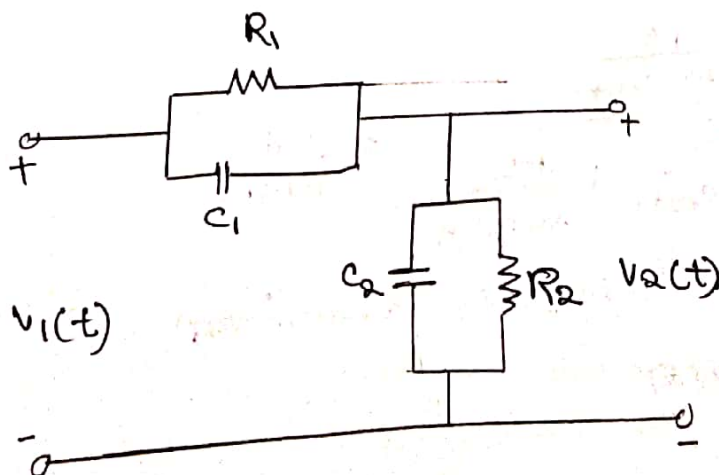4 For the compensated attenuator, of figure the impulse response under the condition  $R_1 C_1 = R_2 C_2$  is




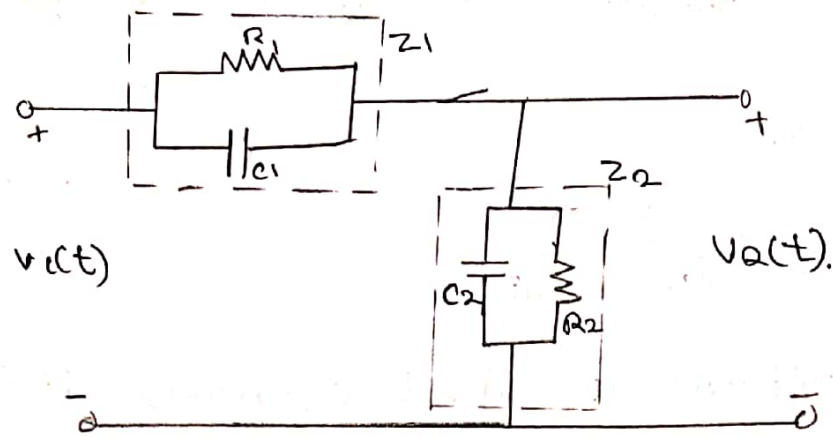

$$Z_1(s) = \frac{R_1 \times \frac{1}{Cs}}{R_1 + \frac{1}{Cs}}$$

$$Z_1(s) = \frac{R_1}{R_1Cs + 1} = \frac{R_1}{R_1Cs + 1}$$
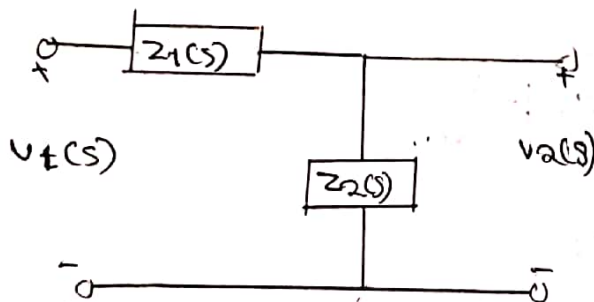
$$Z_2(s) = \frac{R_2 \times \frac{1}{Cs}}{R_2 + \frac{1}{Cs}} = \frac{R_2}{R_2Cs + 1} \quad [\text{Given: } R_1C_1 = R_2C_2]$$



$$\frac{V_2(s)}{V_1(s)} = \frac{Z_2(s)}{Z_1(s) + Z_2(s)}$$

$$\frac{V_2(s)}{V_1(s)} = \frac{\frac{R_2}{R_2Cs + 1}}{\frac{R_1}{R_1Cs + 1} + \frac{R_2}{R_2Cs + 1}} = \frac{R_2}{R_1 + R_2}$$

taking inverse Laplace transform,

$$V_2(t) = \frac{R_2}{R_1 + R_2} V_1(t)$$


$$V_1(t) = \delta(t)$$



$$V_2(t) = \frac{R_2}{R_1 + R_2} V(t)$$


5

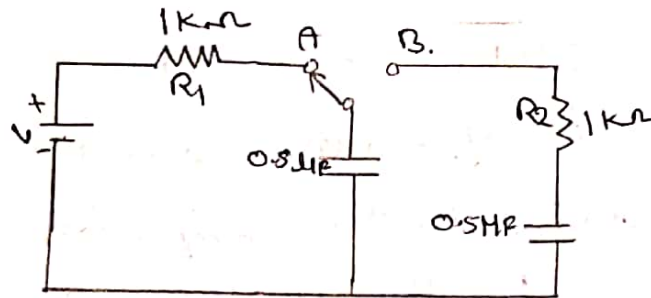5 For the circuit shown below different time constant are given.



1)  $0.5 \times 10^{-3}$  sec, 2)  $2 \times 10^{-3}$  sec, 3)  $0.25 \times 10^{-3}$  sec, 4)  $10^{-3}$  sec

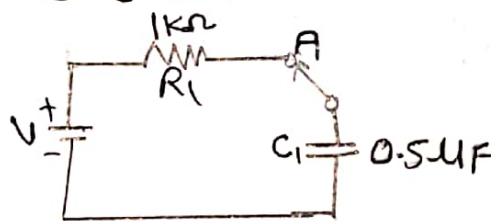i) calculation of charging time constant when a switch is at position A.




Above figure is charging circuit, hence for a RC network, charging time constant is given by

$$\tau_1 = R_1 C_1 = 1 \times 10^3 \times 0.5 \times 10^{-6}$$

$$\tau_1 = 0.5 \times 10^{-3} \text{ sec}$$

ii) calculation of discharging time constant.

when switch is at position B,

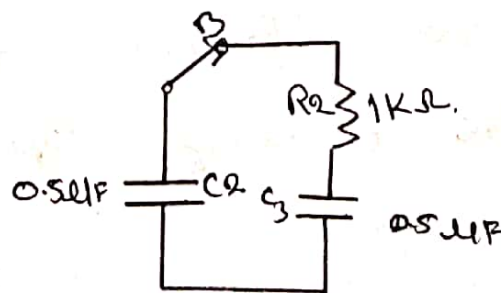

Above figure is a discharging circuit, because it does not have any independent source

From a R-C network, discharging time constant  $\tau$  is given by,

$$\tau = RC = 10^3 \times 0.25 \times 10^{-6}$$


$$\tau = 0.25 \times 10^{-3} \text{ sec}$$

6 Consider a DC voltage source connected to a series R-C circuit, when the steady-state reaches, the ratio of the energy stored in the capacitor to the total energy supplied by the voltage source, is equal to.

current through capacitor is given by

$$i_c(t) = i_c(\infty) + [i_c(0) - i_c(\infty)]e^{-t/\tau} \dots (1)$$

(i) At  $t=0$  (transient):

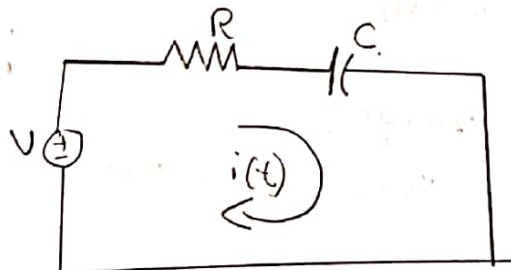

For a R-C network

Time constant  $\tau = RC$  sec

i.i) At  $t=0^+$ :


If there is no information about capacitor then we assume uncharged capacitor i.e.

$$V_c(0^-) = V_c(0^+) = 0V.$$

At  $t=0^+$ , capacitor is replaced by voltage source with initial value, i.e.

$$V_C(\infty) = 0$$

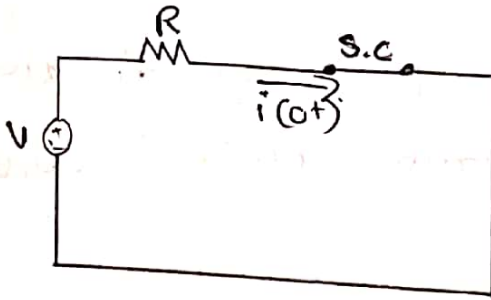
$$V_C(0^-) = 0 \text{ V (short circuit)}$$



$$i(0^+) = \frac{V}{R}$$

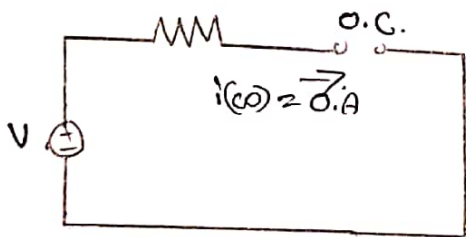ii) At  $t = \infty$  / steady state;

In steady state, capacitor behaves as an open circuit



Put the values of  $i(0^+)$ ,  $i(\infty)$  and  $\tau$  in equation (i)

$$i(t) = \frac{V}{R} e^{-\frac{t}{RC}} u(t)$$

Total energy ws supplied by the voltage source, for.

$0 < t < \infty$  is given by,

$$W_s = \int V i(t) dt$$

$$W_s = \int_0^{\infty} \frac{V^2}{R} e^{-\frac{t}{RC}} dt = \frac{V^2}{R} (-RC) \left[ e^{-\frac{t}{RC}} \right]_0^{\infty}$$

$$W_s = CV^2 \text{ J} \quad \text{--- (2)}$$

$$V_C(\infty) = V$$

Energy stored in the capacitor at  $t = \infty$ ,

$$W_c = \frac{1}{2} CV^2 \text{ J} \quad \text{--- (3)}$$


From equation (2) and (3)

8

$$\frac{W_c}{W_s} = \frac{\frac{1}{2} C V^2}{C V^2} = \frac{1}{2}$$

7

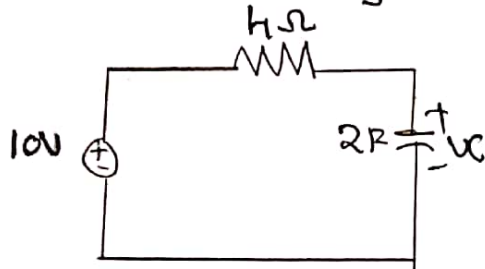
In the circuit of figure the energy absorbed by the  $4\Omega$  resistor in time interval  $(0, \infty)$  is [Given:  $V_c(0) = 6V$ ]



Voltage across the capacitor given by,

$$V_c(t) = V_c(0^+) = 6V \text{ [Given]}$$

(i) At  $t \geq 0$  (Transient):

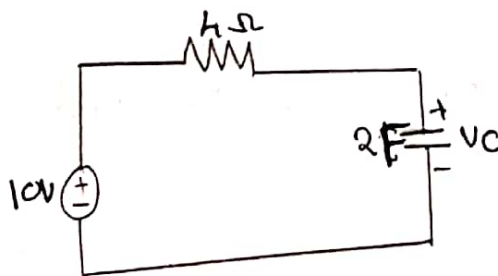


For a RC network

$$\text{Time constant, } \tau = RC = 4 \times 2 = 8 \text{ sec}$$

(ii) At  $t = \infty$  / steady state:

In steady state, capacitors behave as an open circuit.

The circuit will become as shown below

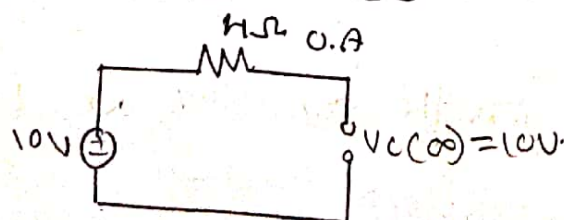



Put the values of  $V_c(0^+)$ ,  $V_c(\infty)$  and  $\tau$  in equation

(i)

$$V_c(t) = 10 + [6 - 10] e^{-t/8}$$

$$V_c(t) = 10 - 4e^{-t/8} V.$$

Current through capacitor is given by,

$$i_c(t) = C \frac{d}{dt} V_c(t)$$

$$i_c(t) = 2 \frac{d}{dt} (10 - 4e^{-t/8})$$

$$i_c(t) = 2 \left[ -4e^{-t/8} \times \left[ -\frac{1}{8} \right] \right]$$

$$i_c(t) = e^{-t/8} A$$

Power absorbed by resistor  $R$  is given by,

$$P = i_c^2(t) R$$

~~Energy~~ to


Energy absorbed by Resistor  $R$  is given by,

$$E_R = \int_0^{\infty} P dt = \int_0^{\infty} i_c^2(t) R dt = \int_0^{\infty} (e^{-t/8})^2 \times 4 dt$$

$$E_R = \int_0^{\infty} 4e^{-t/4} dt = 4 \times (-4) \left[ e^{-t/4} \right]_{t=0}^{\infty}$$


$$E_R = -16 [0 - 1] = 16 \text{ Joules}$$

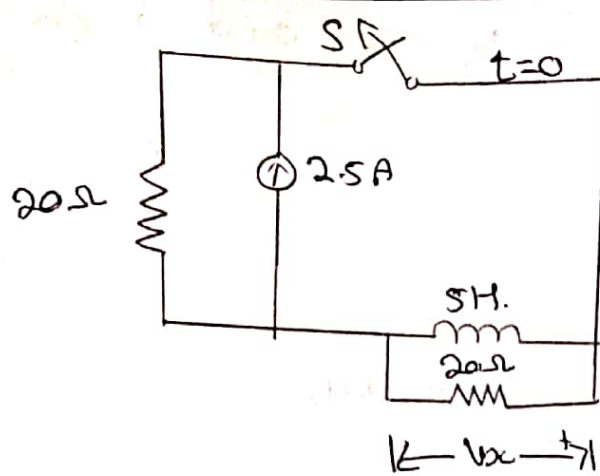8 In figure the switch was closed for a long time before opening at  $t=0$ . The voltage  $V_x$  at  $t=0^+$  will be.



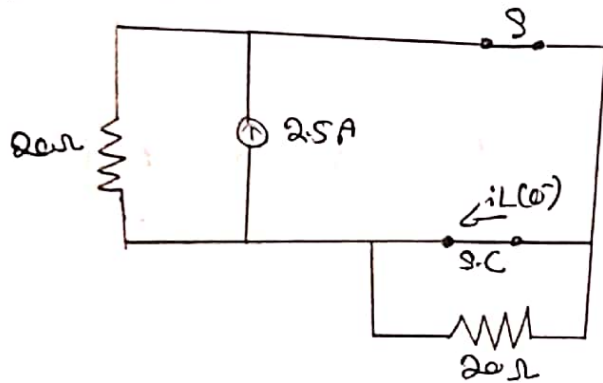(i) At  $t = 0^-$  /  $t < 0$  / steady state:

In steady state, inductor behaves as a short circuit



$$i_L(0^-) = 2.5A$$


From property of inductor.

$$i_L(0^-) = i_L(0^+) = 2.5A$$

ii) At  $t = 0^+$

Inductor is replaced by current source with initial value i.e.

$$i_L(0^-) = i_L(0^+) = 2.5A$$

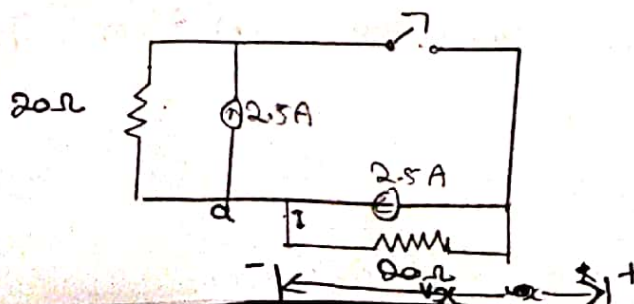

2.5A current will flow through  $20\Omega$  resistor.




Hence,  $I = 2.5A$

11

From ohm's law.

$$V_x = -2.5 \times 20 = -50 \text{ volt}$$

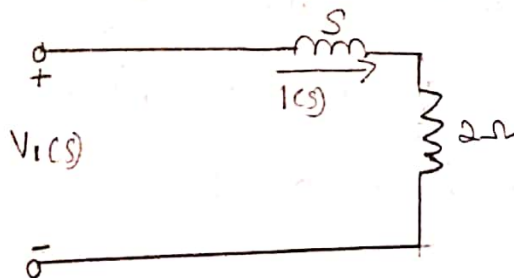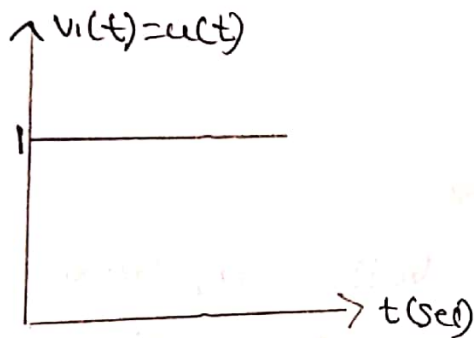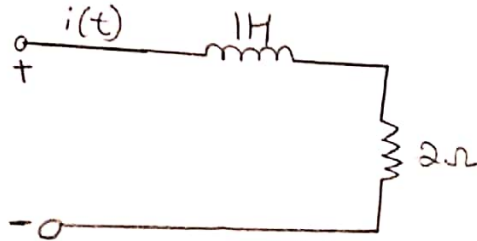11 q For the R-L circuit shown in figure the input voltage  $V_i(t) = u(t)$ . The current  $i(t)$  is



Applying KVL in loop shown,

$$V_i(s) = sI(s) + 2I(s)$$

$$V_i(s) = I(s) [s + 2]$$

$$\text{input} = V_i(t) = u(t) \text{ [Given]}$$

$$V_i(s) = \frac{1}{s}$$

$$\frac{1}{s} = I(s) [s + 2]$$
$$I(s) = \frac{1}{s(s+2)} = \frac{1}{2} \left[ \frac{1}{s} - \frac{1}{s+2} \right]$$

Taking Inverse Laplace transform,

12

$$i(t) = \frac{1}{2} (1 - e^{-2t}) u(t)$$


Time constant,  $\tau = \frac{1}{2}$  sec

$$At = \tau = \frac{1}{2} \text{ sec}$$



$$i(t) = 0.5 [1 - e^{-1}] = 0.31 \text{ A}$$

$$At = \infty,$$
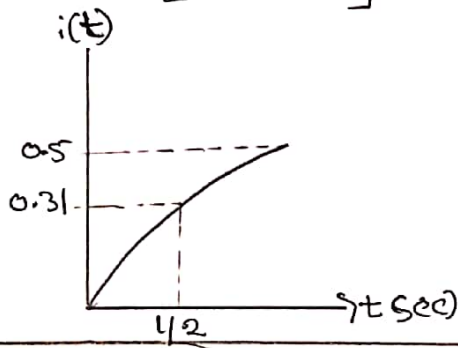
$$i(t) = 0.5 [1 - e^{-2 \times \infty}] = 0.5 \text{ A}$$



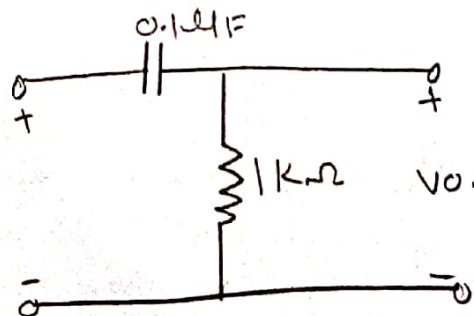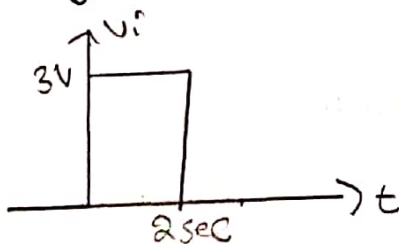- 13 A square pulse of 3 volt amplitude is applied to C-R circuit shown in the figure. The capacitor is initially uncharged. The output voltage  $v_o$  at time  $t = 2$  sec is.





Given:  $R = 1k\Omega$  and  $C = 10\mu F$

13


For an RC network, time constant

$$\tau = RC = 1000 \times 10^{-6} = 100 \mu s$$

Time duration pulse  $T_p = 2 \text{ sec}$

settling time is given by,
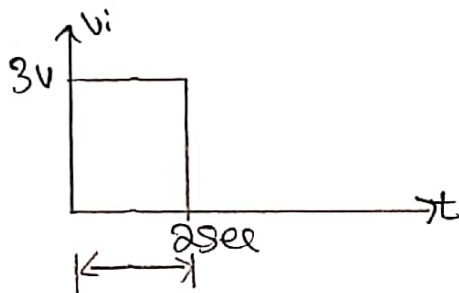
$$t_s = 5\tau = 5 \times 100 = 500 \mu s$$



At settling time, practically circuit will be in steady state


As  $T_p \gg t_s$ , so steady state is reached much before the end of pulse and C behaves as open circuit

$$\text{So; } V_C = V_i = 3V.$$

$$V_C(1.49 \text{ sec}) = 3V.$$

$$V_C(2) = V_C(2^+) = 3V.$$

At  $t = 2/2^+$ :

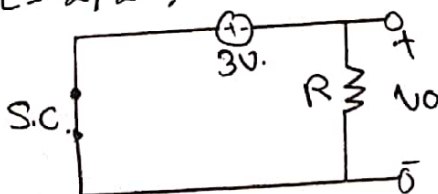

From Figure  
 $0 + 3 + V_o = 0$   
 $V_o = -3V$