

6/08/19

Date _____
Page _____

MODULE: 02

De Morgan's theorem.

$$\text{I law: } \overline{A+B} = \bar{A} \cdot \bar{B}$$

The complement of sum of 2 variables is equal to product of complement of two individual variables

A	B	$A+B$	$\overline{A+B}$	$\bar{A} \cdot \bar{B}$	$\bar{A} \cdot \bar{B}$
0	0	0	1	1	1
0	1	1	0	0	0
1	0	1	0	0	0
1	1	1	0	0	0

$$\text{II law: } \overline{A \cdot B} = \bar{A} + \bar{B}$$

The complement of product of 2 variables is equal to sum of complement of two individual variables

A	B	$A \cdot B$	$\overline{A \cdot B}$	\bar{A}	\bar{B}	$\bar{A} + \bar{B}$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

• Positive and Negative logic code.

- The binary number '0' is for low voltage and binary number '1' is for high voltage and is called positive logic code.
- The binary number '0' is for high voltage and binary number '1' is for low voltage.

and is called negative logic code.

+ve logic.	-ve logic.
$0 \rightarrow \text{LOW}$	$0 \rightarrow \text{HIGH}$
$1 \rightarrow \text{HIGH}$	$1 \rightarrow \text{LOW}$

① Prove +ve AND to -ve OR using truth table.

Soln:

A	B	$A \cdot B$	A	B	$A+B$
0	0	$0 \rightarrow \text{LOW}$	1	1	$1 \rightarrow \text{LOW}$
0	1	$0 \rightarrow \text{LOW}$	1	0	$1 \rightarrow \text{LOW}$
1	0	$0 \rightarrow \text{LOW}$	0	1	$1 \rightarrow \text{LOW}$
1	1	$1 \rightarrow \text{HIGH}$	0	0	$0 \rightarrow \text{HIGH}$

② Prove +ve OR to -ve AND.

Soln:

A	B	$A+B$	A	B	$A \cdot B$
0	0	$0 \rightarrow \text{LOW}$	1	1	$1 \rightarrow \text{LOW}$
0	1	$1 \rightarrow \text{HIGH}$	1	0	$0 \rightarrow \text{HIGH}$
1	0	$1 \rightarrow \text{HIGH}$	0	1	$0 \rightarrow \text{HIGH}$
1	1	$1 \rightarrow \text{HIGH}$	0	0	$0 \rightarrow \text{HIGH}$

③ Prove +ve NOR to -ve NAND.

Soln:

A	B	$A+B$	A	B	$\bar{A} \cdot \bar{B}$
0	0	$1 \rightarrow \text{HIGH}$	1	0	$0 \rightarrow \text{HIGH}$
0	1	$0 \rightarrow \text{LOW}$	1	0	$1 \rightarrow \text{LOW}$
1	0	$0 \rightarrow \text{LOW}$	0	1	$1 \rightarrow \text{LOW}$
1	1	$0 \rightarrow \text{LOW}$	0	0	$1 \rightarrow \text{LOW}$

④ Prove +ve NAND to -ve NOR.


Soln:

A	B	$\bar{A} \cdot \bar{B}$	A	B	$\bar{A}+\bar{B}$
0	0	$1 \rightarrow \text{HIGH}$	1	1	$0 \rightarrow \text{HIGH}$
0	1	$1 \rightarrow \text{HIGH}$	1	0	$0 \rightarrow \text{HIGH}$
1	0	$1 \rightarrow \text{HIGH}$	0	1	$0 \rightarrow \text{HIGH}$
1	1	$0 \rightarrow \text{LOW}$	0	0	$1 \rightarrow \text{LOW}$


V.MP

Prove basic gates using only NAND gate


→ $A \cdot B$

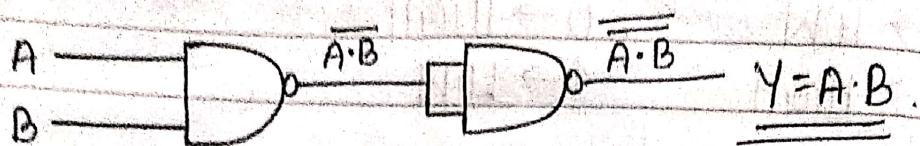

→ $A \rightarrow \bar{A}$

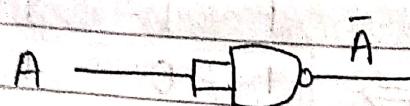

→ $A + B$

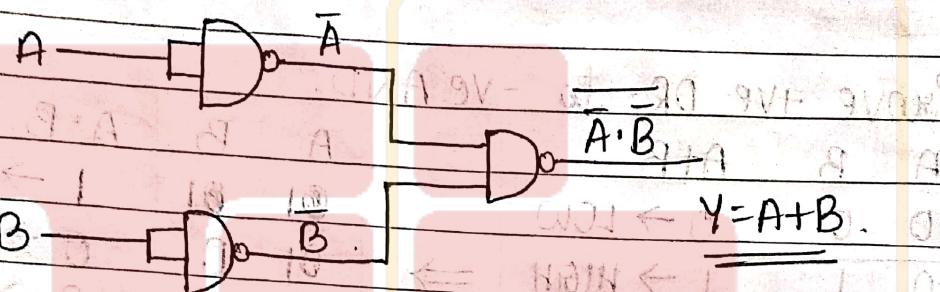

Representation of Combinational logic.

	A	B	C	$C = A$	
0	0	0	0	01 $\rightarrow \overline{ABC}$	
1	0	0	0	10 $\rightarrow \overline{ABC}$	
2	0	0	1	01 $\rightarrow \overline{ABC}$	
3	0	0	1	10 $\rightarrow \overline{ABC}$	
4	1	0	0	0 $\rightarrow A\bar{B}\bar{C}$	
5	1	0	1	1 $\rightarrow A\bar{B}\bar{C}$	
6	1	1	0	0 $\rightarrow A\bar{B}\bar{C}$	
7	1	1	1	1 $\rightarrow A\bar{B}\bar{C}$	

Note:1. Commutative law.

$$A+B = B+A$$

$$AB = BA$$

2. Associative law.

$$(A+B)+C = A+(B+C)$$

$$(AB)C = A(BC)$$

3. De Morgan's law.

$$\overline{A+B} = \overline{A} \cdot \overline{B}$$

$$\overline{AB} = \overline{A} + \overline{B}$$

4. OR operation.

$$A+0 = A$$

$$A+\overline{A} = 1$$

$$A+A = A$$

$$A+1 = 1$$

5. AND Operation.

$$A \cdot 1 = A$$

$$A \cdot 0 = 0$$

$$A \cdot \overline{A} = 0$$

$$\overline{A} = A$$

K-Map.K-Map format.① $F(A, B)$

A \ B	0	1
0	0	1
1	2	3

② $F(A, B, C)$.

A \ B \ C	00	01	10	11
00	0	1	4	5
01	2	3	6	7
10				

③ $F(A, B, C, D)$

		CD	00	01	11	10
		AB	00	01	11	10
00	00	0	1	3	2	
		01	4	5	7	6
11	00	12	13	15	14	
		10	8	9	11	10

Definition of summation (Σ):

Summation symbolises logical OR operation,
i.e. perform on the corresponding min term.

Problems

1) Plot a K-map. Given:

i) $F(A, B) = \sum m(0, 1)$

ii) $F(A, B, C) = \sum m(0, 5, 6, 7)$

iii) $F(A, B, C, D) = \sum m(0, 4, 5, 6, 8, 10, 12, 13, 14, 15)$

i)

		B	0	1
		A	0	1
0	0	0	1	1
		1	2	3

ii)

		CD	00	01	11	10
		AB	00	01	11	10
00	00	0	1	1	1	
		01	2	3	1	1
11	00	12	13	15	14	
		10	6	7	5	4

iii)

		CD	00	01	11	10
		AB	00	01	11	10
00	00	0	1	3	2	
		01	4	5	7	6
11	00	12	13	15	14	
		10	8	9	11	10

i) Find the minimum of the following boolean function using Kmap.

i) $F(A,B,C,D) = \sum m(14,15)$.

AB \ CD		00	01	11	10	
00	0 ₀	0 ₁	0 ₂	0 ₃		$\gamma = ABCD + ABC\bar{D}$
01	0 ₄	0 ₅	0 ₇	0 ₆		$= ABC(D + \bar{D})$
11	0 ₁₂	0 ₁₃	1 ₁₅	1 ₁₄	$\rightarrow Y$	$\underline{\underline{\gamma = ABC}}$
10	0 ₈	0 ₉	0 ₁₁	0 ₁₀		

ii) $F(A,B,C,D) = \sum m(3,7)$.

AB \ CD		00	01	11	10	
00	0 ₀	0 ₁	1 ₃	0 ₆		$\gamma = \bar{A}CD$
01	0 ₄	0 ₅	1 ₇	0 ₆		$\gamma = \bar{A}C\bar{D}$
11	0 ₁₂	0 ₁₃	0 ₁₅	0 ₁₄		$\gamma = \bar{A}\bar{C}D + A\bar{C}\bar{D}$
10	0 ₈	0 ₉	0 ₁₁	0 ₁₀		

iii) $F(A,B,C,D) = \sum m(5,7,8,12)$.

AB \ CD		00	01	11	10	
00	0 ₀	0 ₁	0 ₃	0 ₁₂		$\gamma = (0,1,2,3) \oplus (5,7,8,12)$
01	0 ₄	1 ₅	1 ₇	0 ₆	$\rightarrow Y_1$	$\gamma_1 = \bar{A}CD + \bar{A}C\bar{D}$
11	1 ₁₂	0 ₁₃	0 ₁₅	0 ₁₄		
10	1 ₈	0 ₉	0 ₁₁	0 ₁₀		

$\gamma = Y_1 + Y_2$

$\underline{\underline{\gamma = A\bar{C}D + \bar{A}BD}}$

iv) $F(A,B,C,D) = \sum m(5,7,13,15)$.

AB \ CD		00	01	11	10	
00	0 ₀	0 ₁	0 ₃	0 ₂		$\gamma = BD$
01	0 ₄	1 ₅	1 ₇	0 ₆		$\gamma = BD$
11	0 ₁₂	1 ₁₃	1 ₁₅	0 ₁₄		$\gamma = BD$
10	0 ₈	0 ₉	0 ₁₁	0 ₁₀		

$$V) F(A, B, C, D) = \sum m(4, 5, 6, 7, 12, 13, 14, 15)$$

AB\CD	00	01	11	10	
00	0	0	0	0	
01	1	1	1	1	$\rightarrow y_1$
11	1	1	1	1	$\rightarrow y_2$
10	0	0	0	0	

$$Y = \bar{A}B\bar{C}\bar{D} + A\bar{B}\bar{C}D + \bar{A}BcD + \bar{A}BC\bar{D} + AB\bar{C}\bar{D}$$

$$AB\bar{C}D + ABCD + AB\bar{C}D$$

$$Y = \bar{A}B(\bar{C}\bar{D} + \bar{C}D + CD + C\bar{D}) + AB(\bar{C}\bar{D} + \bar{C}D + CD + C\bar{D})$$

$$Y = \bar{A}B(C \oplus D + \bar{C} \oplus D) + AB(C \oplus D + \bar{C} \oplus D)$$

$$= \bar{A}B + AB$$

$$= B(\bar{A} + A)$$

08/08/19

$$\underline{\underline{Y = B}}$$

$$vi) F(A, B, C, D) = \sum m(1, 2, 3, 8, 9, 10, 14, 16, 12, 13)$$

AB\CD	00	01	11	$\rightarrow y_3$	10	
00	0	1	1		2	
01	0	0	0	1	6	$\rightarrow y_2$
11	1	1	0	1	7	$\rightarrow y_1$
10	1	1	0	1	10	

$$Y = Y_1 + Y_2 + Y_3$$

$$Y = \bar{A}\bar{C} + \bar{C}\bar{D} + \bar{A}\bar{B}D.$$

vii) $F(A, B, C, D) = \sum m(0, 1, 2, 4, 5, 6, 12, 10, 8, 9)$

AB'CD'	AB'CD	ABC'D'	ABC'D	AB'CD'	AB'CD	ABC'D'	ABC'D	AB'CD'	AB'CD	ABC'D'	ABC'D
00	1	1	1	1	1	1	1	1	1	1	1
01	1	1	1	1	1	1	1	1	1	1	1
11	1	1	1	1	1	1	1	1	1	1	1
10	1	1	1	1	1	1	1	1	1	1	1

$$Y = Y_1 + Y_2 + Y_3$$

$$= \bar{C} + \bar{A}\bar{D} + \bar{B}\bar{D}$$

viii)
last year
question

Find the minimal of the SOP expression.


Given; $F(A, B, C, D) = \sum m(1, 3, 5, 7, 8, 10, 12, 14)$

Realise this function using NAND gate only.

AB'CD'	AB'CD	ABC'D'	ABC'D	AB'CD'	AB'CD	ABC'D'	ABC'D	AB'CD'	AB'CD	ABC'D'	ABC'D
00	1	1	1	1	1	1	1	1	1	1	1
01	1	1	1	1	1	1	1	1	1	1	1
11	1	1	1	1	1	1	1	1	1	1	1
10	1	1	1	1	1	1	1	1	1	1	1

$$Y = Y_1 + Y_2$$

$$Y = A\bar{D} + \bar{A}D$$

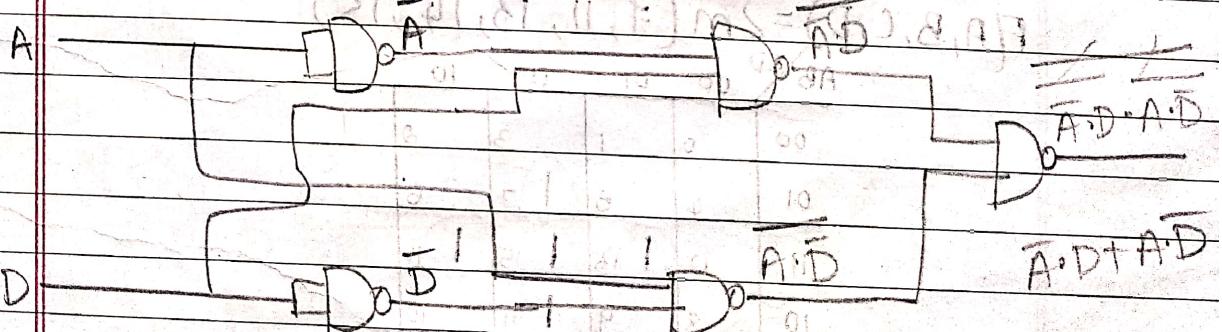

**

V.D.P.
S.Y.S.

10 m

- ix) A system has 4 inputs, the output is high only when the majority of the inputs are high. * Give truth table & simplify using Kmap. * Write the expression in summation of minterms.

* Implement the simplified equation using a NAND gate.

Soln:

	3	4	2	1	y
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	0
4	0	1	0	0	0
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	1
8	1	0	0	0	0
9	1	0	0	1	0
10	1	0	1	0	0
11	1	0	1	1	1
12	1	1	0	0	0
13	1	1	0	1	1
14	1	1	1	0	1
15	1	1	1	1	1

$$F(A, B, C, D) = \sum m(7, 11, 13, 14, 15)$$

AB	CD	00	01	11	10	11	
00		0		1	3	2	$\rightarrow y_1$
01		4		5	1	7	$\rightarrow y_2$
11		12	13	1	15	14	$\rightarrow y_3$
10		8	9	1	11	10	

$$Y = y_1 + y_2 + y_3 + y_4$$

$$Y = BCD + ABC + ACD + ABD$$

A	B	C	D	
0	0	0	0	BCD
0	0	0	1	ABC
0	0	1	0	ACD
0	0	1	1	ABD
1	0	0	0	
1	0	0	1	
1	0	1	0	
1	0	1	1	
1	1	0	0	
1	1	0	1	
1	1	1	0	
1	1	1	1	

Product of Sum (POS)

①

Simplify the following boolean function using

$$F(A, B, C, D) = \sum m(0, 1, 2, 3, 4, 5, 7) \quad \text{POS form:}$$

Solu:

$$F(A, B, C, D) = \prod M(6, 8, 9, 10, 11, 12, 13, 14, 15)$$

AB \ CD	00	01	11	10	
00	0	1	3	2	
01	4	5	7	6	
11	0	0	0	0	
10	12	13	15	14	
	8	9	11	10	$\rightarrow y_2$

$$\begin{aligned} Y &= y_1 + y_2 \\ &= BCD + A \cdot (\text{SOP exp}) \end{aligned}$$

POS expression:

$$y = \bar{A}(\bar{B} + \bar{C} + D)$$

13/08/19

② Simplify the given Boolean function using K map method and express in SOP form. Realize logic circuit using NAND gate only and also simplify the expression in POS form.

$$F(A, B, C, D) = \sum m(7, 9, 10, 11, 12, 13, 14, 15)$$

Solution:

$$F(A, B, C, D) = \sum m(7, 9, 10, 11, 12, 13, 14, 15)$$

AB \ CD	00	01	11	10	
00	0	1	3	2	$\rightarrow y_4$
01	4	5	7	6	$\rightarrow y_1$
11	1	1	1	1	$\rightarrow y_3$
10	12	13	15	14	$\rightarrow y_2$
	8	9	11	10	

$$\begin{aligned} Y &= y_1 + y_2 + y_3 + y_4 \\ &= AB + AC + AD + BCD \end{aligned}$$

$$F(A, B, C, D) = \prod M(1, 2, 3, 4, 5, 6, 8)$$


AB \ CD	00	01	11	10	
00	0	0	0	0	$\rightarrow y_2$
01	0	0	0	0	$\rightarrow y_3$
11	12	13	15	14	$\rightarrow y_1$
10	0	0	0	0	$\rightarrow y_4$
	8	9	11	10	

$$Y = y_1 + y_2 + y_3 + y_4$$

$$Y = \bar{A}(\bar{C} + \bar{AB} + \bar{AD} + \bar{BCD})$$

Realizing using NAND gate

$$Y = AB + AC + AD + BCD$$

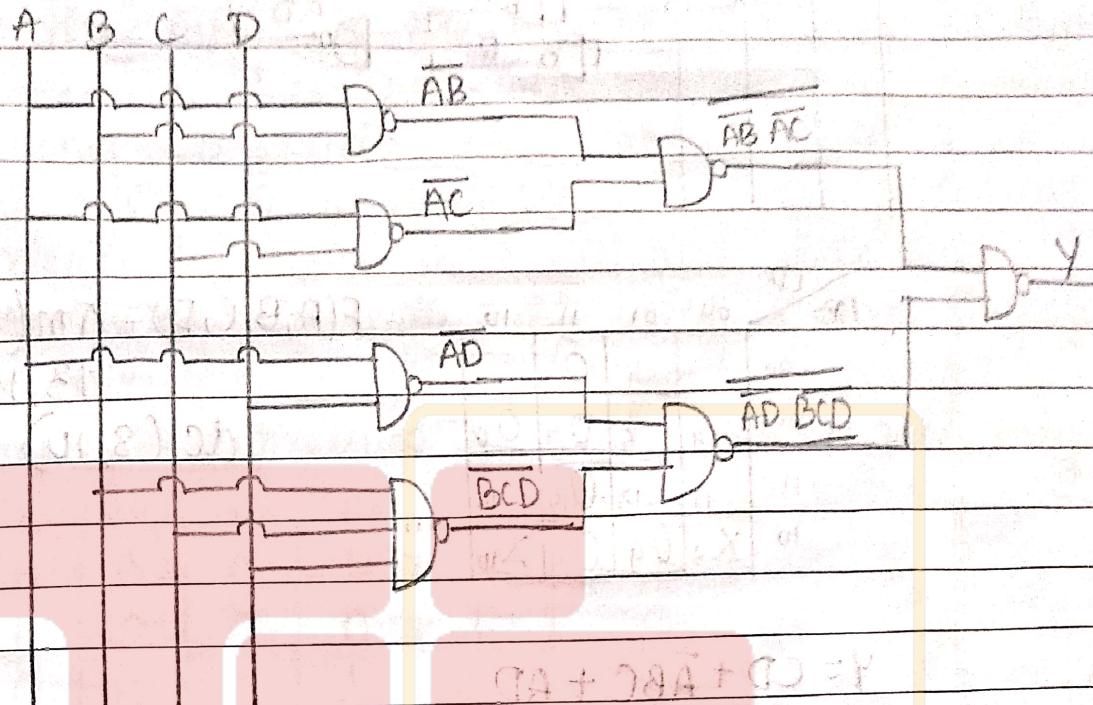

$$QA + 28\bar{A} + G2 = F$$

$$(Q + \bar{A})(\bar{G} + \bar{A} + A)(\bar{G} + \bar{I}) = F$$


Don't Care Condition

- ① Using K-map Simplify the following boolean expression and give implementation for the same
1. SOP form - (NAND gate only)
 2. POS form - (NOR gate only)

$$F(A, B, C, D) = \sum m(0, 1, 2, 4, 5, 12, 14) + dc(8, 10).$$


		CD		00		01		11		10		
		A	B	00	01	11	10	00	01	11	10	
				1	0	1	1	3	1	2		$\rightarrow y_3$
				0	1	1	0	5	7	6		
				1	1	0	1	12	13	15	14	
				10	X ₈	9	11	X ₁₀				$\rightarrow y_2$
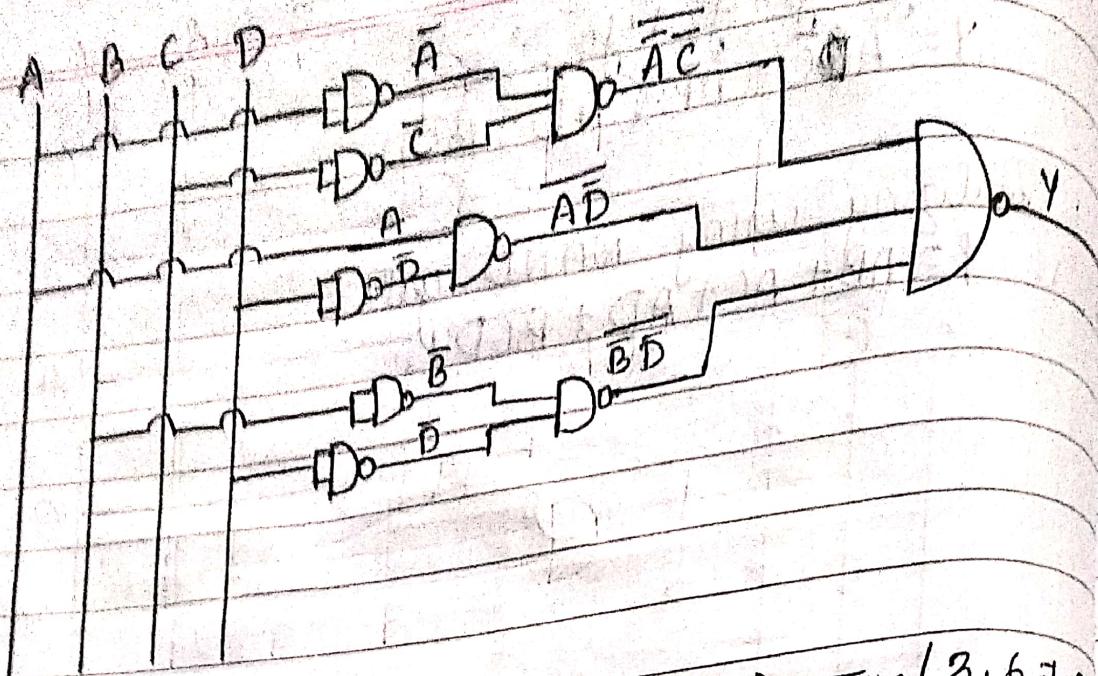
$$Y = \bar{A}\bar{C} + \bar{A}\bar{D} + \bar{B}\bar{D}$$



$AB \backslash CD$	00	01	11	10	$\rightarrow y_1$	$F(A, B, C, D) = \pi m(3, 6, 7, 9, 13, 15)$
00	0	1	0 ₃	2	$\rightarrow y_2$	dc (8, 10)
01	4	5	0 ₇	0 ₆	$\rightarrow y_3$	
11	12	0 ₁₃	0 ₁₅	14		
10	X ₈	0 ₉	0 ₁₁	X ₁₀		
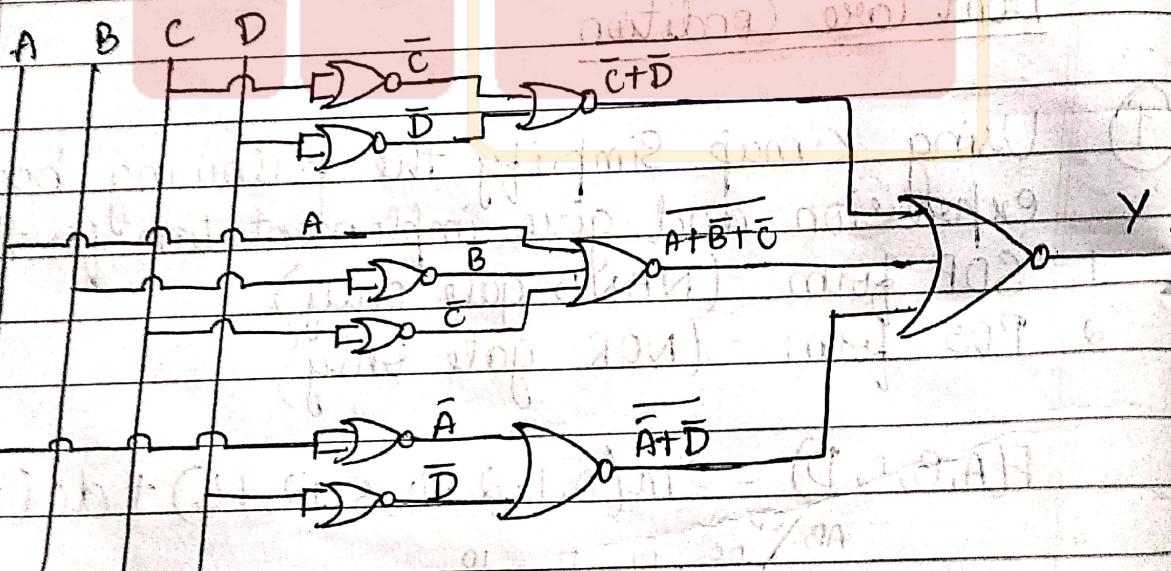
$$\begin{aligned}
 Y &= CD + \bar{A}BC + AD \\
 &= (\bar{C} + \bar{D})(A + \bar{B} + \bar{C})(\bar{A} + \bar{D}) \quad [\text{POS}]
 \end{aligned}$$



V.V. JMD

② A digital system is to be designed in which the month of the year is given as input in 4-bit form. The month January is represented as "0 0 0 0" & February is "0 0 0 1" and so on. The output of the system should be 1 corresponding to the input of the month containing 31 days otherwise it is 0. Consider the excess no. of input beyond "1011" as don't care condition, for the system of 4 variable. Find the following boolean expression and ΣM and max term form. Write the truth table using K-map. Simplify the expression in min term form. Implement simplified expression in NAND-NAND gate only.

Soln:-


s	4	3	2	1	y
0J	0	0	0	0	1
1F	0	0	0	1	0
2M	0	0	1	0	1
3A	0	0	1	1	0
4M	0	1	0	0	1
5J	0	1	0	1	0
6J	0	1	1	0	1
7A	0	1	1	1	1
8S	1	0	0	0	0
9O	1	0	0	1	1
10N	1	0	1	0	0
11D	1	0	1	1	1
12	1	1	0	0	x
13	1	1	0	1	x
14	1	1	1	0	x
15	1	1	1	1	x

$$\text{POS} \Rightarrow F(A, B, C, D) = \sum m(0, 2, 4, 6, 7, 9, 11) + \\ d(\bar{m}(12, 13, 14, 15))$$

AB\CD	00	01	11	10	
00	1	0	1	1	y_3
01	1	4	5	7	y_1
11	X	X	X	X	y_2
10	12	13	15	14	
08	1	1	11	10	
09	1	1	10	10	

$$Y = Y_1 + Y_2 + Y_3$$

$$Y = BC + AD + \bar{A}\bar{D}$$

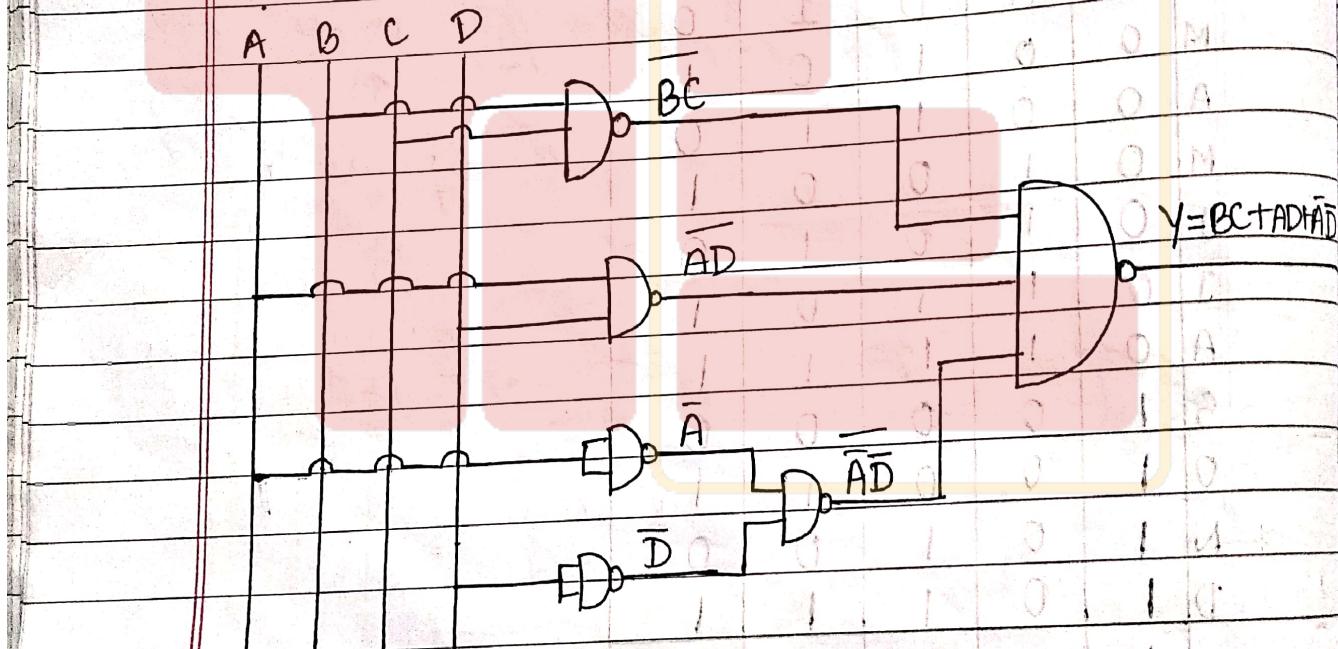


$$\text{SOP} \Rightarrow F(A, B, C, D) = \prod M(1, 3, 5, 8, 10) + \text{dc}(12, 13, 14, 15)$$

	AB	CD	00	01	11	10	
00	0	0	0	3	2		$\rightarrow y_3$
01	4	0	5	7	6		$\rightarrow y_2$
11	X	X	X	X	X	X	
10	0	8	9	11	0	10	$\rightarrow y_0$

$$Y = Y_1 + Y_2 + Y_3$$

$$= \bar{A}\bar{D} + A\bar{C}D + \bar{A}\bar{B}D$$
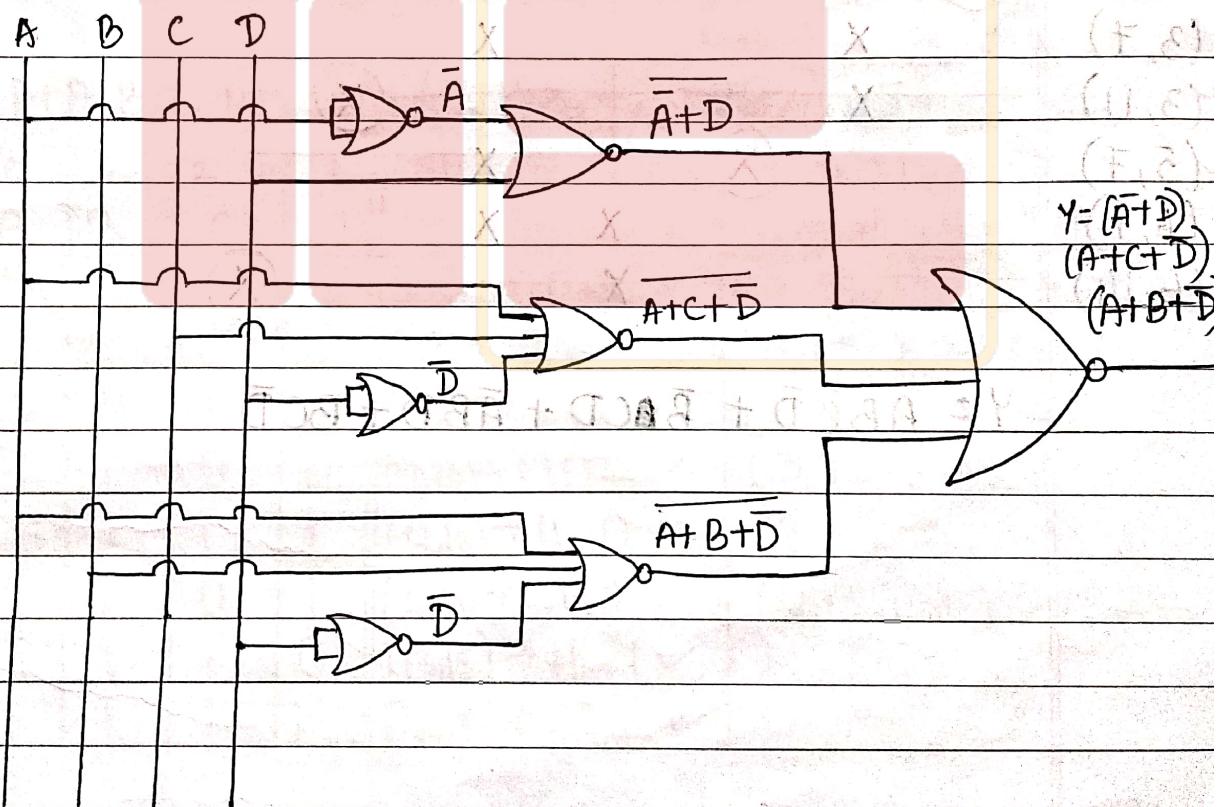
$$= (\bar{A} + \bar{D})(A + C + \bar{D})(A + B + \bar{D})$$



Quine - McClusky.


$$\textcircled{1} \quad F(A, B, C, D) = \sum m(0, 3, 5, 6, 7, 11, 14)$$

	STEP 1				STEP 2
	A	B	C	D	
0	0	0	0	0	$0 \rightarrow 0000$
3	0	0	1	1	$(3, 7) \rightarrow 0-11$
5	0	1	0	1	$(3, 11) \rightarrow -011$
6	0	1	1	0	$(5, 7) \rightarrow 01-1$
7	0	1	1	1	$(6, 7) \rightarrow 011-$
11	1	0	1	1	$(6, 14) \rightarrow -110$
14	1	1	1	0	

Prime Representation:

	0	3	5	6	7	11	14
✓ 0	(X)						
(3, 7)		X					
(3, 11)		X					
✓ (5, 7)			(X)		X		
(6, 7)				X	X		
✓ (6, 14)				X			(X)
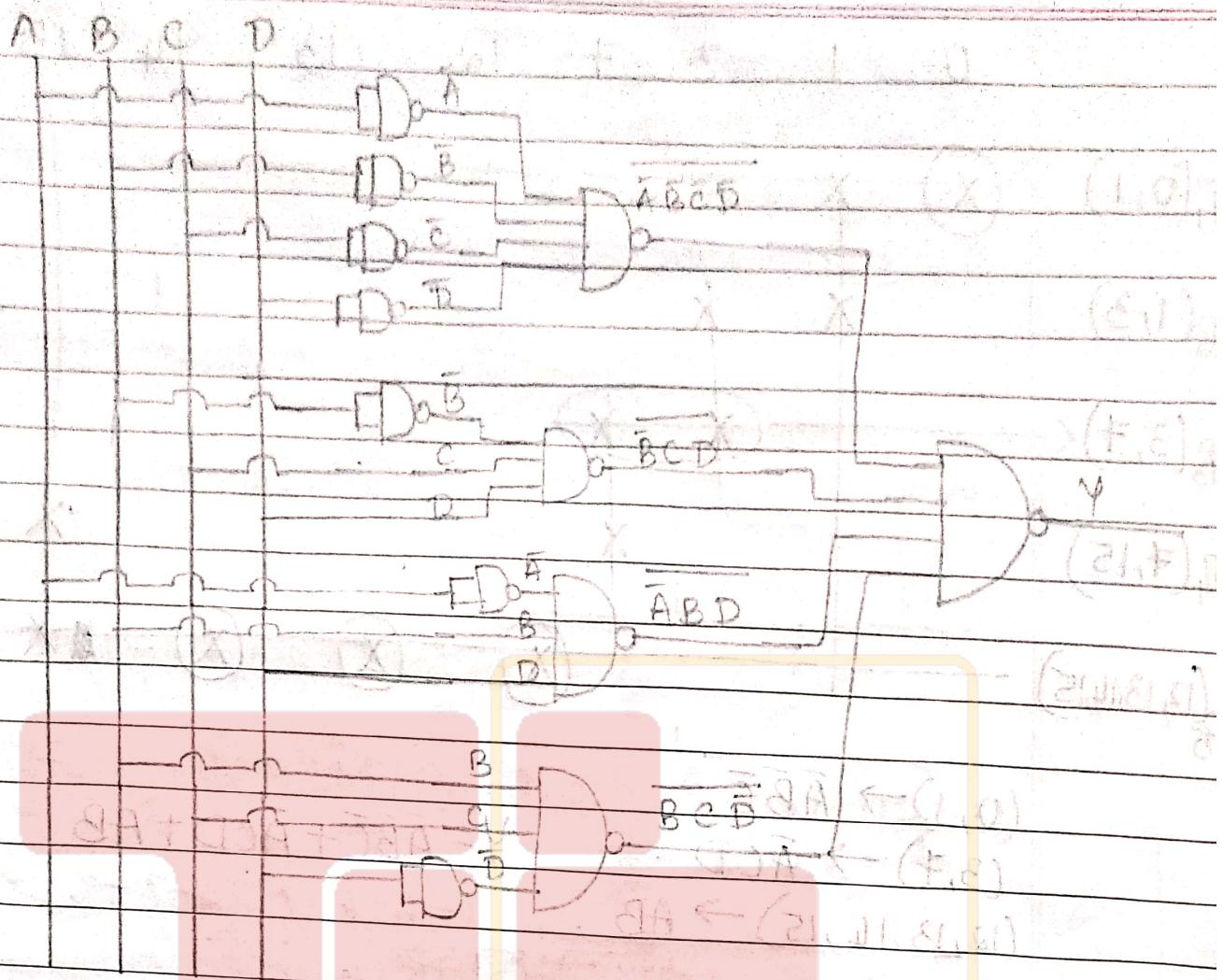
$$Y = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{B}CD + \bar{A}BD + BCD$$




19/08/19

②

$$F(A, B, C, D) = \sum m(0, 1, 3, 7, 12, 13, 14, 15)$$

	8	4	2	1	STEP: 2	STEP: 3
A	B	C	D			
0	0	0	0	0	$(0,1) \rightarrow 000\cancel{X}$	$(12,13,14,15) \rightarrow 11--$
1	0	0	0	1	$(1,3) \rightarrow 00\cancel{1}1$	$(12,14,13,15) \rightarrow 11--$
3	0	0	1	1	$(3,7) \rightarrow 0-11$	$(0,1) \rightarrow 000-$
7	1	1	0	0	$(12,13) \rightarrow 110-$	$(1,3) \rightarrow 00-1$
12	0	1	1	1	$(12,14) \rightarrow 11-0$	$(3,7) \rightarrow 0-11$
13	1	1	0	1	$(7,15) \rightarrow -111$	$(9,15) \rightarrow -111$
14	1	1	1	0	$(13,15) \rightarrow 11-1$	$(12,13,14,15) \rightarrow 11--$
15	1	1	1	1	$(14,15) \rightarrow 111\cancel{1}$	$\cancel{1} = 000 + 001$

0 1 3 ≠ 12 13 14 15

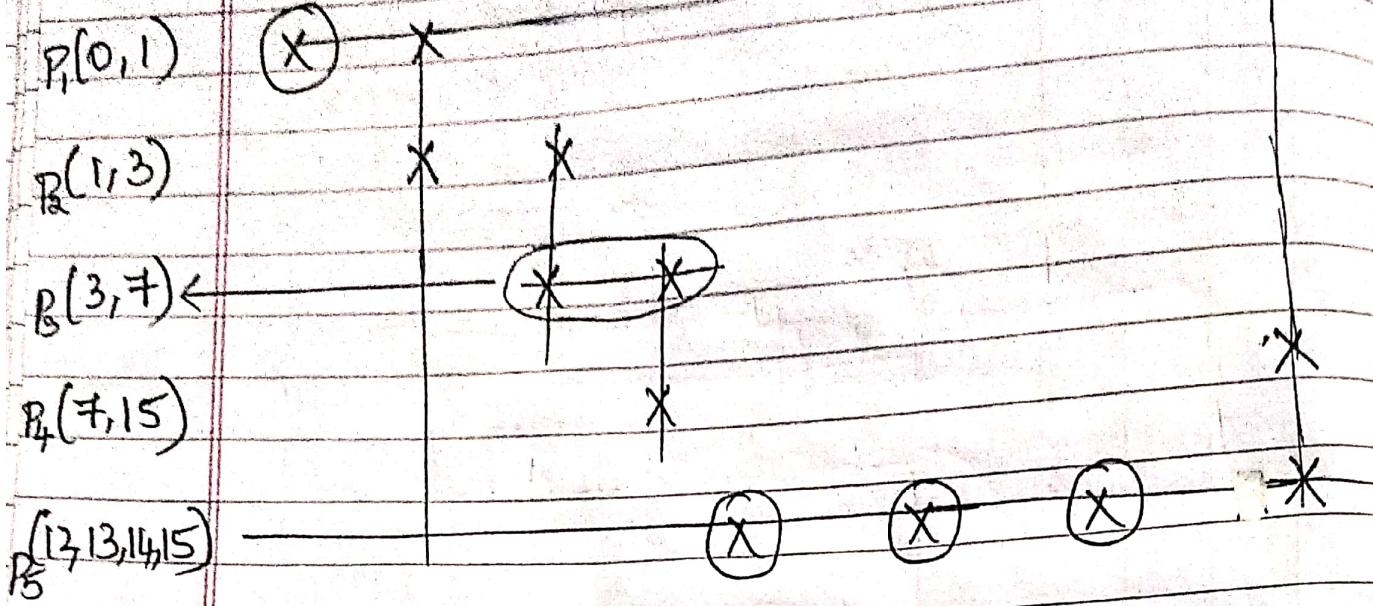

$$(0, 1) \rightarrow \bar{A}\bar{B}\bar{C}$$

$$(3, \neq) \rightarrow \bar{A}CD$$

$$(12, 13, 14, 15) \rightarrow AB$$

$$Y = \bar{A}\bar{B}\bar{C} + \bar{A}CD + AB$$

$$Y = (A+B+C)(A+\bar{C}+\bar{D})(\bar{A}+B)$$

→ POS

→ SOP

NO

Petrie method:

$$\Rightarrow (x+y)(x+z) = (x+yz) \quad \text{LHS} = (T, 0, 0, 1) \neq$$

$$\text{LHS} = (x+y)(x+z)$$

$$x+xz+xy+yz$$

$$x(1+y)+xz+yz$$

$$x+xz+yz$$

$$x(1+z)+yz$$

$$\text{RHS} = (x+yz)$$

$$(P_1+P_2)(P_2+P_3)(P_3+P_4)(P_4+P_5) = 1$$

$$(P_2+P_1P_3)(P_4+P_3P_5) = 1$$


$$P_2P_4 + P_1P_3P_4 + P_2P_3P_5 + P_1P_3P_5 = 1$$

$$P_2P_4 + P_2P_3P_5 = 1$$

$$③ F(A, B, C, D) = \sum m(0, 1, 2, 3, 5, 8, 12, 14, 15)$$

	STEP:1				STEP:2				STEP:3			
	A	B	C	D								
0	0	0	0	0	(0,1)	→	000-		(0,1,2,3)	→	00--	✓
1	0	0	0	1	(0,2)	→	00-0		(0,2,1,3)	→	0D--	X
2	0	0	1	0	(0,8)	→	-000		(0,8)	→	-000	
8	1	0	0	0	(1,3)	→	00-1		(1,5)	→	0_01	
3	0	0	1	1	(1,5)	→	0-01		(8,12)	→	1_-00	
5	0	1	0	1	(2,3)	→	D01-		(12,14)	→	11-0	
12	1	1	0	0	(8,12)	→	1_-00		(14,15)	→	111-	
14	1	1	1	0	(12,14)	→	11-0					
15	1	1	1	1	(14,15)	→	111-					

$$0 = 1 + 2 + 3 + 5 + 8 + 12 + 14 + 15$$

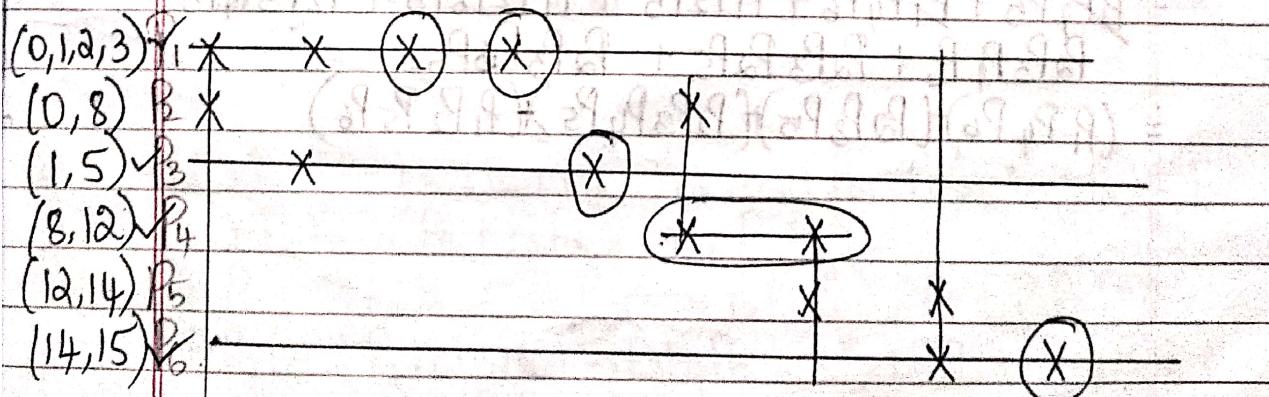

$$(0, 1, 2, 3) \rightarrow \bar{A}\bar{B}$$


$$Y = \bar{A}\bar{B} + \bar{A}\bar{C}D + A\bar{C}\bar{D} + ABC$$

$$(1, 5) \rightarrow \bar{A}\bar{C}D$$

$$(8, 12) \rightarrow A\bar{C}\bar{D}$$

$$(14, 15) \rightarrow ABC$$

A B C D

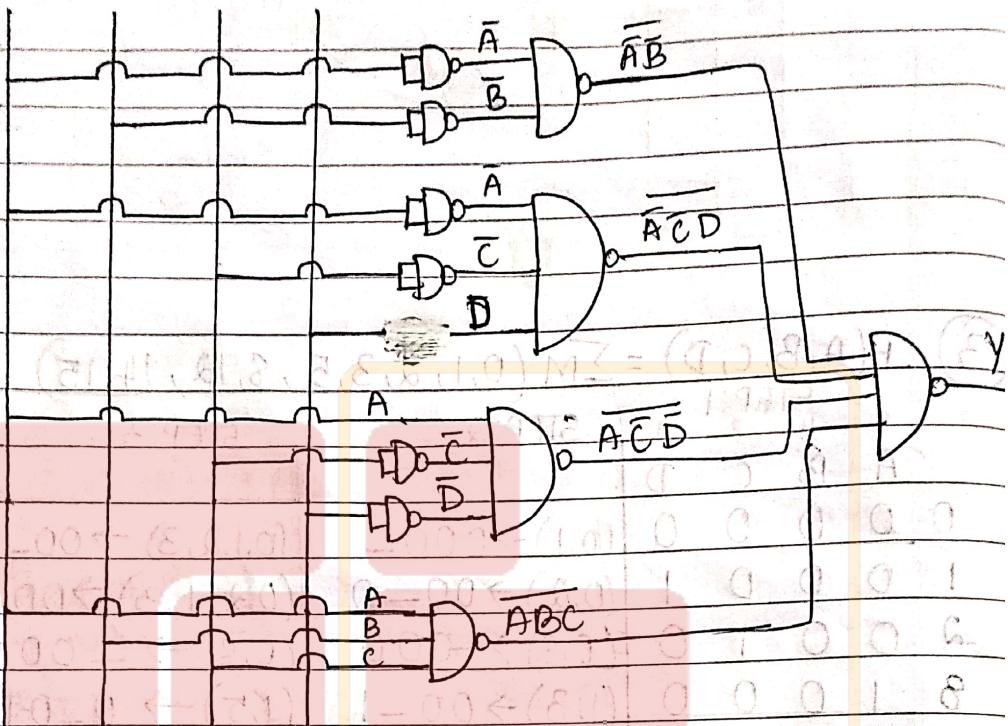

Petrie's method:

$$(P_1 + P_2)(P_1 + P_3)(P_2 + P_4)(P_4 + P_5)(P_5 + P_6) = 1$$

~~$$(P_1 + P_2 P_3 + P_1 P_2 + P_2 P_3)$$~~

$$(P_1 + P_2 P_3)(P_4 + P_2 P_5)(P_5 + P_6) = 1.$$

$$= (P_1 + P_2 P_3)(P_4 P_5 + P_4 P_6 + P_2 P_5 + P_2 P_6 P_5) = 1.$$

$$= P_1 P_4 P_5 + P_1 P_4 P_6 + P_1 P_2 P_5 + P_1 P_2 P_6 P_5 + P_2 P_3 P_4 P_5 +$$

~~$$P_2 P_3 P_4 P_6 + P_2 P_3 P_2 P_5 + P_2 P_3 P_4 P_5$$~~

$$= (P_1 P_4 P_6) \bar{H} (P_2 P_3 P_5) \bar{H} (P_2 P_3 P_4 P_5) \bar{H} (P_1 P_2 P_5 P_6)$$

28/08/19

classmate

Date _____
Page _____

4

$$F = \sum M(0,1,2,5,6,7)$$

min

$\sum m$

Step: 1

	4	2	1	
	A	B	C	
0	0	0	0	$(0,1) \rightarrow 00-$
1	0	0	1	$(0,2) \rightarrow 0-0$
2	0	1	0	$(1,5) \rightarrow -01$
5	1	0	1	$(2,6) \rightarrow 10-$
6	1	1	0	$(5,7) \rightarrow 1-1$
7	1	1	1	$(6,7) \rightarrow 11-$

Step: 2

$$0 \quad 1 \quad 2 \quad 5 \quad 6 \quad 7 \quad F = \sum M(0,1,2,5,6,7)$$

$$P_1 \checkmark (0,1) \quad * \quad *$$

$$P_2 \quad (0,2) \quad X \quad X$$

$$P_3 \quad (1,5) \quad X \quad |$$

$$P_4 \checkmark (2,6) \quad * \quad | \quad X$$

$$P_5 \checkmark (5,7) \quad * \quad | \quad X$$

$$P_6 \quad (6,7) \quad (F,7) \quad -1 \quad 0 \quad X \quad X$$

$$(0,1) \rightarrow \bar{A}\bar{B}$$

$$(2,6) \rightarrow B\bar{C}$$

$$(5,7) \rightarrow AC$$

$$Y = \bar{A}\bar{B} + B\bar{C} + AC.$$

	0	1	
00	1	0	4
01	0	1	5
11	3	1	7
10	1	2	6

$$Y = \bar{A}\bar{B} + B\bar{C} + AC.$$

$$(P_1 + P_2)(P_1 + P_3)(P_2 + P_4)(P_3 + P_5)(P_4 + P_6)(P_5 + P_6) = 1$$

$$(P_1 + P_2 P_3)(P_4 + P_2 P_6)(P_5 + P_3 P_6) = 1$$


$$(P_1 P_4 + P_1 P_2 P_6 + P_2 P_3 P_4 + P_2 P_3 P_6) / (P_5 + P_3 P_6) = 1$$

$$(P_1 P_4 P_5 + P_1 P_2 P_5 P_6 + P_2 P_3 P_4 P_5 + P_2 P_3 P_5 P_6 + P_1 P_4 P_3 P_6 + P_1 P_2 P_6 P_3 + P_2 P_3 P_4 P_6 + P_2 P_3 P_6) = 1$$

$$P_1 P_4 P_5 + P_1 P_2 P_5 P_6 + P_2 P_3 P_4 P_5 + P_1 P_3 P_4 P_6 + P_2 P_3 P_6 = 1$$

$$P_1 P_4 P_5 + P_1 P_2 P_5 P_6 + P_2 P_3 P_4 P_5 + P_1 P_3 P_4 P_6 + P_2 P_3 P_6 = 1$$

A B C.

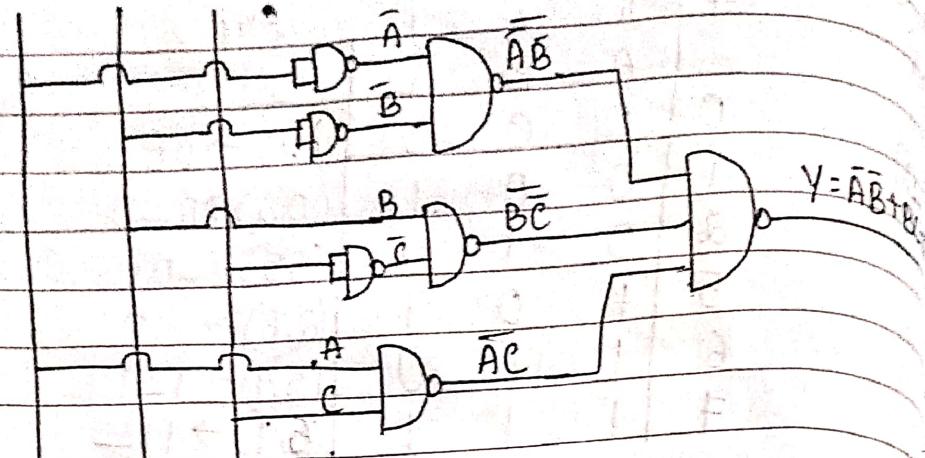

$$(5) \quad F = \sum M(1, 2, 5, 6, 7, 13, 15)$$

Step 1

Step 2

Step 3

S	A	B	C	D		
1	0	0	0	1	(1,5) $\rightarrow 0-01$	(5,1,13,15) $\rightarrow -1-$
2	0	0	1	0	(2,6) $\rightarrow 0-10$	(5,13,7,15) $\rightarrow -1-$
5	0	1	0	1	(5,7) $\rightarrow 01-1$ ✓	(1,5) $\rightarrow 0-01$
6	0	1	1	0	(5,13) $\rightarrow -101$ ✓	(2,6) $\rightarrow 0-10$
7	0	1	1	1	(6,7) $\rightarrow 011-$	(6,7) $\rightarrow 011-$
13	1	1	0	1	(7,15) $\rightarrow -111$ ✓	
15	1	1	1	1	(13,15) $\rightarrow 11-1$ ✓	

(5,13,7,15) \leftarrow (1,0)
1 2 5 6 7 13 15 \leftarrow (2,0)

(5,13,7,15) ✓	X	X	X	X	P ₁
(1,5) ✓	(X)	X			P ₂
(2,6) ✓	(X)	X	X		P ₃
(6,7).		X	X		P ₄

$$Y = BD + \bar{A}\bar{C}D + \bar{A}CD$$


$$(P_1 + P_4)(P_3 + P_4) + (P_1 + P_2) = 1$$

$$(P_4 + P_1 P_3) + (P_1 + P_2) = 1$$

$$P_4 + P_1 + P_4 P_2 + P_1 P_3 + P_1 P_2 P_3 = 1$$

$$+ P_2 P_3 + P_2 P_3 P_4 = 1$$

A B C D

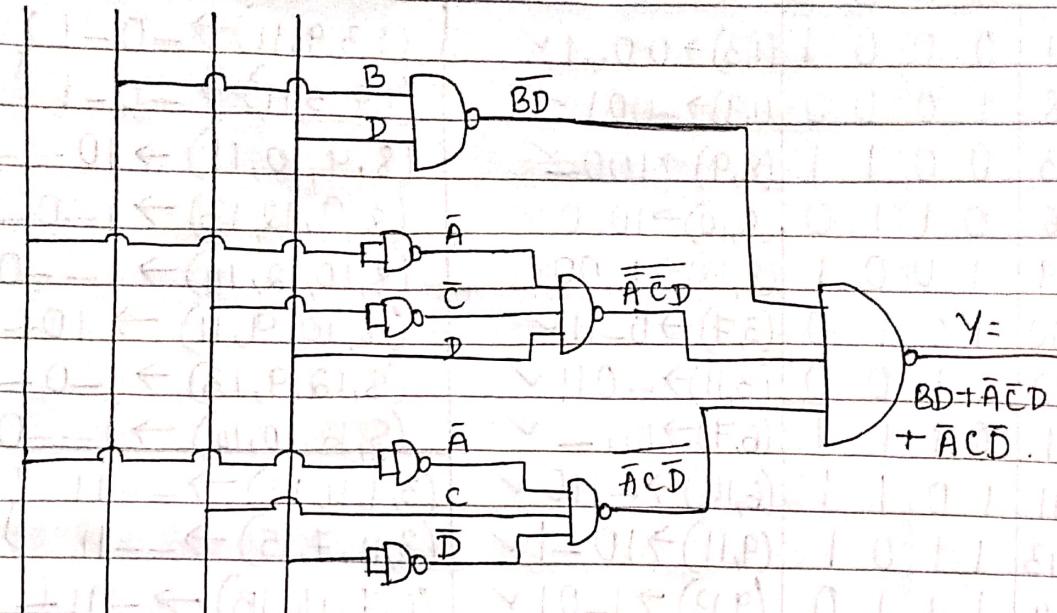K-map verification:

		CD	00	01	11	10
		AB	00	01	11	10
CD	AB	00	0	1	3	12
		01	4	5	7	16
CD	AB	11	12	13	15	14
		10	8	9	11	10

24/08/14 $Y = BD + \bar{A}\bar{C}D + \bar{A}\bar{C}\bar{D}$

(6) $F(A, B, C, D) = \sum m(1, 3, 6, 7, 8, 9, 10, 12, 14, 15) + d(11, 13)$.

20-M

		CD	00	01	11	10
		AB	00	01	11	10
CD	AB	00	0	1	1	12
		01	4	5	7	16
CD	AB	11	1	X	1	14
		10	12	13	15	10
			8	9	X	10

A

STEP-1.

	A	B	C	D	STEP:2
1	0	0	0	1	(1,3) \rightarrow 00-1 ✓
8	1	0	0	0	(1,9) \rightarrow -001 ✓
3	0	0	1	1	(8,9) \rightarrow 100- ✓
6	0	1	1	0	(8,10) \rightarrow 10-0 ✓
9	1	0	0	1	(8,12) \rightarrow 1-00 ✓
10	1	0	1	0	(3,7) \rightarrow 0-11 ✓
12	1	1	0	0	(3,11) \rightarrow -011 ✓
7	0	1	1	1	(6,7) \rightarrow 011- ✓
11	1	0	1	1	(6,14) \rightarrow -110 ✓
13	1	1	0	1	(9,11) \rightarrow 10-1 ✓
14	1	1	1	0	(9,13) \rightarrow 1-01 ✓
15	1	1	1	1	(10,11) \rightarrow 101- ✓ (10,14) \rightarrow 1-10 ✓ (12,13) \rightarrow 110- ✓ (12,14) \rightarrow 11-0 ✓ (7,15) \rightarrow -111 ✓ (11,15) \rightarrow 1-11 ✓ (13,15) \rightarrow 11-1 ✓ (14,15) \rightarrow 111- ✓

STEP:3

$(1,3,9,11) \rightarrow -0-1\}$
 $(1,9,3,11) \rightarrow -0-1\}$
 $(8,9,10,11) \rightarrow 10--$
 $(8,9,12,13) \rightarrow 1-0-$
 $(8,10,12,14) \rightarrow 1--0$
 $(8,10,9,11) \rightarrow 10-$
 $(8,12,9,13) \rightarrow 1-0-$
 $(8,12,10,14) \rightarrow 1--0$
 $(3,7,11,15) \rightarrow --11\}$
 $(3,11,7,15) \rightarrow --11\}$
 $(6,7,14,15) \rightarrow -11-\}$
 $(6,14,7,15) \rightarrow -11-\}$
 $(9,11,13,15) \rightarrow 1--1\}$
 $(9,13,11,15) \rightarrow 1--1\}$
 $(10,11,14,15) \rightarrow 1-1-\}$
 $(10,14,11,15) \rightarrow 1-1-\}$
 $(12,13,14,15) \rightarrow 11--\}$
 $(12,14,13,15) \rightarrow 11--\}$

STEP:04: $c_1, c_2, p_2, F, 3, 8, 11, m^3 = (1, 3, 8, 11, 7)$

$(8,9,10,11,12,13,14,15) \rightarrow 1---\checkmark$
 $(8,9,10,11,12,14,13,15) \rightarrow 1-12-\checkmark$
 $(8,9,12,13,10,14,11,15) \rightarrow 1-1--$
 $(8,9,12,13,10,11,14,15) \rightarrow 1-1--$
 $(8,10,12,14,9,11,13,15) \rightarrow 1-1--$
 $(8,10,12,14,9,13,11,15) \rightarrow 1-1--$
 $(8,10,9,11,12,14,13,15) \rightarrow 1-1--$
 $(8,10,9,11,12,13,14,15) \rightarrow 1-1--$
 $(8,12,9,13,10,14,11,15) \rightarrow 1-1--$
 $(8,12,10,14,9,11,13,15) \rightarrow 1-1--$
 $(8,12,10,14,9,13,11,15) \rightarrow 1-1--$

1 3 6 7 8 9 10 12 14 15

(8,9,10,11,12,13,14,15) ✓

(X) X (X) (X) X X

(1,3,9,11) ✓

(X) ↑ X

(3,7,11,15)

X X

(6,7,14,15) ✓

(X) X

$$Y = A + \bar{B}D + BC.$$

Petric method:

1 3 6 7 8 9 10 12 14 15

$P_1(8,9,10,11,12,13,14,15)$

(X) X (X) (X) X X

$P_2(1,3,9,11)$

(X) X

$P_3(3,7,11,15)$

X X

$P_4(6,7,14,15)$

(X) X

$$(P_1+P_2)(P_2+P_3)(P_3+P_4)(P_1+P_4)(P_1+P_3) = 1$$


$$(P_1+P_2+P_4)(P_3+P_1+P_2)(P_3+P_4) = 1$$

$$(P_1P_3 + P_1P_2 + P_2P_3 + P_1P_4)(P_3+P_4) = 1$$

$$P_1P_3 + P_1P_2P_3 + P_2P_3 + P_1P_3 + P_1P_3P_4 + P_1P_2P_4 +$$

$$P_2P_3P_4 + P_1P_4 = 1$$

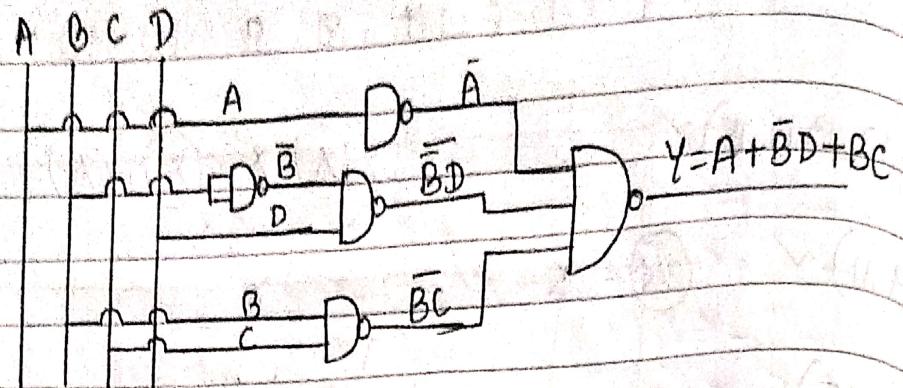
$$P_1P_3 + P_1P_4 + P_1P_2P_3 + P_2P_3 + P_1P_2P_4 + P_2P_3P_4$$



26/08/19

⑦ $F(A, B, C, D) = \sum m(1, 3, 6, 7, 9, 10, 12, 13, 14, 15)$

	A	B	C	D	Step 2	Step 3
01	0	0	0	1	(1,3) $\rightarrow 00-1$	(6,7,14,15) $\rightarrow -11-$ ✓
3	0	0	1	1	(1,9) $\rightarrow 001$	(6,14,7,15) $\rightarrow -11-$
6	0	1	1	0	(3,7) $\rightarrow 0-11$	(12,13,14,15) $\rightarrow 11--$ ✓
9	1	0	0	1	(6,7) $\rightarrow 011-$ ✓	(12,14,13,15) $\rightarrow 11--$
10	1	0	1	0	(6,14) $\rightarrow -110$ ✓	Remaining: (11,0,8)
12	1	1	0	0	(9,13) $\rightarrow 1-01$	(1,3) $\rightarrow 00-1$
13	0	1	1	1	(10,14) $\rightarrow 1-10$	(1,9) $\rightarrow -001$
14	1	1	0	1	(12,13) $\rightarrow 110-$ ✓	(3,7) $\rightarrow 0-11$
15	1	1	1	1	(7,15) $\rightarrow -111$ ✓	(10,14) $\rightarrow 1-101$
					(13,15) $\rightarrow 11-1$ ✓	(11,0,8) $\rightarrow 111-111$
					(14,15) $\rightarrow 111$ ✓	(11,0,8) $\rightarrow 111-111$

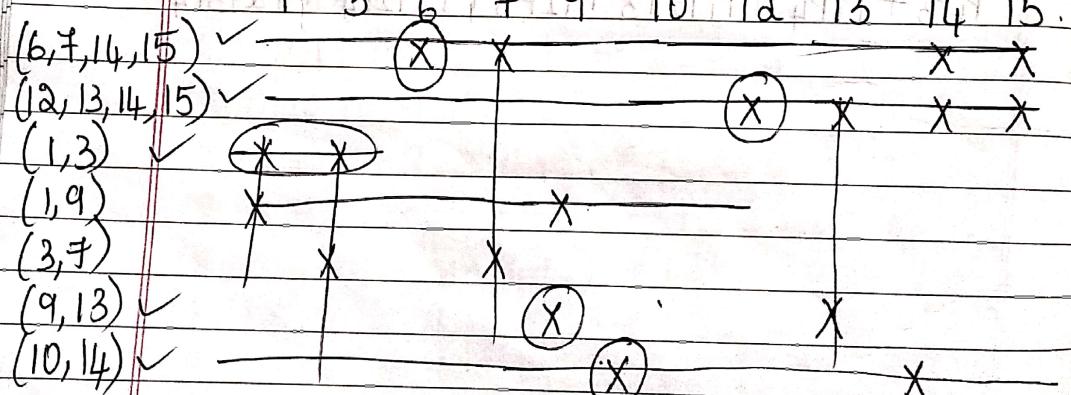

$$Y = BC + AB + \bar{A}BD + A\bar{C}D + A\bar{C}\bar{D}$$

CD:

AB	00	01	11	10	
00	0	1	1	3	2
01	4	5	7	6	
11	1	1	1	1	
10	12	13	14	15	
PB	8	1	9	11	10
\bar{PCD}					

→ $A\bar{B}D$


→ BC

→ $PC\bar{D}$

	1	3	6	7	9	10	12	13	14	15
$P_1(6,7,14,15)$	✓		(X)	X					X	X
$P_2(12,13,14,15)$			(X)	(X)			(X)	X	X	X
$P_3(1,3)$	✓		(X)	(X)						
$P_4(1,9)$			*				X			
$P_5(3,7)$				X						
$P_6(9,13)$	✓					(X)			X	
$P_7(10,14)$	✓					(X)			X	

(No petric)

A B C D

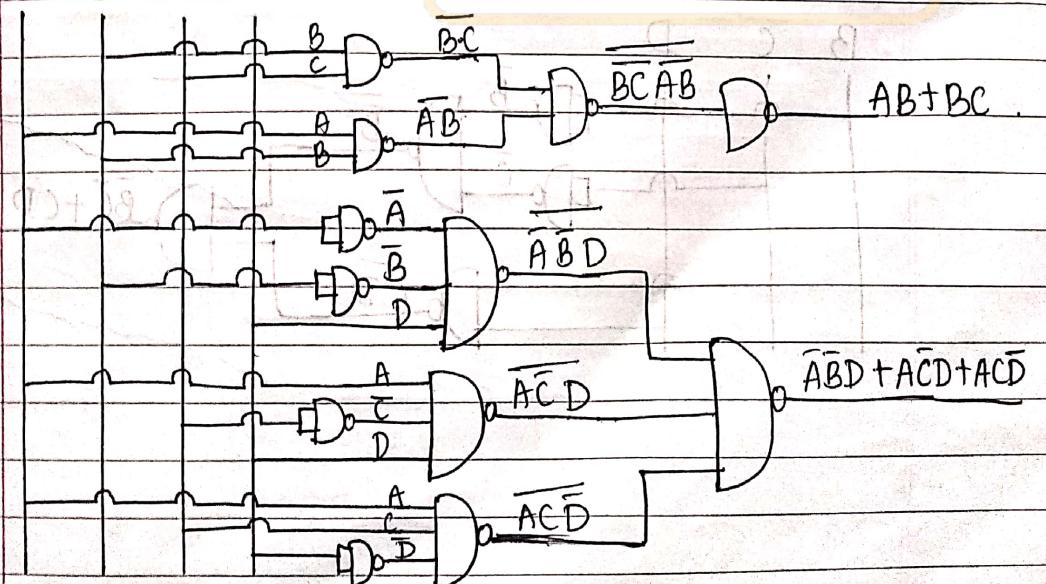

$$⑧ F(A, B, C, D) = \sum m(0, 1, 3, 7, 8, 9, 11, 15)$$

Step 1 Step 2

Step 1

Steps

Step 3.

A	B	C	D		Step 3.
0	0	0	0	$(0,1) \rightarrow 000 - \checkmark$	$(0,1,8,9) \rightarrow -00 - \checkmark$
1	0	0	0	$(0,8) \rightarrow -000 \checkmark$	$(0,8,1,9) \rightarrow -00 - \checkmark$
8	1	0	0	$(1,3) \rightarrow 00 - 1 \checkmark$	$(1,3,9,11) \rightarrow -0-1 \checkmark$
3	0	0	1	$(1,9) \rightarrow -001 \checkmark$	$(1,9,3,11) \rightarrow -0-1 \checkmark$
9	1	0	0	$(8,9) \rightarrow 100 - \checkmark$	$(3,7,11,15) \rightarrow - - 11 \checkmark$
7	0	1	1	$(3,7) \rightarrow 0-11 \checkmark$	$(3,11,7,15) \rightarrow - - 11 \checkmark$
11	1	0	1	$(3,11) \rightarrow -011 \checkmark$	
15	1	1	1	$(9,11) \rightarrow 100 - 1 \checkmark$	
				$(7,15) \rightarrow - - 11 \checkmark$	
				$(11,15) \rightarrow 1-11 \checkmark$	

(1, 3, 9, 11) X X X X X

(3, 7, 11, 15) ✓ — * X X X

$$Y = \bar{B}\bar{C} + CD$$

