

9.4.2 Operation with RL Load

Voltage and current waveforms for single-phase bridge inverter with RL load are shown in Fig. 9.8. The operation of the circuit is explained in four-modes.

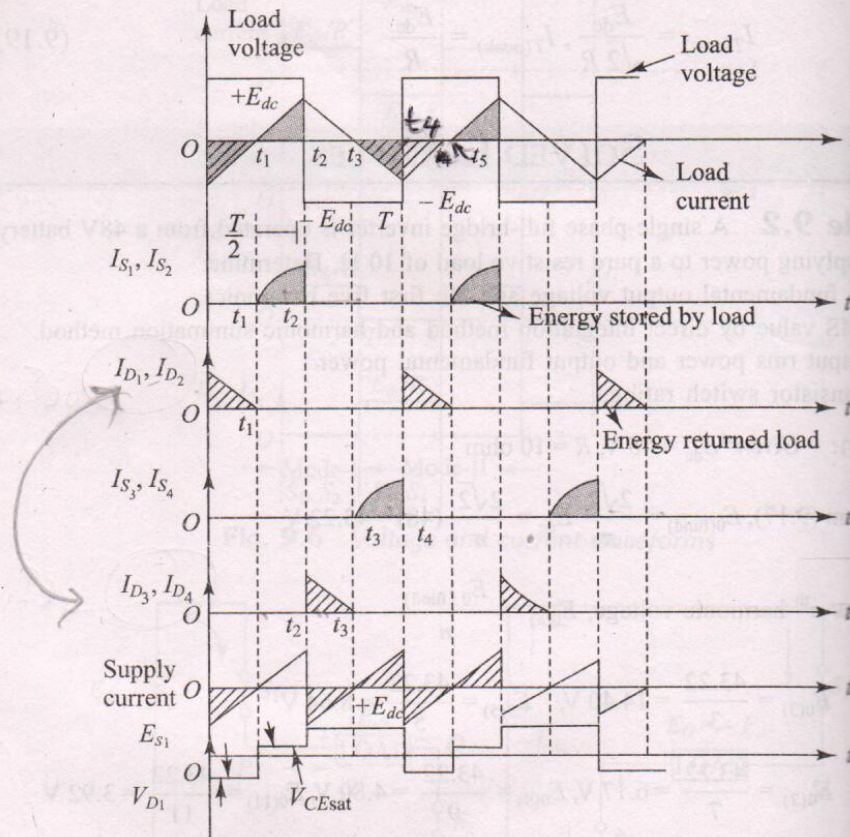


Fig. 9.8 Voltage and current waveforms

(i) Mode-I ($t_1 < t < t_2$): At instant t_1 , the switch S_1 and S_2 are turned-on. Switches are assumed to be ideal switches. Point P gets connected to positive point of d.c. Source E_{dc} through S_1 and point Q gets connected to negative point of input supply. The output voltage, $e_o = +E_{dc}$, Fig. 9.9(a). The load current starts increasing exponentially due to the inductive nature of the load. The instantaneous current through S_1 and S_2 is equal to the instantaneous load current. During this interval, energy is stored in inductive load.

(ii) Mode-II ($t_2 < t < t_3$): Both the switches Q_1 and Q_2 are turned-off at instant t_2 . Due to the inductive nature of the load, the load current does not reduce to zero instantaneously. There is a self-induced voltage across the load which maintains the flow of current in the same-direction. The polarity of the voltage is exactly opposite to that in mode-1, The output voltage becomes $-E_{dc}$ but the load current continues to flow in the same direction, through D_3 and D_4 as shown in Fig. 9.9(b). Thus, in this mode, the stored energy in the load inductor

back to the source. Load current decreases exponentially and goes to zero at t_3 when all the energy stored in the load is returned back to supply. D_3 and D_4 are turned-off at t_3 .

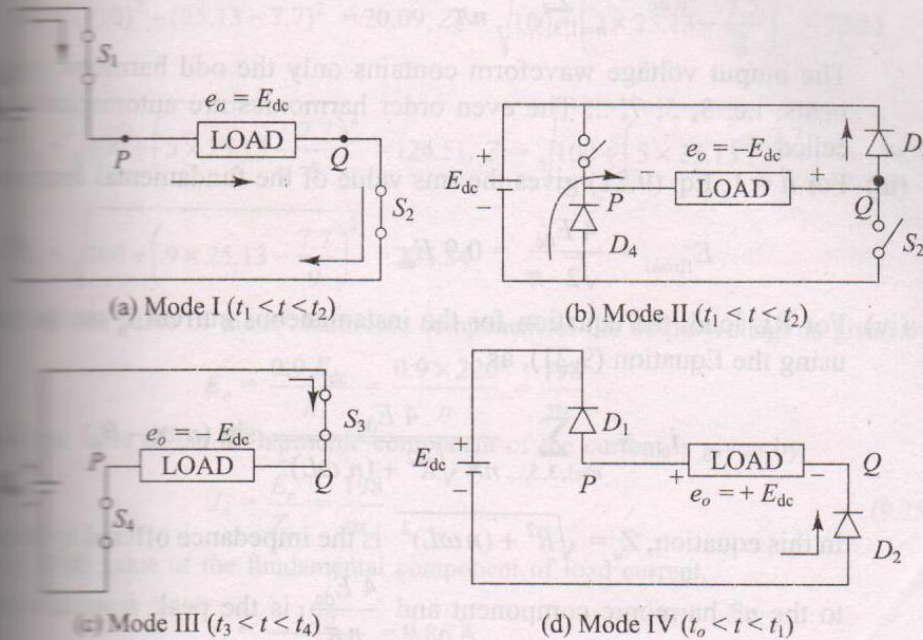


Fig. 9.9 Equivalent circuits

Mode III ($t_3 < t < t_4$): Switches S_3 and S_4 are turned-on simultaneously at instant t_3 . Load voltage remains negative ($-E_{dc}$) but the direction of load current will reverse. The current increases exponentially in the other direction and the load again stores the energy.

Mode IV ($t_0 < t < t_1$): Switches S_3 and S_4 are turned-off at instant t_0 (or t_4). The load inductance tries to maintain the load current in the same direction by inducing the positive-load voltage. This will forward-bias the diodes D_1 and D_2 . Stored energy is returned back to the input dc supply. The load voltage becomes $eo = +E_{dc}$ but the load current remains negative and decreases exponentially towards zero. At t_1 (or t_5), the load current goes to zero and switches S_1 and S_2 can be turned-on again. The conduction period with a very highly inductive load, will be 180° for all the switches as well as the diodes. The conduction period of switches will increase towards $T/2$ or 180° with increase in the load power-factor.

Output Analysis

The RMS output voltage can be obtained from

$$E_{0\text{rms}} = \left[\frac{2}{T/2} \int_0^{T/2} E^2 dt \right]^{1/2} \quad \therefore E_{0\text{rms}} = E_{dc} \quad (9.20)$$