

Similarly, we obtain y_{12} and y_{22} by connecting a current source I_2 to port 2 and shorting port 1 as in Fig. 7.4, finding I_1 and V_2 , and then calculating,

$$y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

$$y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

y_{12} is called the *short-circuit trans-admittance* and y_{22} is called the *short-circuit output admittance*. Collectively the parameters are referred to as short-circuit admittance parameters.

Please note that $y_{12} = y_{21}$ only when there are no dependent sources or Op-amps within the two-port network.

7.1

Determine the admittance parameters of the T network shown in Fig. 7.5.

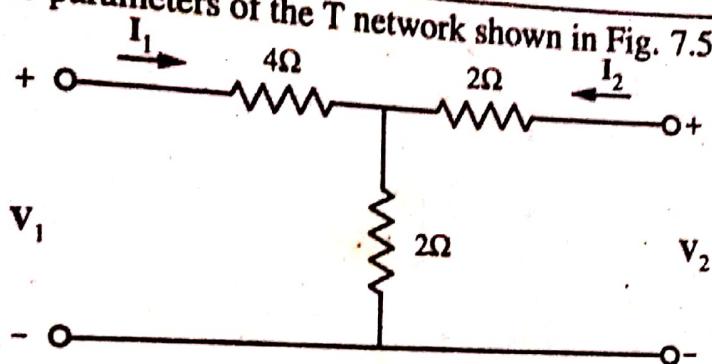


Figure 7.5

To find y_{11} and y_{21} , we have to short the output terminals and connect a current source I_1 to the input terminals. The circuit so obtained is shown in Fig. 7.6(a).

$$I_1 = \frac{V_1}{4 + \frac{2 \times 2}{2+2}} = \frac{V_1}{5}$$

$$\text{Hence, } y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = \frac{1}{5} S$$

Using the principle of current division,

$$-I_2 = \frac{I_1 \times 2}{2+2} = \frac{I_1}{2}$$

$$\Rightarrow -I_2 = \frac{1}{2} \left[\frac{V_1}{5} \right]$$

$$\text{Hence, } y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} = \frac{-1}{10} S$$

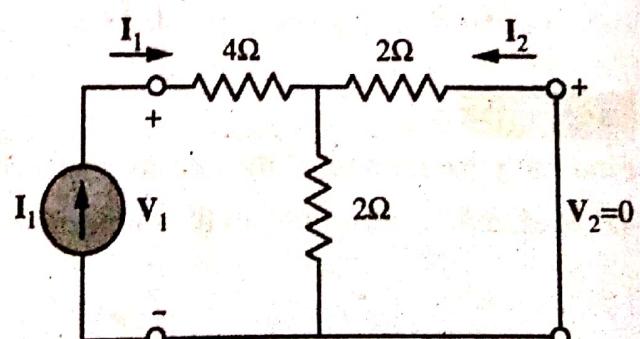


Figure 7.6(a)

To find y_{12} and y_{22} , we have to short-circuit the input terminals and connect a current source I_2 to the output terminals. The circuit so obtained is shown in Fig. 7.6(b).

$$I_2 = \frac{V_2}{2 + \frac{4 \times 2}{4 + 2}}$$

$$= \frac{V_2}{2 + \frac{8}{6}} = \frac{V_2}{\frac{10}{3}}$$

$$= \frac{3V_2}{10}$$

$$\text{Hence, } y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = \frac{3}{10} \text{ S}$$

Employing the principle of current division, we have

$$-I_1 = \frac{I_2 \times 2}{2 + 4}$$

$$\Rightarrow -I_1 = \frac{2I_2}{6}$$

$$\Rightarrow -I_1 = \frac{1}{3} \left[\frac{3V_2}{10} \right]$$

Hence,

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} = \frac{-1}{10} \text{ S}$$

It may be noted that, $y_{12} = y_{21}$. Thus, in matrix form we have

$$\begin{aligned} I &= YV \\ \Rightarrow \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} &= \begin{bmatrix} \frac{1}{5} & -\frac{1}{10} \\ -\frac{1}{10} & \frac{3}{10} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \end{aligned}$$

EXAMPLE 7.2

Find the y parameters of the two-port network shown in Fig. 7.7. Then determine the current in a 4Ω load, that is connected to the output port when a $2A$ source is applied at the input port.

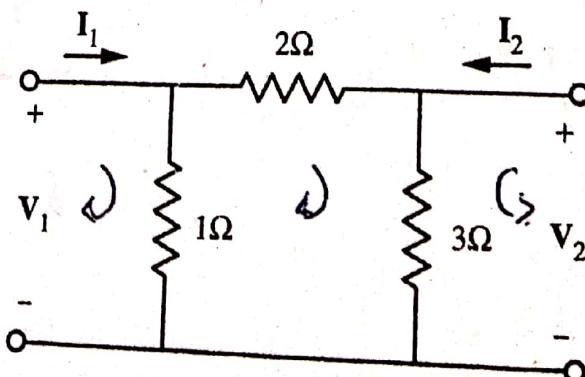



Figure 7.7

y_{11} and y_{21} , short-circuit the output terminals and connect a current source I_1 to the input terminals. The resulting circuit diagram is shown in Fig. 7.8(a).

$$I_1 = \frac{V_1}{1\Omega \parallel 2\Omega} = \frac{V_1}{\frac{1 \times 2}{1+2}} = \frac{V_1}{\frac{2}{3}}$$

$$\Rightarrow I_1 = \frac{3}{2}V_1$$

$$\text{Hence, } y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = \frac{3}{2}S$$

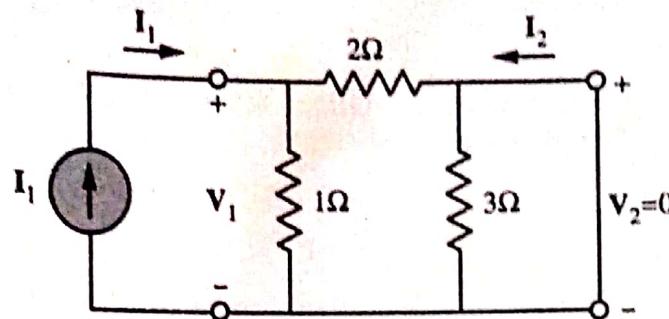

Using the principle of current division,

Figure 7.8(a)

$$-I_2 = \frac{I_1 \times 1}{1+2}$$

$$\Rightarrow -I_2 = \frac{1}{3}I_1$$

$$\Rightarrow -I_2 = \frac{1}{3} \left[\frac{3}{2}V_1 \right]$$

$$\text{Hence, } y_{21} = \frac{I_2}{V_1} = \frac{-1}{2}S$$

To find y_{12} and y_{22} , short the input terminals and connect a current source I_2 to the output terminals. The resulting circuit diagram is shown in Fig. 7.8(b).

$$I_2 = \frac{V_2}{2\Omega \parallel 3\Omega}$$

$$= \frac{V_2}{\frac{2 \times 3}{2+3}} = \frac{5V_2}{6}$$

$$y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = \frac{5}{6}S$$

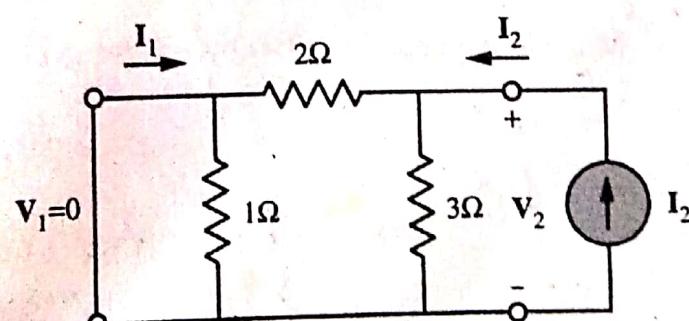


Figure 7.8(b)

Employing the current division principle,

$$-I_1 = \frac{I_2 \times 3}{2+3}$$

$$\Rightarrow -I_1 = \frac{3}{5}I_2$$

$$\Rightarrow -I_1 = \frac{3}{5} \left[\frac{5V_2}{6} \right]$$

$$\Rightarrow I_1 = \frac{-1}{2} V_2$$

Hence,

$$y_{12} = \left. \frac{-I_1}{V_2} \right|_{V_1=0} = \frac{-1}{2} S$$

Therefore, the equations that describe the two-port network are

$$I_1 = \frac{3}{2} V_1 - \frac{1}{2} V_2 \quad (7.3)$$

$$I_2 = -\frac{1}{2} V_1 + \frac{5}{6} V_2 \quad (7.4)$$

Putting the above equations (7.3) and (7.4) in matrix form, we get

$$\begin{bmatrix} \frac{3}{2} & \frac{-1}{2} \\ \frac{-1}{2} & \frac{5}{6} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Referring to Fig. 7.8(c), we find that $I_1 = 2A$ and $V_2 = -4I_2$

Substituting $I_1 = 2A$ in equation (7.3), we get

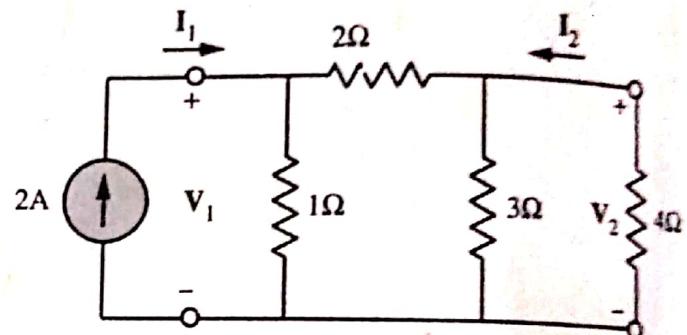


Figure 7.8(c)

$$2 = \frac{3}{4} V_1 - \frac{1}{2} V_2 \quad (7.5)$$

Multiplying equation (7.4) by -4 , we get

$$\begin{aligned} -4I_2 &= 2V_1 - \frac{20}{6} V_2 \\ \Rightarrow V_2 &= 2V_1 - \frac{20}{6} V_2 \\ \Rightarrow 0 &= 2V_1 - \left(\frac{20}{6} + 1 \right) V_2 \\ \Rightarrow 0 &= \frac{-1}{2} V_1 + \frac{13}{12} V_2 \end{aligned} \quad (7.6)$$

Putting equations (7.5) and (7.6) in matrix form, we get

$$\begin{bmatrix} \frac{3}{2} & \frac{-1}{2} \\ \frac{-1}{2} & \frac{13}{12} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \end{bmatrix}$$

It may be noted that the above equations are simply the nodal equations for the circuit shown in Fig. 7.9. Solving these equations, we get

$$V_2 = \frac{3}{2} V$$

$$I_2 = \frac{-1}{4} V_2 = \frac{-3}{8} A$$

EXAMPLE 7.3

For the network shown in the Fig. 7.9 containing a current-controlled current source. For this network, find the y parameters.

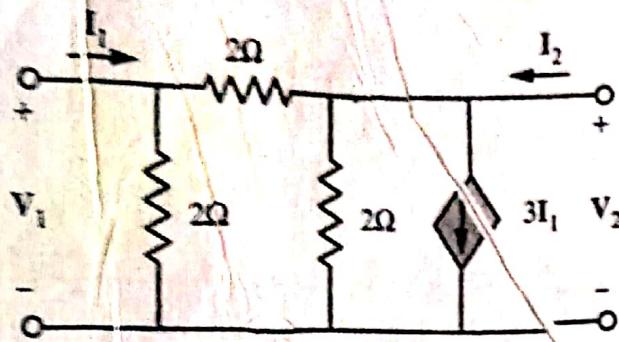


Figure 7.9

SOLUTION
To find y_{11} and y_{21} , short the output terminals and connect a current source I_1 to the input terminals. The resulting circuit diagram is as shown in Fig. 7.10(a) and it is further reduced to Fig. 7.10(b).

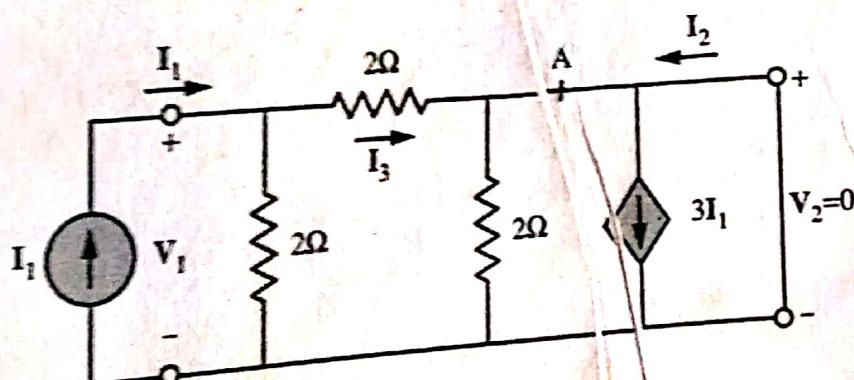


Figure 7.10(a)

$$\begin{aligned} I_1 &= \frac{V_1}{2 \times 2} \\ &= \frac{V_1}{2+2} \\ \Rightarrow I_1 &= \frac{V_1}{4} \\ y_{11} &= \left. \frac{I_1}{V_1} \right|_{V_2=0} = 1S \end{aligned}$$

Hence,

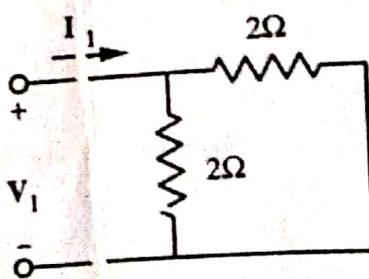


Figure 7.10(b)

Applying KCL at node A gives (Referring to Fig. 7.10(a)).

$$\begin{aligned} I_3 + I_2 &= 3I_1 \\ \Rightarrow \frac{V_1}{2} + I_2 &= 3I_1 \\ \Rightarrow \frac{V_1}{2} + I_2 &= 3V_1 \\ \Rightarrow \frac{5V_1}{2} &= I_2 \end{aligned}$$

Hence,

$$y_{21} = \frac{I_2}{V_1} = \frac{5}{2} S$$

To find y_{22} and y_{12} , short the input terminals and connect a current source I_2 at the output terminals. The resulting circuit diagram is shown in Fig. 7.10(c) and further reduced to Fig. 7.10(d).

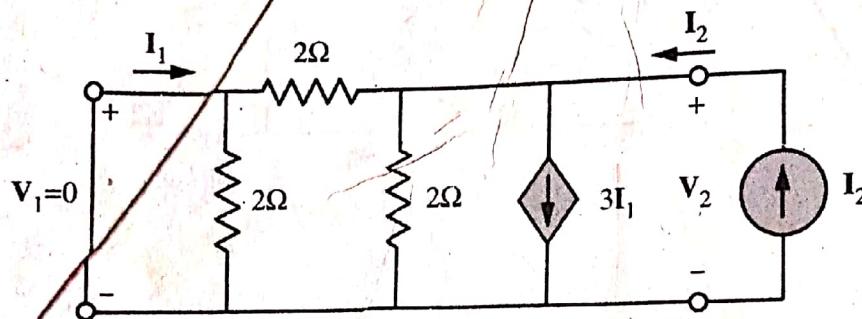


Figure 7.10(c)

$$I_2 = -I'_1 = -\frac{V_2}{2}$$

$$-I_1 = \frac{V_2}{2}$$

$$y_{12} = \frac{I_1}{V_2} = \frac{-1}{2} S$$

Hence,

Applying KCL at node B gives

$$I_2 = \frac{V_2}{2} + \frac{V_1}{2} + 3I_1$$

But

$$I_1 = \frac{-V_2}{2}$$

Hence,

$$I_2 = \frac{V_2}{2} + \frac{V_2}{2} - 3\frac{V_2}{2}$$

$$\Rightarrow y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = -0.5 S$$

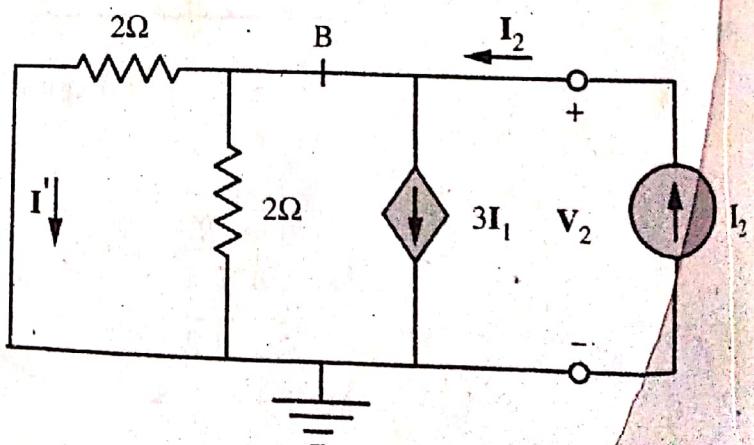


Figure 7.10(d)

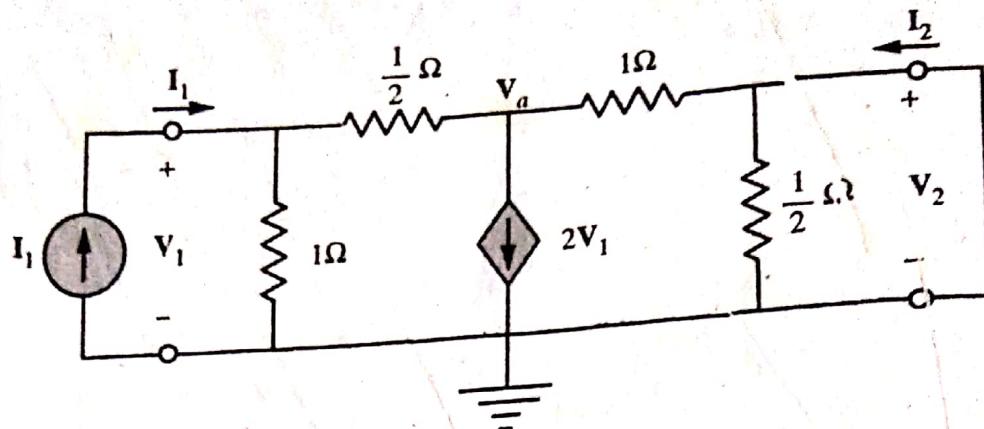


Figure 7.12(a)

KCL at node V₁:

$$\begin{aligned} I_1 &= \frac{V_1}{1} + \frac{V_1 - V_a}{\frac{1}{2}} \\ \Rightarrow \quad 3V_1 - 2V_a &= I_1 \end{aligned} \tag{7.7}$$

KCL at node V_a:

$$\begin{aligned} \frac{V_a - V_1}{\frac{1}{2}} + \frac{V_a - 0}{1} + 2V_1 &= 0 \\ \Rightarrow \quad 2V_a - 2V_1 + V_a + 2V_1 &= 0 \\ \Rightarrow \quad V_a &= 0 \end{aligned} \tag{7.8}$$

Making use of equation (7.8) in (7.7), we get

$$3V_1 = I_1$$

$$\text{Hence, } y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = 3S$$

Since V_a = 0, I₂ = 0,

$$\Rightarrow \quad y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = 0S$$

To find y₂₂ and y₁₂ short-circuit the input terminals and connect a current source I₂ to the output terminals. The resulting circuit diagram is shown in Fig. 7.12(b).

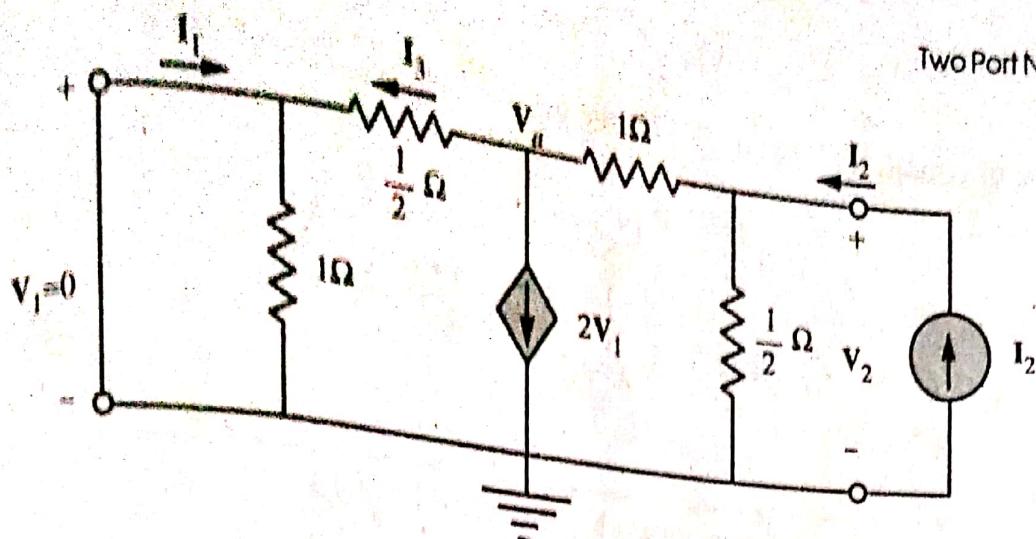


Figure 7.12(b)

CL at node V_2 :

$$\frac{V_2}{\frac{1}{2}} + \frac{V_2 - V_a}{1} = I_2$$

$$\Rightarrow 3V_2 - V_a = I_2 \quad (7.9)$$

CL at node V_a :

$$\frac{V_a - V_2}{1} + \frac{V_a - 0}{\frac{1}{2}} + 0 = 0$$

$$\Rightarrow 3V_a - V_2 = 0$$

$$\text{or } V_a = \frac{1}{3}V_2 \quad (7.10)$$

Substituting equation (7.10) in (7.9), we get

$$3V_2 - \frac{1}{3}V_2 = I_2$$

$$\Rightarrow \frac{8}{3}V_2 = I_2$$

$$y_{22} = \frac{I_2}{V_2} = \frac{8}{3}S$$

$$V_a = \frac{1}{3}V_2 \quad (7.11)$$

Hence,

We have,

Also,

$$I_1 + I_3 = 0$$

$$I_1 = -I_3$$

$$= \frac{-V_a}{\frac{1}{2}} = -2V_a \quad (7.12)$$

Making use of equation (7.12) in (7.11), we get

$$-\frac{I_1}{2} = \frac{1}{3}V_2$$

Hence,

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} = \frac{-2}{3} S$$

EXAMPLE 7.5

Find the y parameters for the resistive network shown in Fig. 7.13.

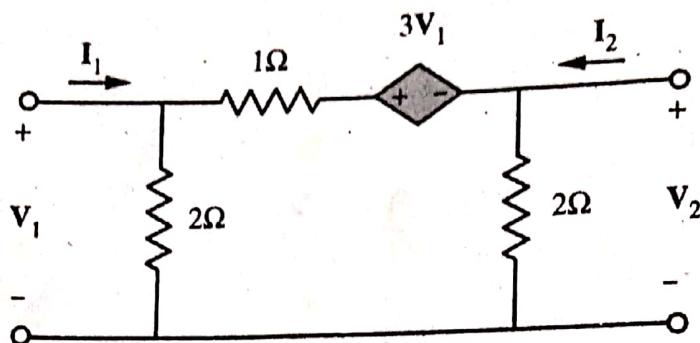


Figure 7.13

SOLUTION

Converting the voltage source into an equivalent current source, we get the circuit diagram shown in Fig. 7.14(a).

To find y_{11} and y_{21} , the output terminals of Fig. 7.14(a) are shorted and connect a current source I_1 to the input terminals. This results in a circuit diagram as shown in Fig. 7.14(b).

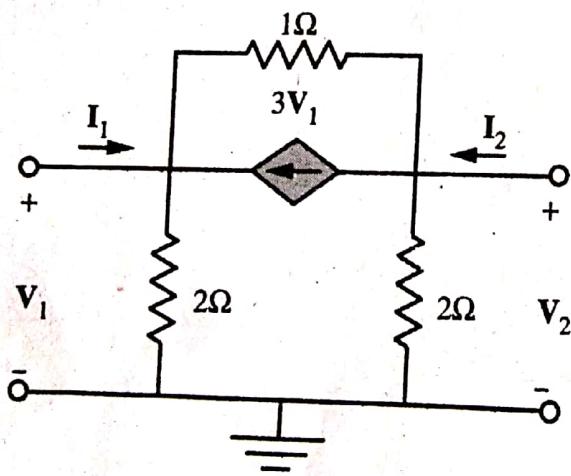


Figure 7.14(a)

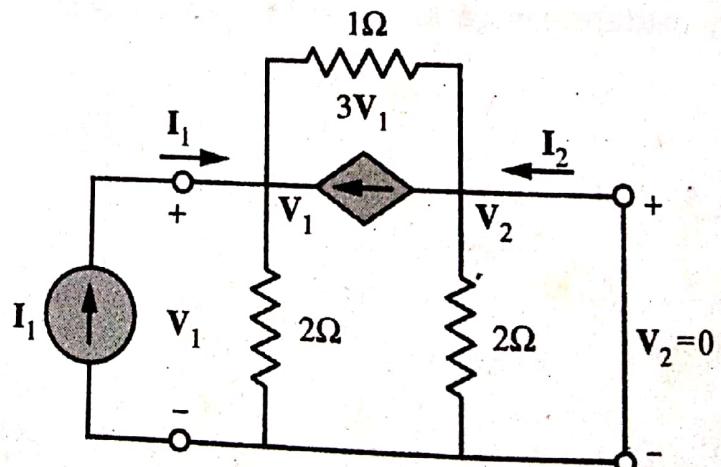


Figure 7.14(b)

KCL at node V_1 :

$$\frac{V_1}{2} + \frac{V_1 - V_2}{1} = I_1 + 3V_1$$

Since $V_2 = 0$, we get

$$\frac{V_1}{2} + V_1 = I_1 + 3V_1$$

$$\Rightarrow I_1 = \frac{-3}{2}V_1$$

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = \frac{-3}{2} S$$

Hence,

KCL at node V_2 :

$$\frac{V_2}{2} + 3V_1 + \frac{V_2 - V_1}{1} = I_2$$

Since $V_2 = 0$, we get

$$0 + 3V_1 - V_1 = I_2$$

$$\Rightarrow I_2 = 2V_1$$

$$y_{21} = \frac{I_2}{V_2} = 2S$$

Hence

To find y_{21} and y_{22} , the input terminals of Fig. 7.14(a) are shorted and connect a current source I_2 to the output terminals. This results in a circuit diagram as shown in Fig. 7.14(c).

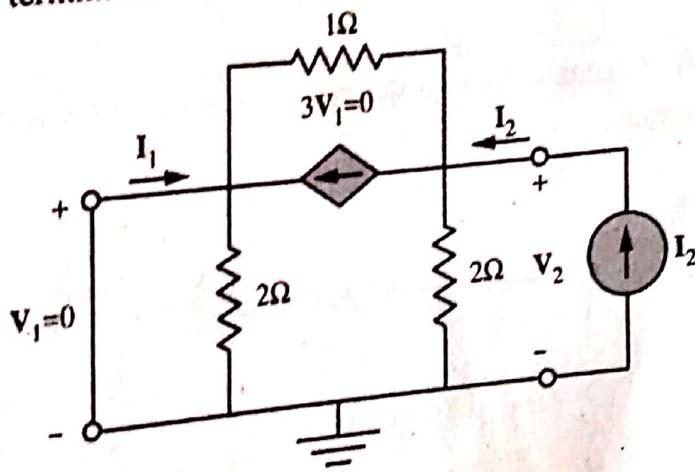


Figure 7.14(c)

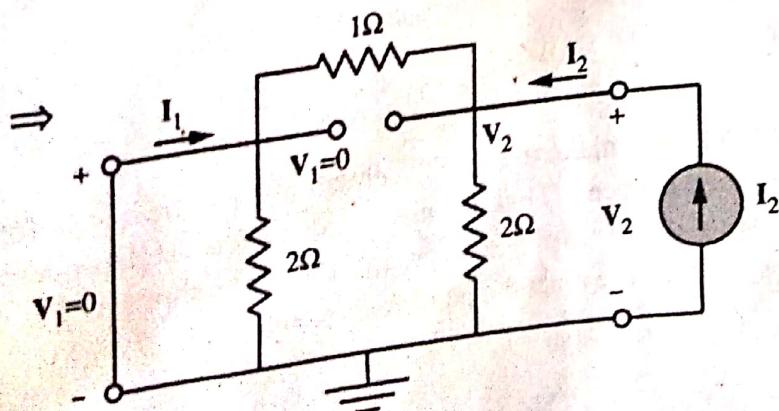


Figure 7.14(d)

KCL at node V_2 :

$$\frac{V_2}{2} + \frac{V_2 - 0}{1} = I_2$$

\Rightarrow

$$\frac{3}{2}V_2 = I_2$$

Hence,

$$y_{22} = \frac{I_2}{V_2} = \frac{3}{2}S$$

KCL at node V_1 :

$$I_1 = \frac{V_1}{2} + \frac{V_1 - V_2}{1} = 0$$

Since $V_1 = 0$, we get

$$I_1 = -V_2$$

Hence,

$$y_{12} = \frac{I_1}{V_2} = -1S$$

EXAMPLE 7.6

The network of Fig. 7.15 contains both a dependent current source and a dependent voltage source. Find the y parameters.

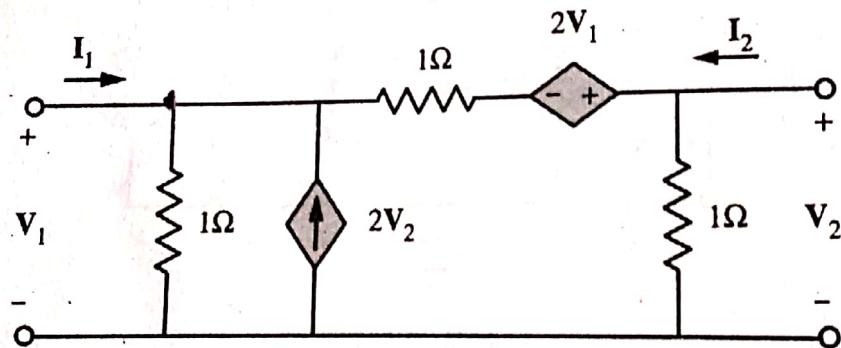


Figure 7.15

SOLUTION

While finding y parameters, we make use of KCL equations. Hence, it is preferable to have current sources rather than voltage sources. This prompts us to convert the dependent voltage source into an equivalent current source and results in a circuit diagram as shown in Fig. 7.16(a).

To find y_{11} and y_{21} , refer the circuit diagram as shown in Fig. 7.16(b).

KCL at node V_1 :

$$\frac{V_1}{1} + \frac{V_1 - V_2}{1} + 2V_1 = 2V_2 + I_1$$

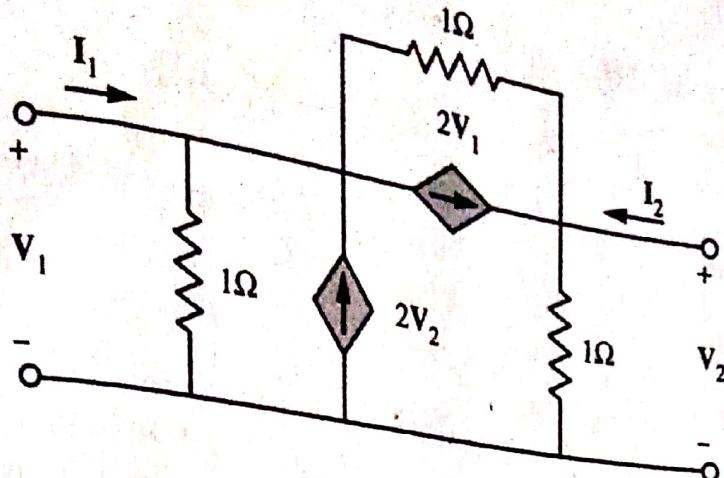


Figure 7.16(a)

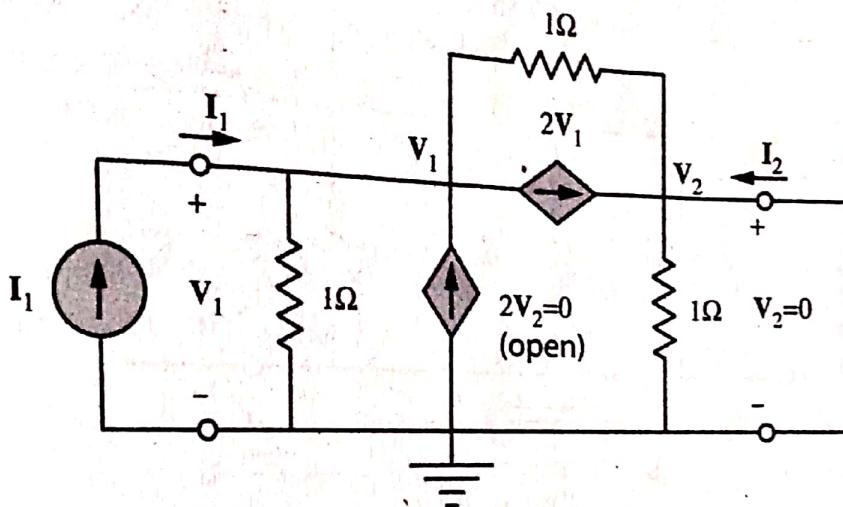


Figure 7.16(b)

Since $V_2 = 0$, we get

$$\begin{aligned} V_1 + V_1 + 2V_1 &= I_1 \\ 4V_1 &= I_1 \\ y_{11} &= \frac{I_1}{V_1} = 4S \end{aligned}$$

Hence,

KCL at node V_2 :

$$\frac{V_2}{1} + \frac{V_2 - V_1}{1} = 2V_1 + I_2$$

Since $V_2 = 0$, we get

$$\begin{aligned} -V_1 &= 2V_1 + I_2 \\ -3V_1 &= I_2 \\ y_{21} &= \left. \frac{I_2}{V_1} \right|_{V_2=0} = -3S \end{aligned}$$

Hence,

To find y_{22} and y_{12} , refer the circuit diagram shown in Fig. 7.16(c).
KCL at node V_1 :

$$\frac{V_1}{1} + \frac{V_1 - V_2}{1} + 2V_1 = 2V_2 + I_1$$

Since $V_1 = 0$, we get

$$\Rightarrow \begin{aligned} -V_2 &= 2V_2 + I_1 \\ -3V_2 &= I_1 \end{aligned}$$

Hence,

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0} = -3S$$

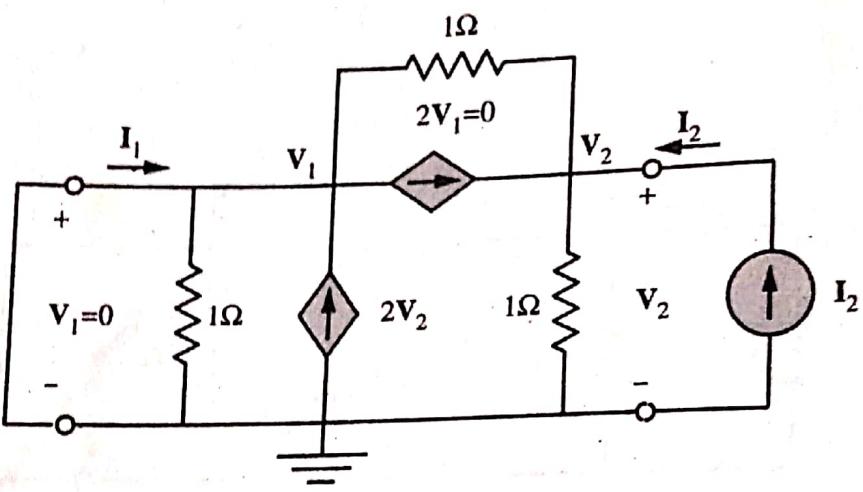


Figure 7.16(c)

KCL at node V_2 :

$$\frac{V_2}{1} + \frac{V_2 - V_1}{1} = 2V_1 + I_2$$

Since $V_1 = 0$, we get

$$V_2 + V_2 = 0 + I_2$$

$$\Rightarrow -2V_2 = I_2$$

Hence,

$$y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0} = 2S$$

7.3 Impedance parameters

Let us assume the two port network shown in Fig. 7.17 is a linear network that contains no independent sources. Then using superposition theorem, we can write the input and output voltages as the sum of two components, one due to I_1 and other due to I_2 :

$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$

