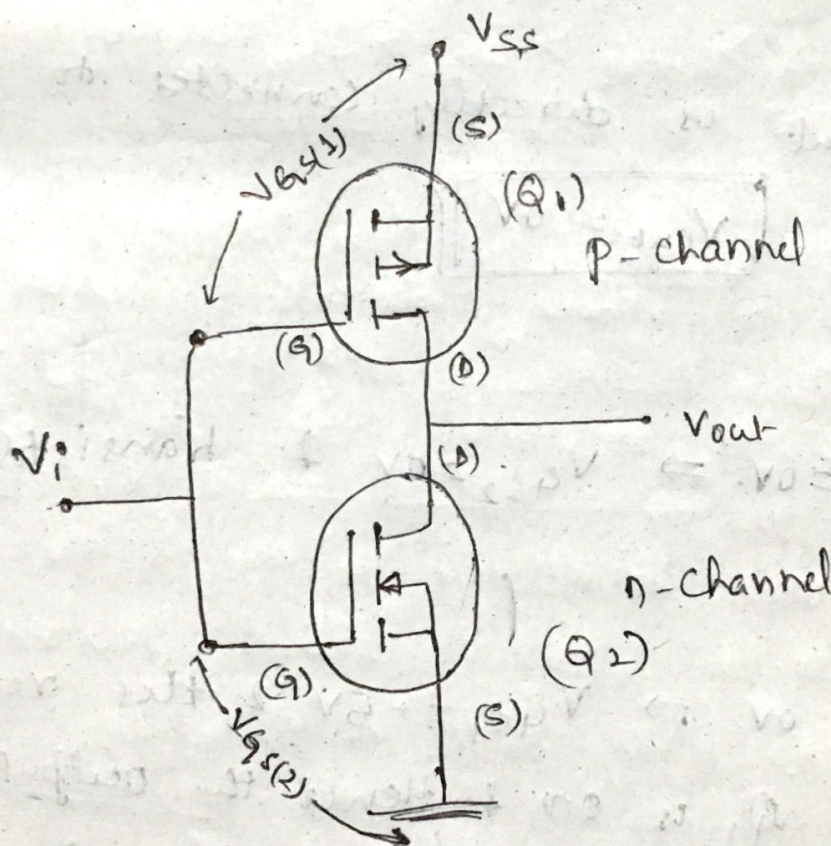


CMOS

(Complementary metaloxide semiconductor Field effect transistor)

A very effective logic circuit can be established by constructing a p-channel & n-channel MOSFET on the same substrate as is shown below. A very effective use of complementary arrangement is as an Inverter.



In the above figure both the gates are connected to the input voltage (V_i), both the drains are connected to the o/p voltage (V_{out}), the source of p-channel MOSFET is connected to the V_{ss} .

where source of n-channel MOSFET is connected to the Ground.

⇒ when $V_i = 5V \Rightarrow V_{GS(2)} = V_i$ & transistors

Q_2 is on.

|||⁴
 V_i & V_{SS} are at same +5V hence

$V_{GS(1)} = 0V$ this results transistors Q_1 is

off

V_{out} is directly connected to ground
 Hence $V_{out} = 0V$

⇒ when $V_i = 0V \Rightarrow V_{GS(2)} = 0V$ & transistors Q_2 is

off

|||⁴
 $V_i = 0V \Rightarrow V_{GS(1)} = -5V$ & this results

transistors Q_1 is on & hence the output voltage

(V_{out}) is directly connected to the V_{SS} &


$V_{out} = +5V$

	i/p	o/p
①	0V	+5V
②	5V	0V

SCR (silicon controlled rectifier)

V-I characteristics

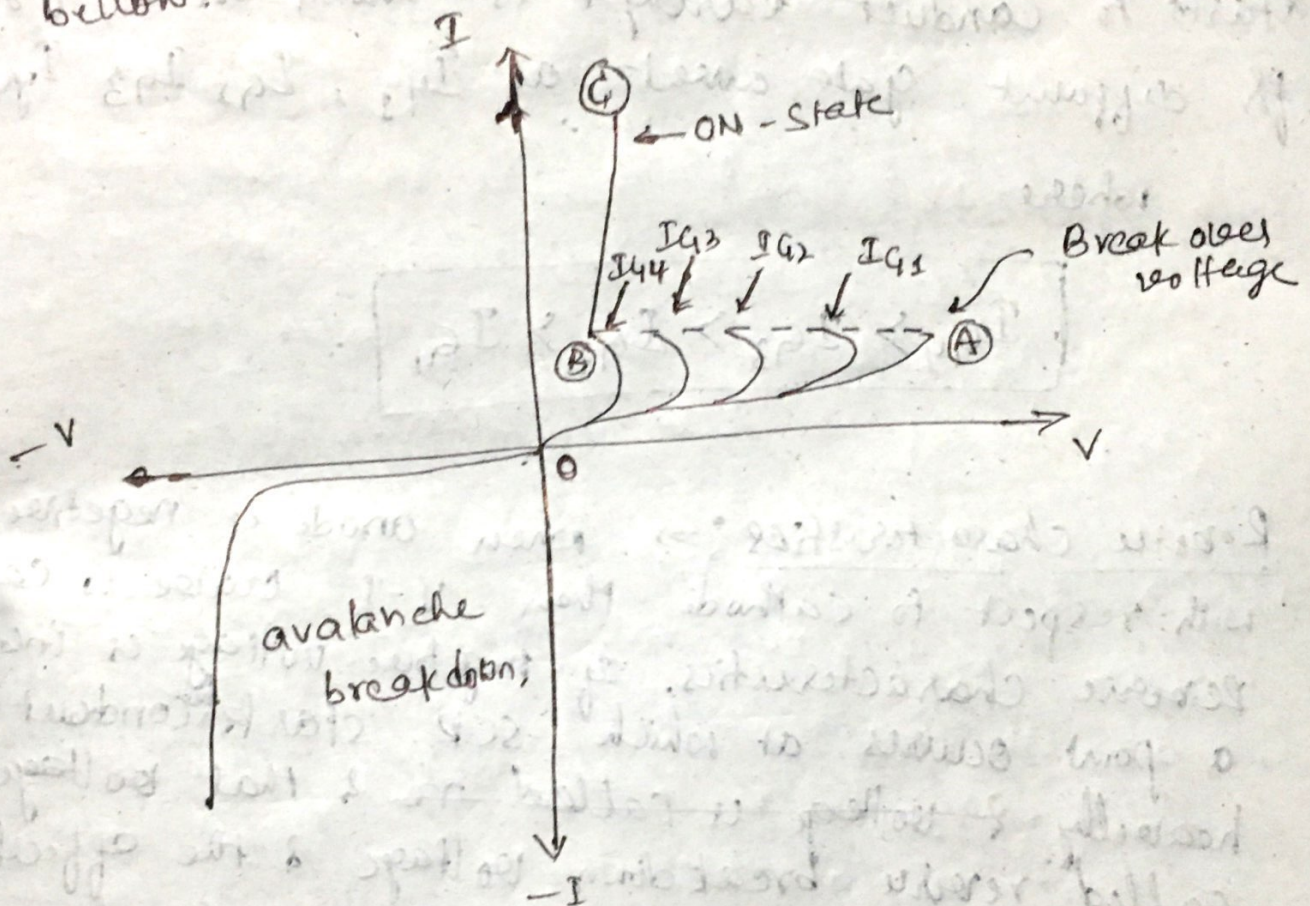It is the graphical curve b/w anode-cathode voltage & anode current. & is shown below.



Forward characteristics :- When the anode is positive with respect to cathode, the curve b/w $V-I$ is called forward characteristic. $OABC$ is forward characteristic of SCR at $I_G = 0$. When a supply voltage is increased from zero, then a point A is reached the SCR starts conducting. ~~under~~ the voltage is called breakover voltage.

Under this condition voltage across SCR suddenly drops as shown by the dotted curve AB & most of supply voltage appear across the load resistance R.

If proper gate voltage is applied then SCR starts to conduct early & is shown in the figure for different gate current as I_{G1} , I_{G2} , I_{G3} , I_{G4} .



where

$$I_{G4} > I_{G3} > I_{G2} > I_{G1}$$

Reverse characteristics : \Rightarrow when anode is negative with respect to cathode then V-I curve is called reverse characteristics. If negative voltage is increased a point occurs at which SCR starts to conduct heavily & ~~voltage is called~~ V_R & that voltage is called reverse breakdown voltage & the effect that conducts current is called avalanche breakdown. It is shown in the figure.

Two transistor model of SCR

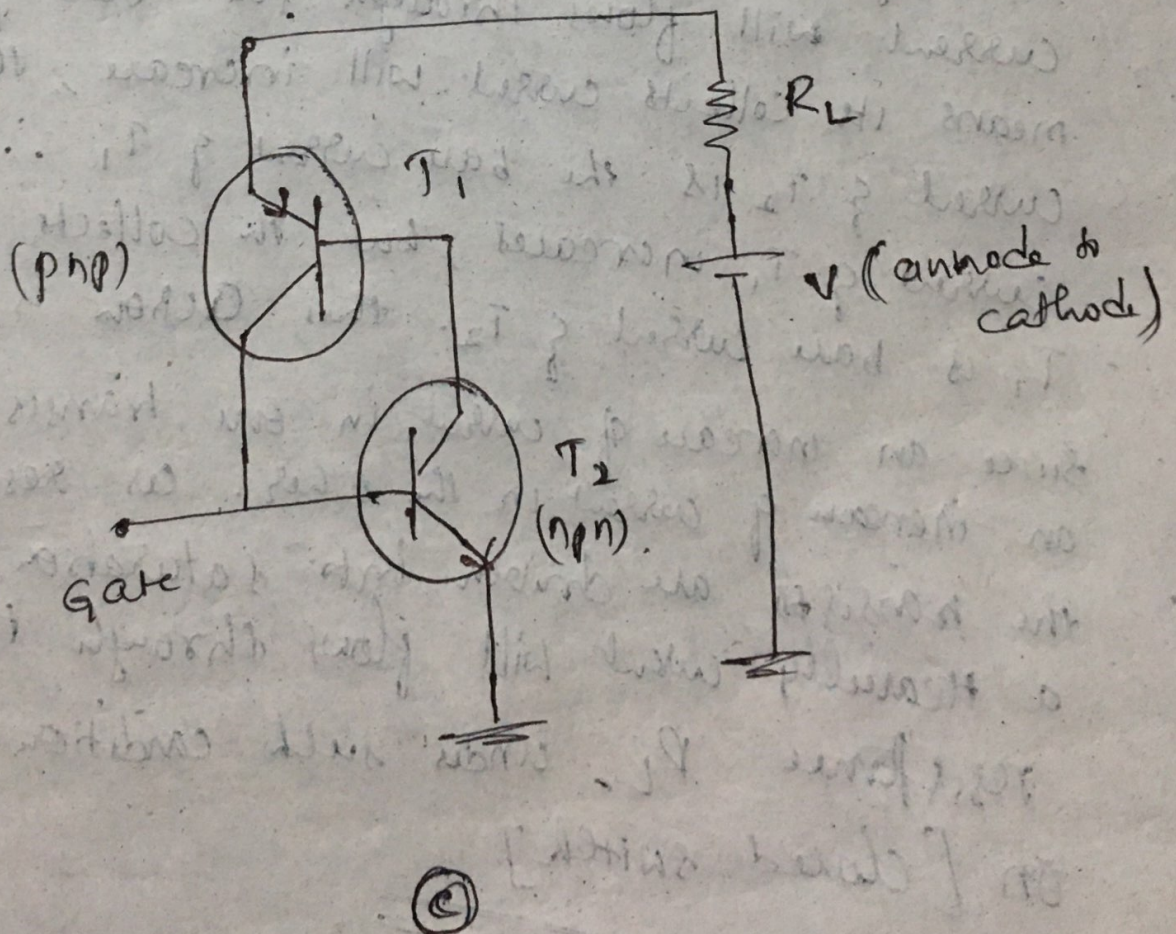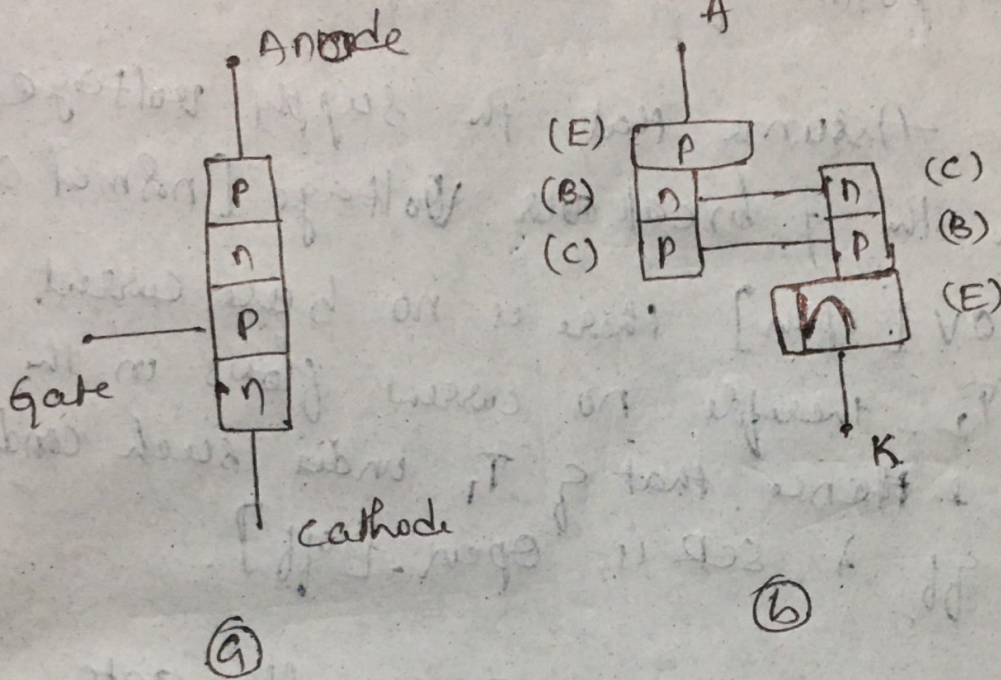The fig shows the two transistor model of SCR



The equivalent circuit of SCR is composed of npn & pnp transistors. In the figure the collector of each is coupled to the base of other there by making a positive feedback loop.

operation :- Assume that the supply voltage is less than the break over voltage [normal case]
⇒ with gate = 0V [open] there is no base current in transistors T_2 . therefore no current flows in the collector T_2 & hence that of T_1 under such condition T_1 & T_2 are off & SCR is open. [off].

⇒ with gate = +ve voltage: a small gate current will flow through the base of T_2 which means its collector current will increase, the collector current of T_2 is the base current of T_1 . ∴ the collector current of T_1 increases; but the collector current of T_1 is base current of T_2 . this action is accumulation since an increase of current in one transistor causes an increase of current in the other. as result of this the transistors are driven into saturation & hence a heavily current will flow through the load resistance R_L under such condition SCR is on [closed switch]
